

Binary Blah Blah!

- The Binary system comprises only two numbers viz. 0 and 1.

- Numbers could be of the form:

- 00, 01, 10, 11

(meaning 0, 1, 2, 3 in decimal)

- Thus,

$$(0101)_2 = 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

Similarly,

$$(110.01)_2 = 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 + 0 \times 2^{-1} + 1 \times 2^{-2}$$

Bits, Nibbles and Bytes!

- **Bit:** Binary digiT
- 4 bits make a Nibble e.g. 1011
- 8 bits make a Byte e.g. 11001101
- Using 2 bits we can generate 4 combinations viz. 00, 01, 10, 11 standing for 0, 1, 2 and 3 in the decimal system
- Thus, using n bits we can generate 2^n combinations

Thinking in terms of 0s and 1s

The Truth Table

A	B	C	P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0



The buzzer P is activated only under this condition -

A=1, B=1, C=0

A is **TRUE** **AND** B is **TRUE** **AND** C is **FALSE**

Observe that there is some logic that drives P

LOGIC GATES




- A **logic gate** is an electronic component whose output is computed based on a function of the inputs.
- A gate can have one or more inputs.
- Inputs may be given directly as **0 (LOW VOLTAGE*)** or **1 (HIGH VOLTAGE*)** or they could be derived from the output of other logic gates.
- * LOW generally means 0V and HIGH generally means 3V or 5V.
- Computers use a very large number of such interconnected gates.

LOGIC GATES: AND

P

- In order for current to flow & the lamp light up, both switches must be closed

- Logic notation $A \cdot B = C$

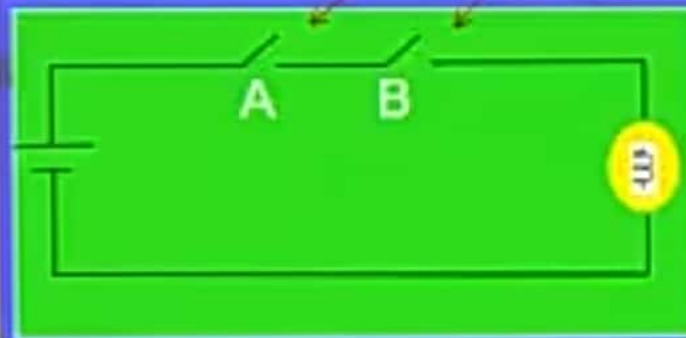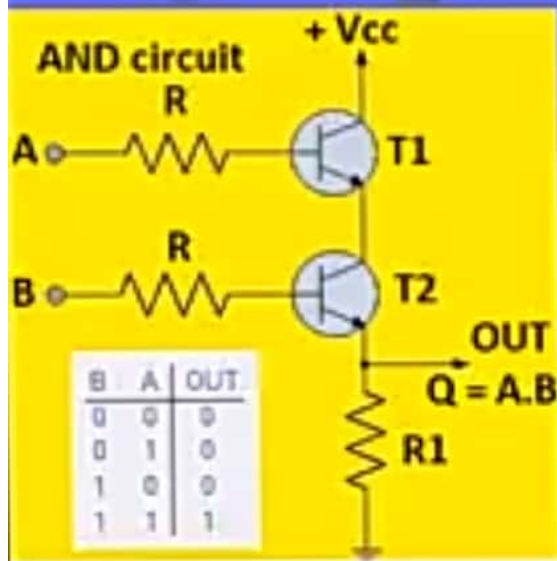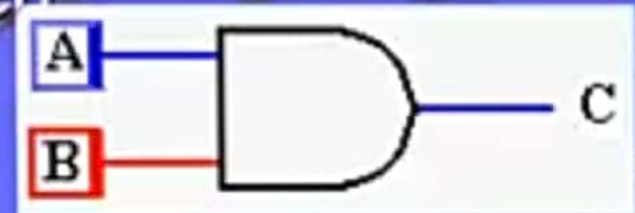

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1



Tuesday, March 9, 2021

Scanned with CamScanner

LOGIC GATES: OR


- Current flows if either switch is closed

- Logic notation $A + B = C$

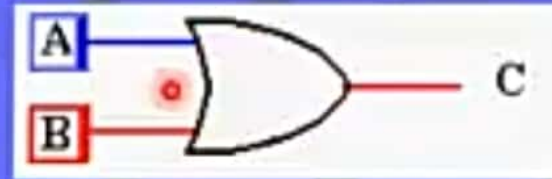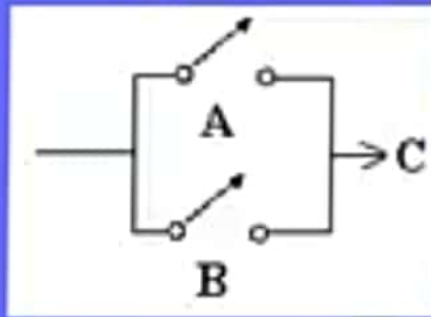

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

GATES: Inversion (NOT)

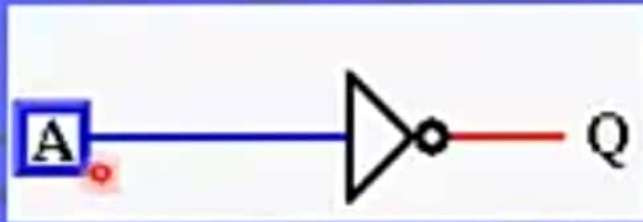


Logic: $Q = A'$

A	Q
0	1
1	0

Q is said to be the complement of A and is denoted as either \bar{A} or A'

GATES: Exclusive OR (XOR)

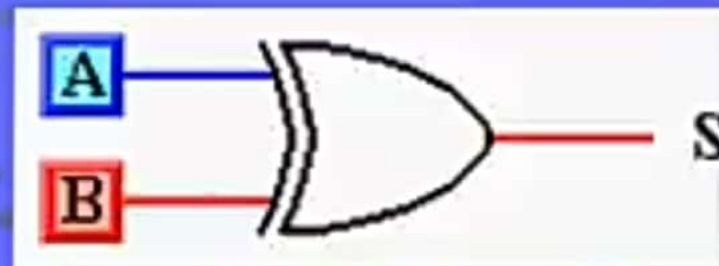

Either A or B, but not both, should be TRUE

This is sometimes called the **inequality detector**, because the result will be 0 when the inputs are the same and 1 when they are different.

A	B	S
0	0	0
1	0	1
0	1	1
1	1	0

Using Logic Gates

How can we realize a function say,
 $F = A.B' + A'B$ using such logic gates?

AND OR AND


NOT NOT

Requirement:


2 AND

2 NOT

1 OR

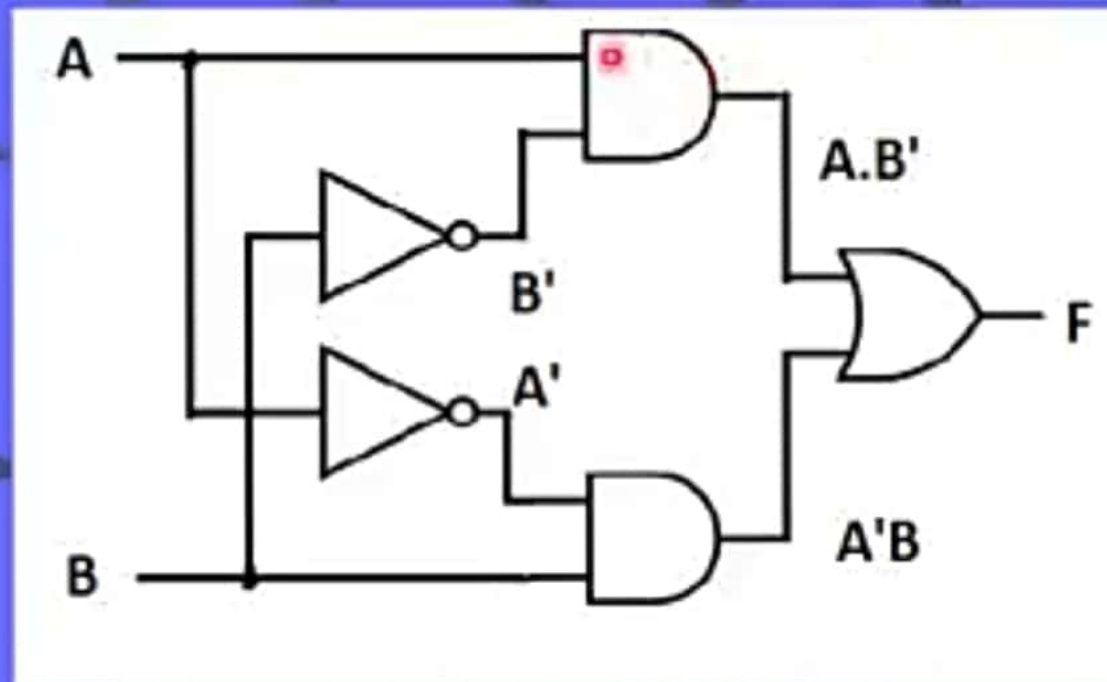

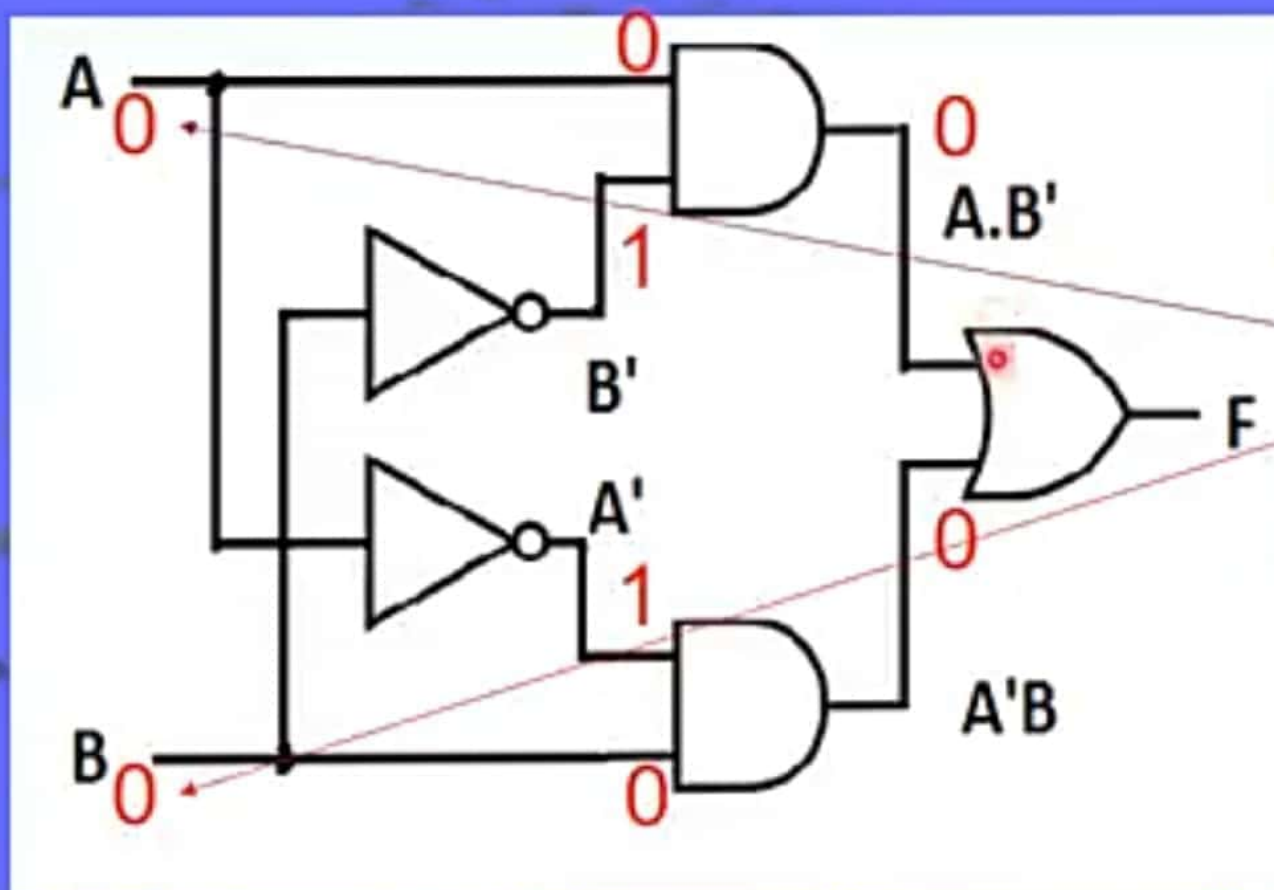Guess which truth table this circuit satisfies?




A	B	F
0	0	0
1	0	1
0	1	1
1	1	0


Fill the rest of the entries accordingly to find what it satisfies.

Tuesday, March 9, 2021

A quick peek into other logic gates

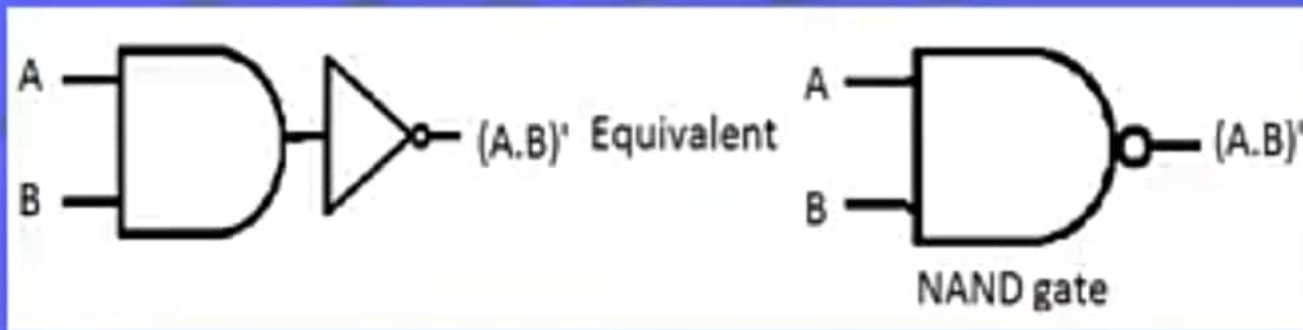

A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

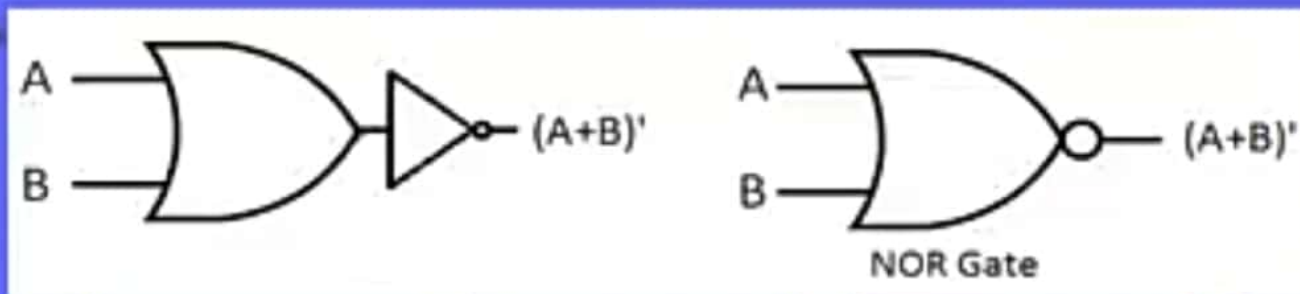

A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

Tuesday, March 9, 2021