

**CS221: Digital Design**

# **RTL Design: Serial Multiplier**

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Outline

- RTL Design
- Modulo 14 Counter Example
- Serial Multiplier Example
- **Can we automate this RTL design process?**
  - **Given C code/Parallel Code**

# **ASM Charts: An Complete Example**

## **Ref: Mano Book**

# ASM Charts: An Example


## Mod 14 counter:

- There is a 4 bit counter (A)
- E specify: less than 12 or less than 4
- EF=11 specify : value =12,
  - It time to reset after next counting
- E depends of  $A_2$ , F depends on  $A_2, A_3$

If  $A_2=1 \rightarrow E=1$ , else  $E=0$

$A_3A_2=1, \rightarrow F=1$ , counter reset

# AMS DP+CP : to be High Level

 


# ASM Charts: An Example

- A is a register;
- $A_i$  stands for  $i^{\text{th}}$  bit of the A register.

$$A = A_3A_2A_1A_0$$


- E and F are single-bit flip-flops.

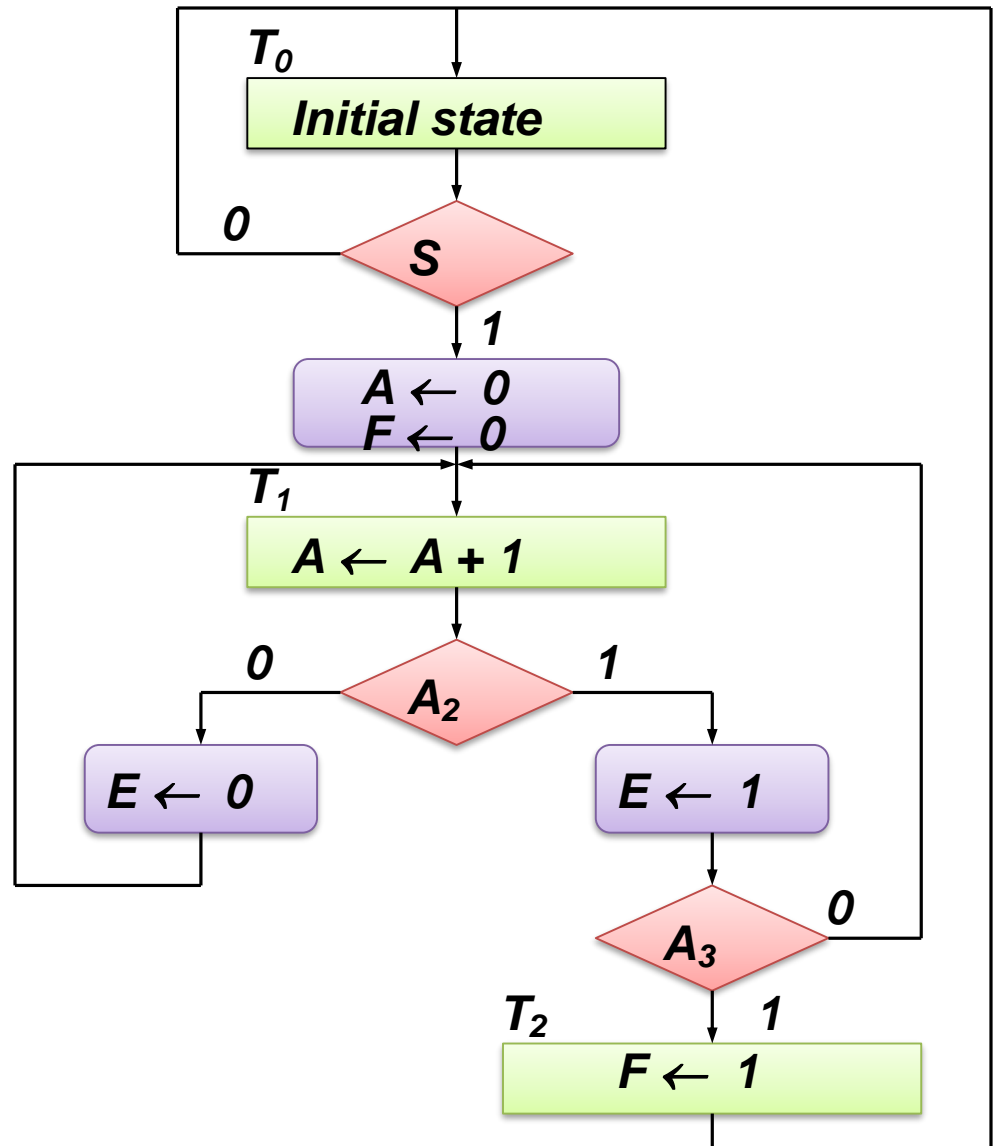

# Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
  - Operations in an **ASM block** occur at the same time in ***one clock cycle***
  - Decision boxes are dependent on the status of the ***previous clock cycle*** (that is, they do not depend on operations of current block)

# Timing in ASM Charts

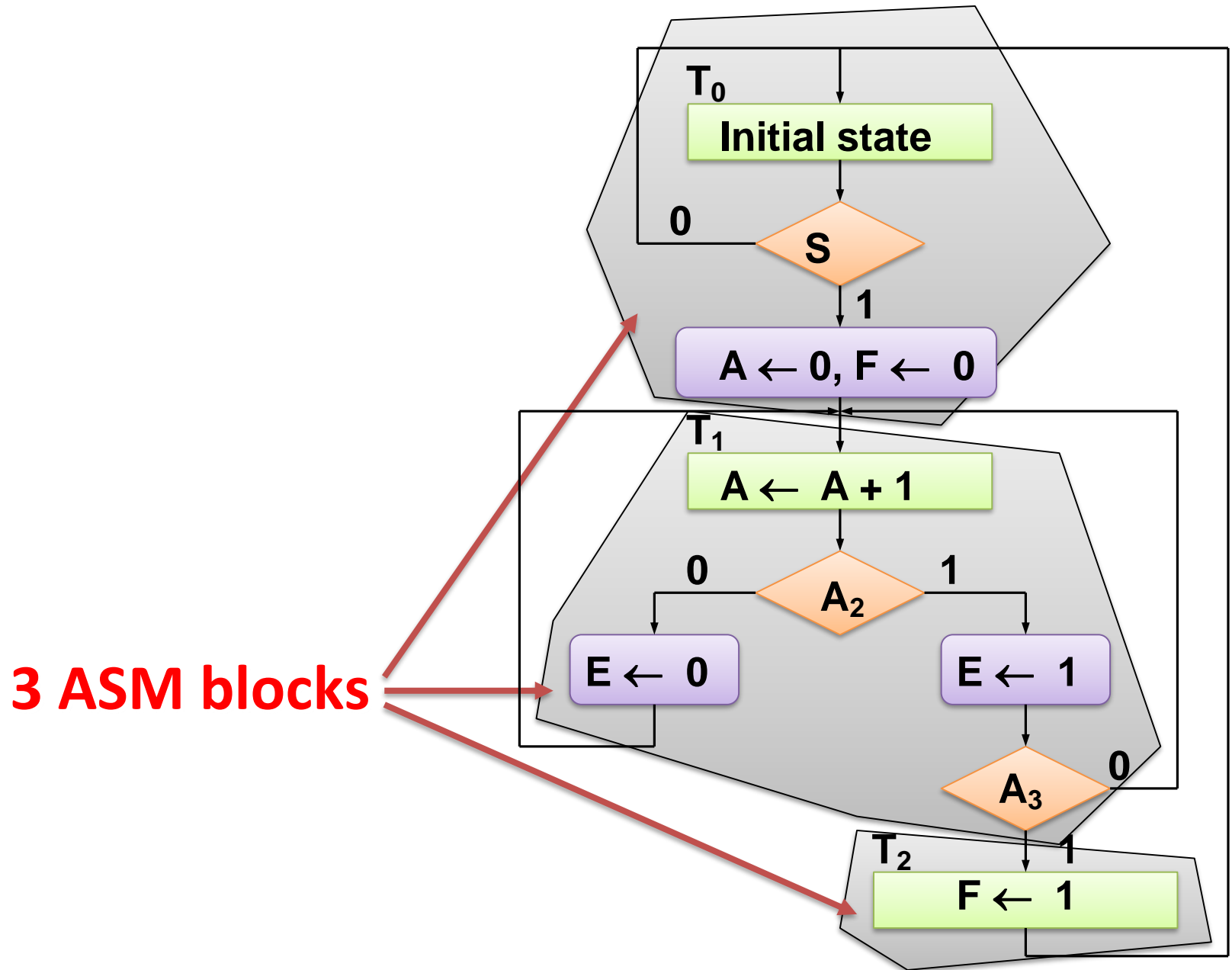




# Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
  - Operations in an ASM block occur at the same time in *one clock cycle*
  - Decision boxes are dependent on the status of the *previous clock cycle* (that is, they do not depend on operations of current block)

# Timing in ASM Charts

CTR	E, F	Conditions	State
0000	1,0	$A_2=0, A_3=0$	T1
0001	0,0	--	--
0010	0,0	---	--
0011	0,0	---	--
0100	0,0	$A_2=1, A_3=0$	--
0101	1,0	--	--
0110	1,0	--	--
0111	1,0	--	--
1000	1,0	$A_2=0, A_3=1$	--
1001	0,0	--	--
1010	0,0	--	--
1011	0,0	--	--
1100	0,0	$A_2=1, A_3=1$	--
1101	1,0		T2
1101	1,1		T0

 



# ASM Chart => Digital System

- ASM chart describes a digital system. From ASM chart, we may obtain:
  - Controller logic (via State Table/Diagram)
  - Architecture/Data Processor
- Design of controller is determined from the decision boxes and the required state transitions.
- Design requirements of data processor can be obtained from the operations specified with the state and conditional boxes.

# ASM Chart => Controller

- Procedure:
  - Step 1: Identify all states and assign suitable codes.
  - Step 2: Formulate state table using
    - State** from state boxes
    - Inputs** from decision boxes
    - Outputs** from operations of state/conditional boxes.
  - Step 3: Obtain state/output equations and draw circuit.

# ASM Chart => Controller

 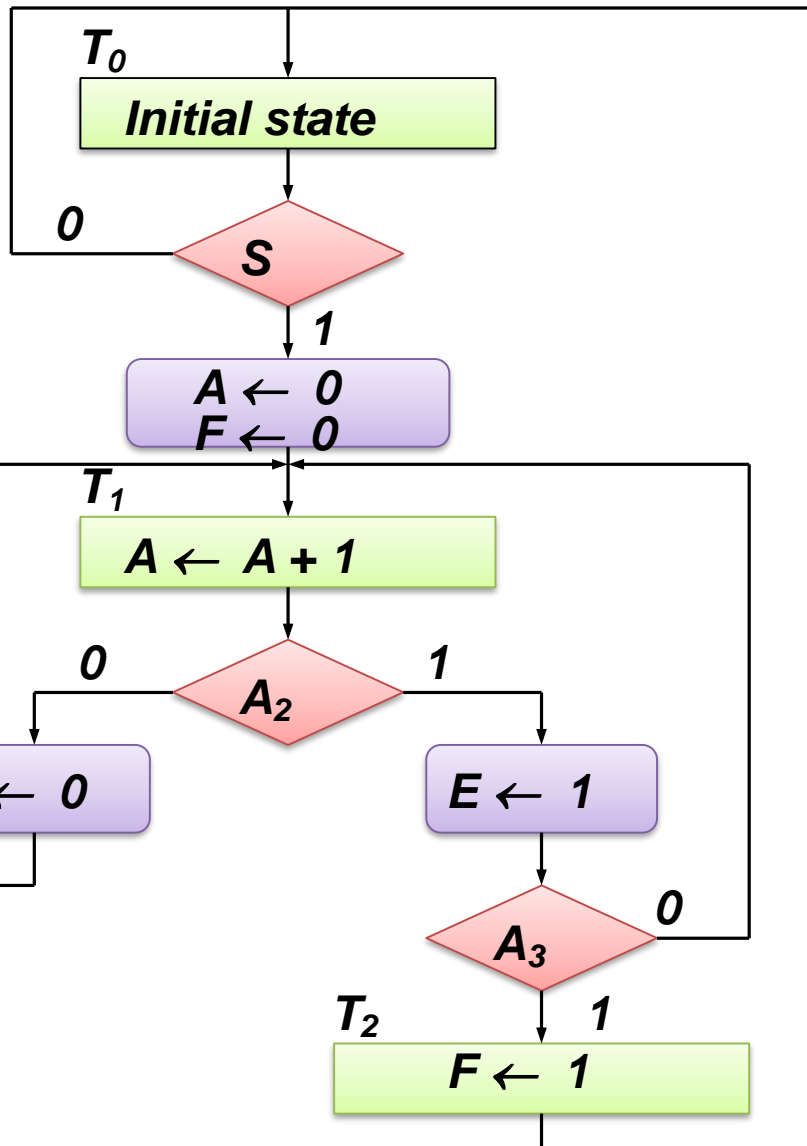

*Assign codes to states:*

$T_0 = 00$

$T_1 = 01$

$T_2 = 11$

Present state		inputs			Next state		outputs		
$G_1$	$G_0$	$S$	$A_2$	$A_3$	$G_1^+$	$G_0^+$	$T_0$	$T_1$	$T_2$
0	0	0	X	X	0	0	1	0	0
0	0	1	X	X	0	1	1	0	0
0	1	X	0	X	0	1	0	1	0
0	1	X	1	0	0	1	0	1	0
0	1	X	1	1	1	1	0	1	0
1	1	X	X	X	0	0	0	0	1

*Inputs from conditions in decision boxes.*

*Outputs = present state of controller.*

# ASM Chart => Architecture/Data Processor


- Architecture is more difficult to design than controller.
- Nevertheless, it can be deduced from the ASM chart. In particular, the operations from the ASM chart determine:
  - What registers to use
  - How they can be connected
  - What operations to support
  - How these operations are activated.
- Guidelines:
  - always use high-level units
  - simplest architecture possible.

# ASM Chart => Architecture/Data Processor

- Various operations are:
  - Counter incremented ( $A \leftarrow A + 1$ ) when state =  $T_1$ .
  - Counter cleared ( $A \leftarrow 0$ ) when state =  $T_0$  and  $S = 1$ .
  - E is set ( $E \leftarrow 1$ ) when state =  $T_1$  and  $A_2 = 1$ .
  - E is cleared ( $E \leftarrow 0$ ) when state =  $T_1$  and  $A_2 = 0$ .
  - F is set ( $F \leftarrow 0$ ) when state =  $T_2$ .
  - F is cleared ( $F \leftarrow 0$ ) when state =  $T_0$  and  $S = 1$ .
- Deduce:
  - One 4-bit register A (e.g.: 4-bit synchronous counter with clear/increment).
  - Two flip-flops needed for E and F (e.g.: JK/D flip-flops).
 
# ASM Chart => Architecture/Data Processor

$(A \leftarrow A + 1)$  when state =  $T_1$ .  
 $(A \leftarrow 0)$  when state =  $T_0$  and  $S = 1$ .  
 $(E \leftarrow 1)$  when state =  $T_1$  and  $A_2 = 1$ .





RTL/ASM example  
for  
8 bit Sequential Multiplier

Ref: Mano Book

# RTL: Multiplier Example

- Example:  $(101 \times 011)$  Base 2
- Note that the partial product summation for  $n$  digits, base 2 numbers requires adding up to  $n$  digits (with carries) in a column.
- Note also  $n \times m$  digit multiply generates up to an  $m + n$  digit result (same as decimal).

■ Partial products are:

$101 \times 0$ ,  $101 \times 1$ , and  $101 \times 1$

$$\begin{array}{r}
 \phantom{00}101 \\
 \times \phantom{00}011 \\
 \hline
 \phantom{00}101 \\
 101\phantom{00} \\
 000\phantom{00} \\
 \hline
 001111
 \end{array}$$

# Example (1 0 1) x (0 1 1) Again


- Reorganizing example to follow hardware algorithm:

		<b>1</b>	<b>0</b>	<b>1</b>				
	x	<b>0</b>	<b>1</b>	<b>1</b>				
→	0	0	0	0		Clear C    A		
→	+	1	0	1		Multiplier0 = 1 => Add B		
→	0	1	0	1		Addition		
→	0	0	1	0	1	Shift Right (Zero-fill C)		
→	+	1	0	1		Multiplier1 = 1 => Add B		
→	0	1	1	1	1	Addition		
→	0	0	1	1	1	1	Shift Right	
→	0	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	Multiplier2 = 0 => No Add, Shift Right

# Binary Multiplication

- Polynomial Multiplication
  - You can think Binary number A, B as polynomials
  - $A(X) = A_{n-1} \cdot 2^{n-1} + \dots + A_2 \cdot 2^2 + A_1 \cdot 2^1 + A_0 \cdot 2^0$
  - Multiply polynomial to get another one
  - Time complexity:  $O(n^2)$  Basic serial Algorithm,  $O(n^{1.5})$  for divide conquer approach,  $O(n \lg n)$  using FFT
- Booth Algorithm reduce number Partial addition
  - 99 Represent using 100-1, 95 is 100-5
  - 111 represent as 1000-1 in binary: possibly reduce


# Sequential Multiplier

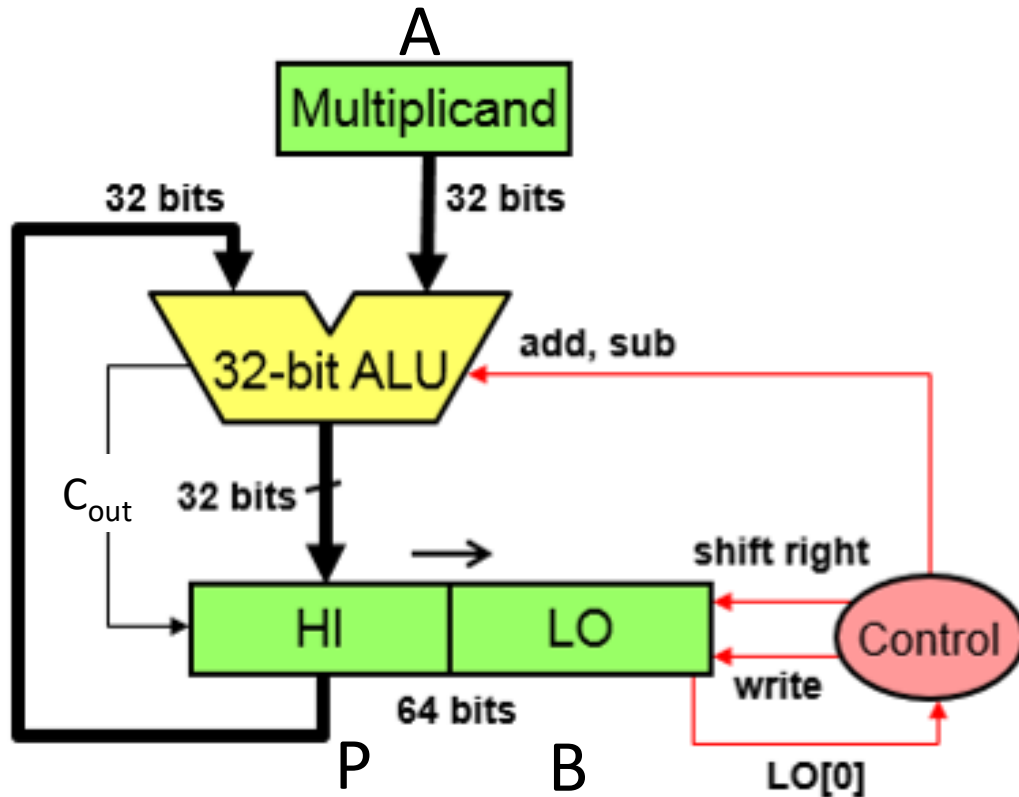

## Control Algorithm:

1.  $P \leftarrow 0$ ,  $A \leftarrow$  multiplicand,  $B \leftarrow$  multiplier **//Initialization**
2. If LSB of  $B == 1$  then add  $A$  to  $P$  else add 0
3. Shift  $[P][B]$  right 1
4. Repeat steps 2 and 3  $n-1$  times.
5.  $[P][B]$  has product.

# Multiplier Example: Block Diagram

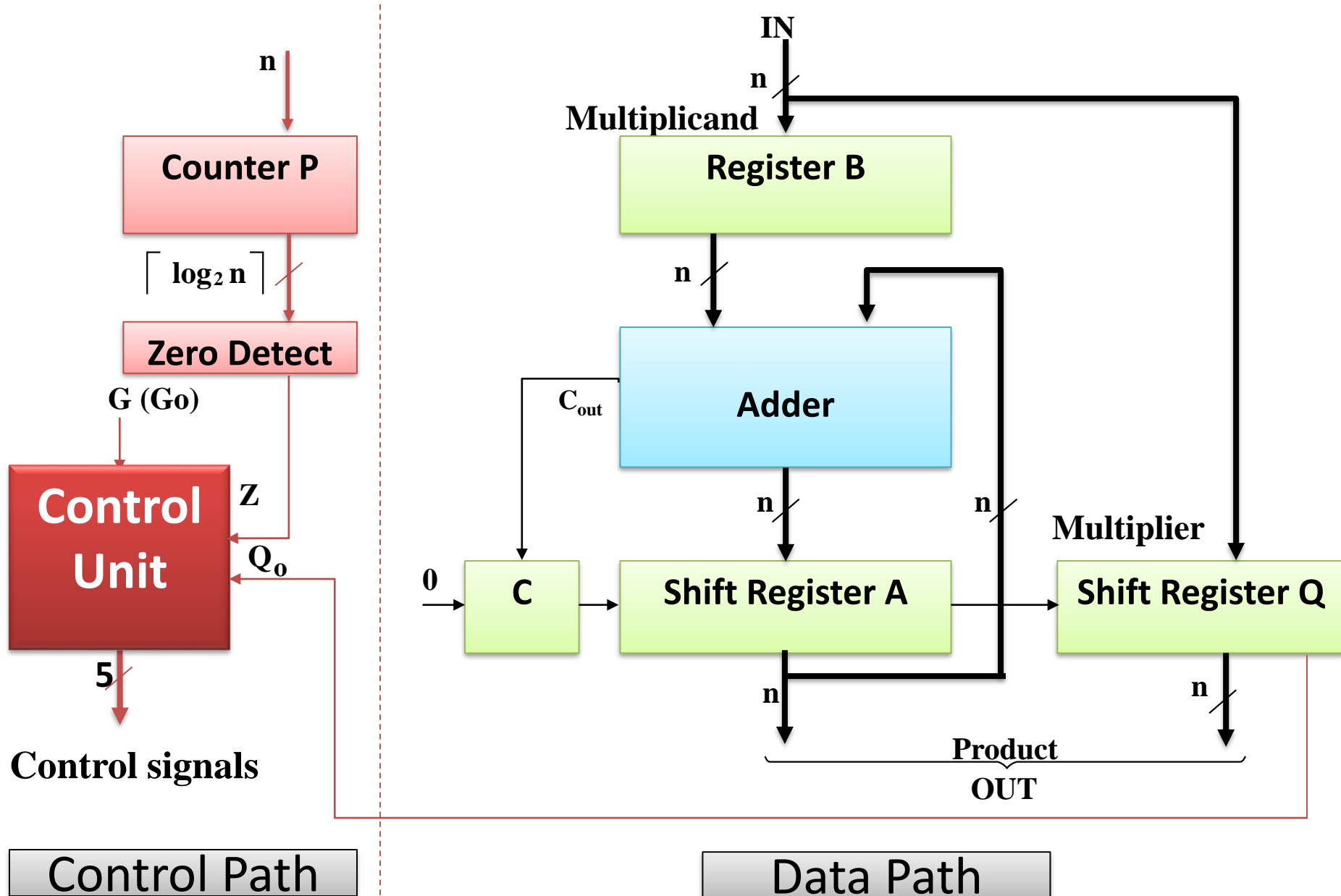

## Multiplier Example: Operation


- Step1: The multiplicand (top operand) is loaded into register B.
- Step2: The multiplier (bottom operand) is loaded into register Q.
- Step3: Register C || A is initialized to 0 when G becomes 1.
- Step4: The partial products are summed iteratively in register C || A || Q.

## Multiplier Example: Operation

- Step5: Each multiplier bit, beginning with the LSB, is processed (if bit is 1, use adder to add B to partial product; if bit is 0, do nothing)
- Step6:  $C || A || Q$  is shifted right using the shift register
  - Partial product bits fill vacant locations in Q as multiplier is shifted out
  - If overflow during addition, the outgoing carry is recovered from C during the right shift
- Step 7: Steps 5 and 6 are repeated until Counter P = 0 as detected by Zero detect.
  - Counter P is initialized in step 4 to  $n - 1$ ,  $n$  = number of bits in multiplier



# Multiplier Example: ASM Chart

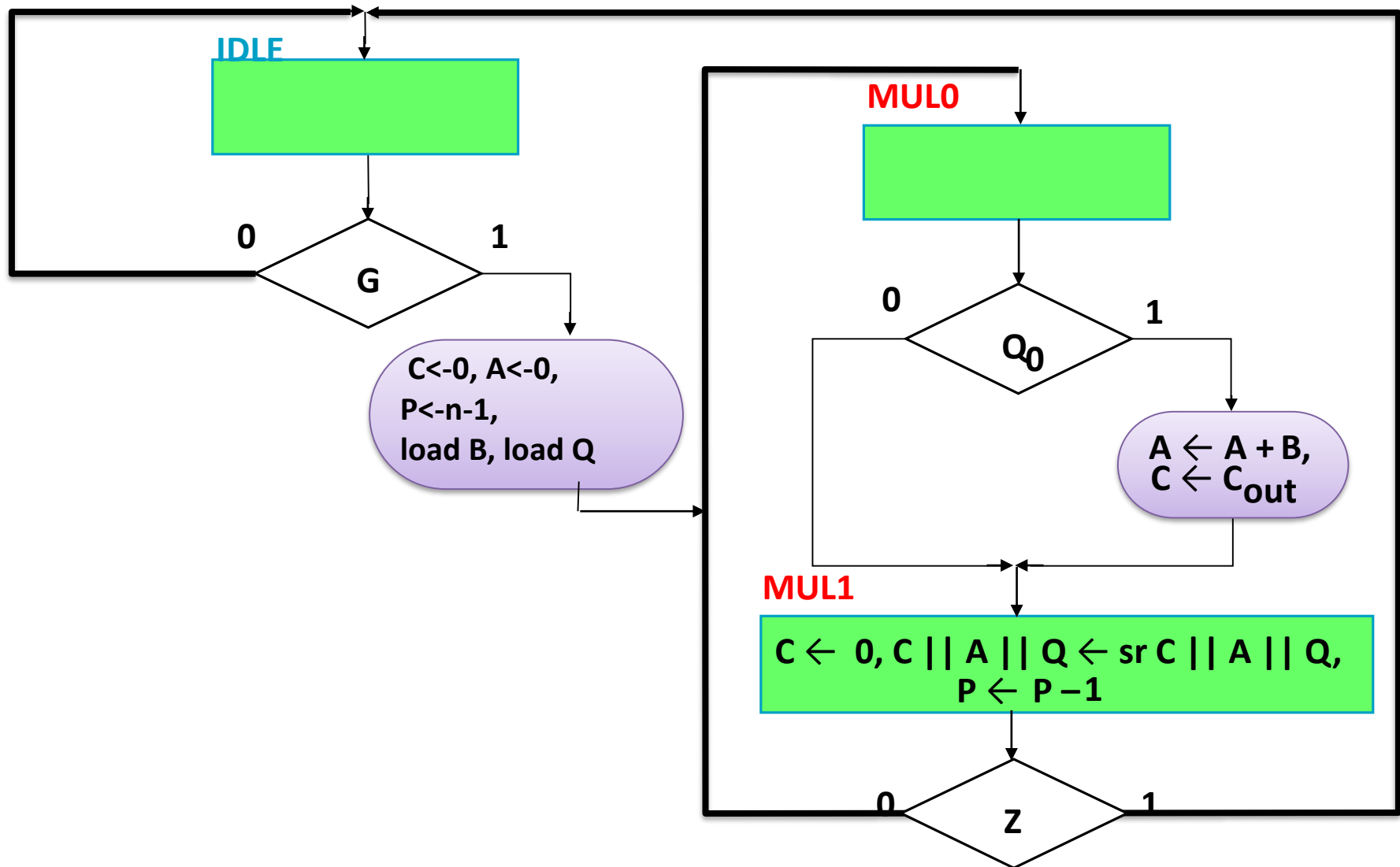

# Multiplier Example: ASM Chart (continued)

- Combined Mealy - Moore output model
- **IDLE - state**
  - Input G is used as the condition for starting the multiplication, and
  - *C, A, and P are initialized and Load B, Load Q*
- **MUL0 - state**
  - Conditional addition is performed based on the value of  $Q_0$ .
- **MUL1 - state**
  - Right shift is performed to capture the partial product and position the next bit of the multiplier in  $Q_0$
  - the terminal count of 0 for down counter P is used to sense completion or continuation of the multiply.

# Multiplier Example: Control Signal Table

Module	Micro Operations	Control Signal Name	Control Expression
Reg A	$A \leftarrow 0$ $A \leftarrow A + B$ $C    A    Q \leftarrow sr(C    A    Q)$	Load_regs Add_regs Shift CAQ	IDLE.G MUL0.Q <sub>0</sub> MUL1
Reg B	$B \leftarrow IN$	Load_regs	LOAD_B
FF C	$C \leftarrow 0$ $C \leftarrow Cout$	Clear C Load	IDLE.G+MUL1 --
Reg Q	$Q \leftarrow IN$ $C    A    Q \leftarrow sr(C    A    Q)$	Load_regs ShiftCAQ	LOAD_Q
Ctr P	$P \leftarrow N-1$ $P \leftarrow P-1$	Load_regs Decr_P	MUL1

# Multiplier Example: Control Circuit

PS	PS	Inputs			NS	Ready	Load Regs	Decr_ P	Add_ regs	Shift_ CAQ
		G	Q0	Z						
Idle	00	0	x	X	00	1				
Idle	00	1	X	x	01	1	1			
Mul0	01	x	0	X	10			1		
Mul0	01	x	1	X	10				1	
Mul1	10	x	x	0	01			1		1
Mul1	10	x	x	1	00			1		1

Ready=Idle


Load\_Regs=Idle.G

Decr\_P=Mul0

Add\_regs=Mul0.Q<sub>0</sub>

ShiftCAQ=Mul1

# Multiplier Example: Control Circuit

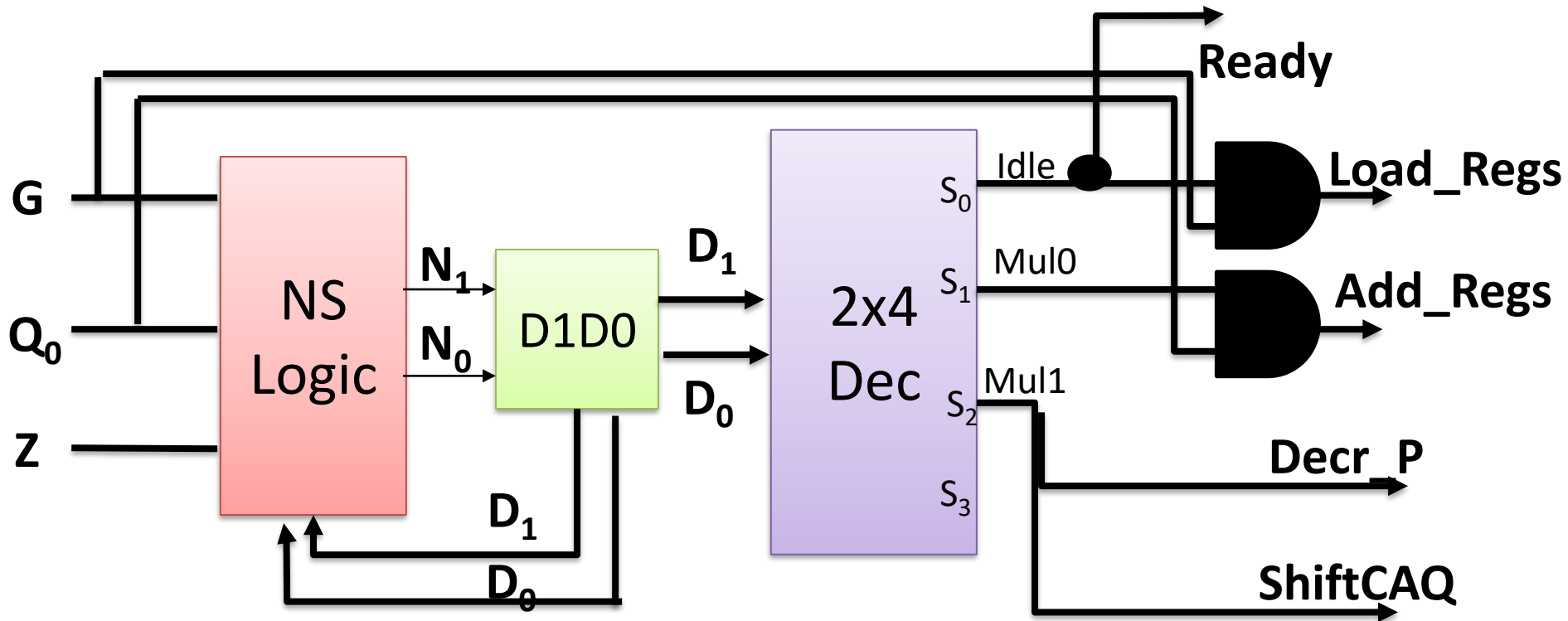

$$N1 = D_1' D_0$$

$$N0 = D_1' D_0' G + D_1 D_0' Z'$$

$$\text{Ready} = \text{Idle}$$

$$\text{Load\_Regs} = \text{Idle} \cdot G$$

$$\text{Decr\_P} = \text{Mul1}$$

$$\text{Add\_regs} = \text{Mul0} \cdot Q_0$$

$$\text{ShiftCAQ} = \text{Mul1}$$