

CS221: Digital Design

Register and Memory

A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

Outline


- Register
 - Parallel Load, Parallel out : (PIPO)
 - Serial Load, Wrap around load, Serial out (SISO)
 - PISO, SIPO Register
- Multifunction Register : How to design?
- Memory Design using array of PIPO registers
 - RAM: Random Access Memory

Rotate Register

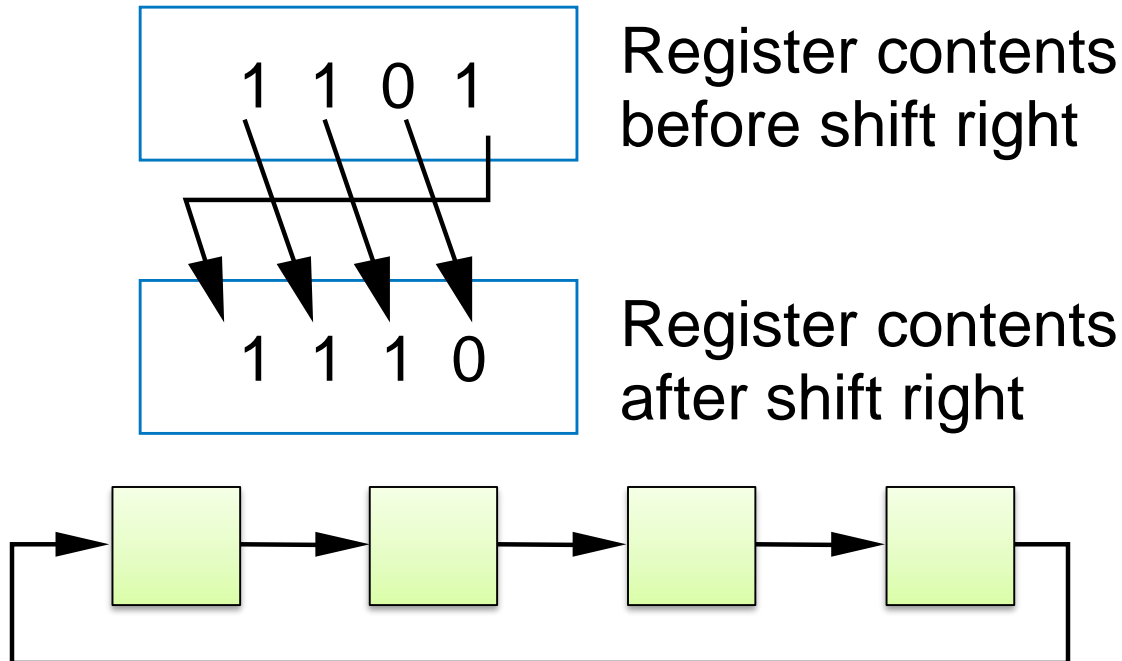- Rotate right: Like shift right, but leftmost bit comes from rightmost bit




Serial Transfer

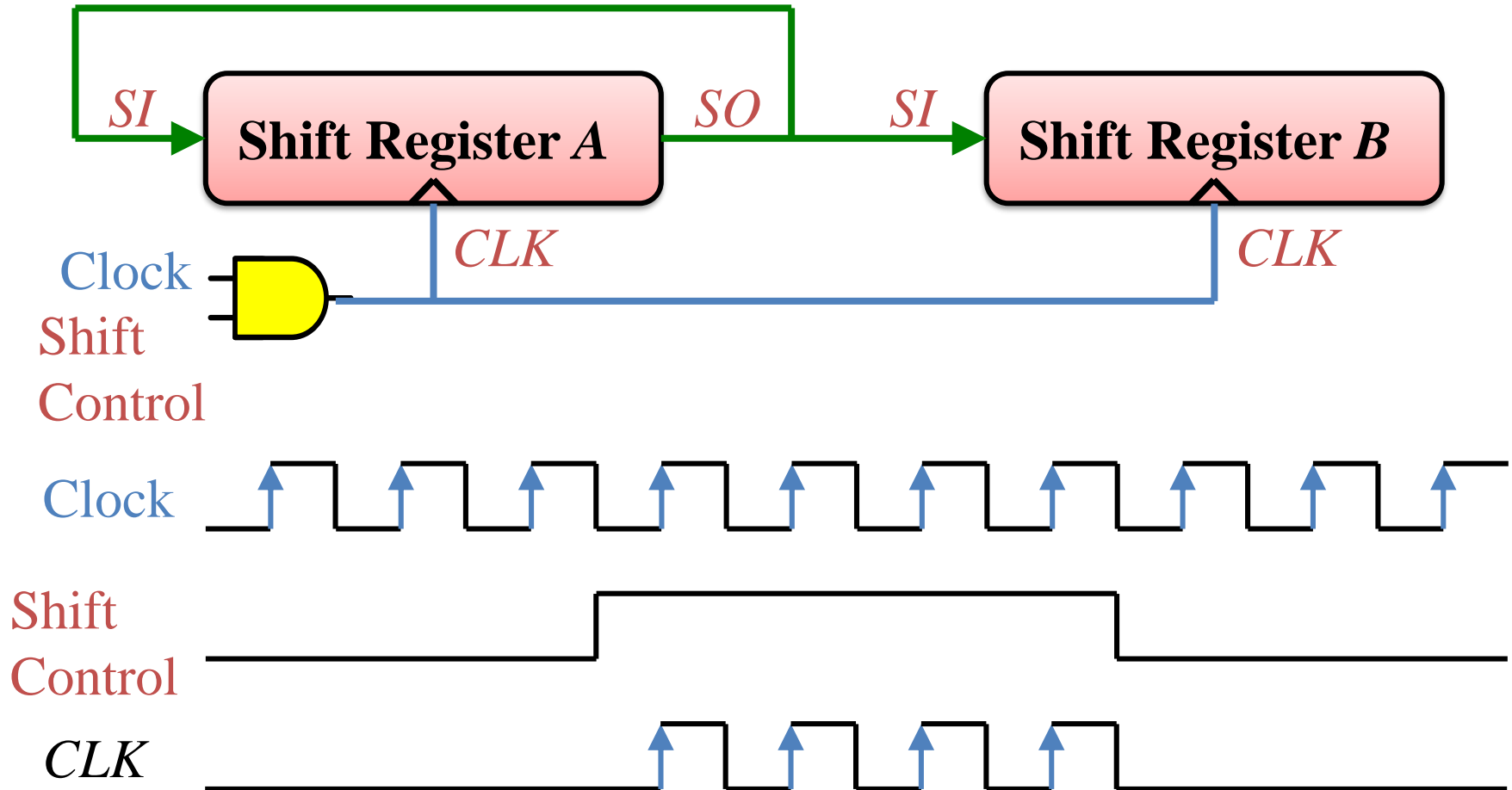


N-Bit RCA: Series of FA Cells

- To add two n-bit numbers

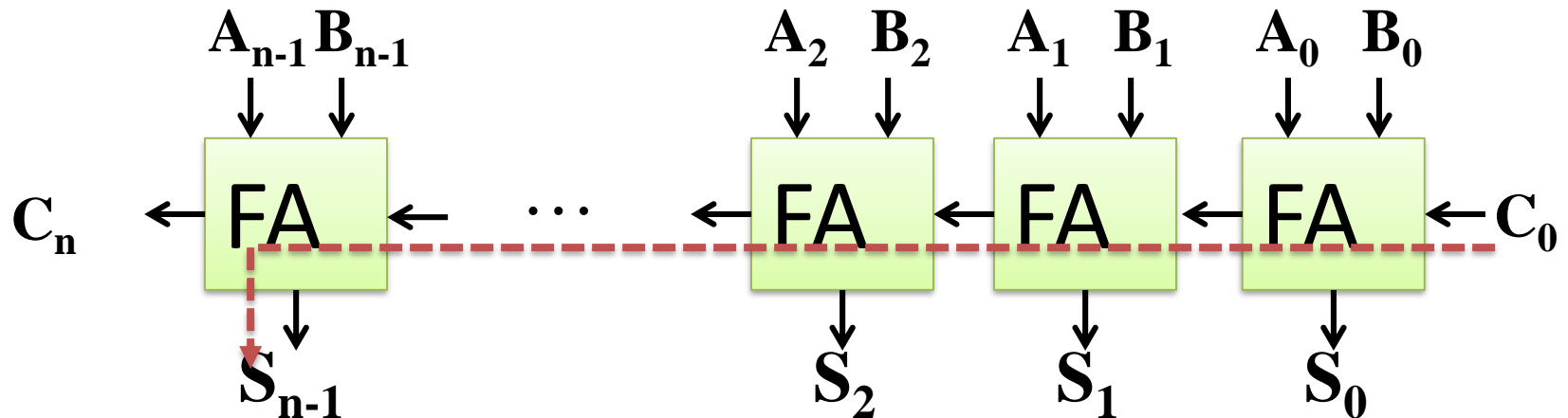


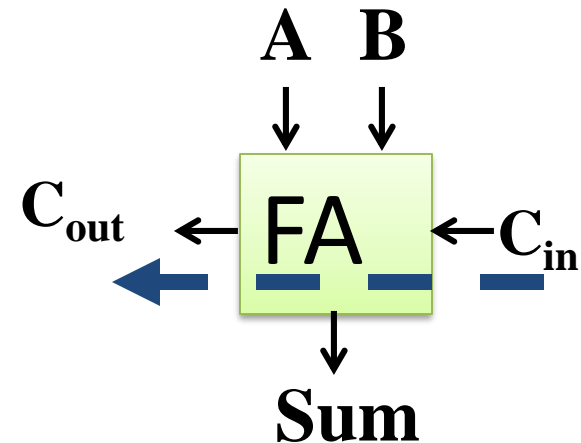- Adder delay = $T_c * n$
- $T_c = (C_{in} \text{ to } C_{out} \text{ delay}) \text{ of a FA}$



N-Bit Ripple-Carry Adder


- To add two n-bit numbers

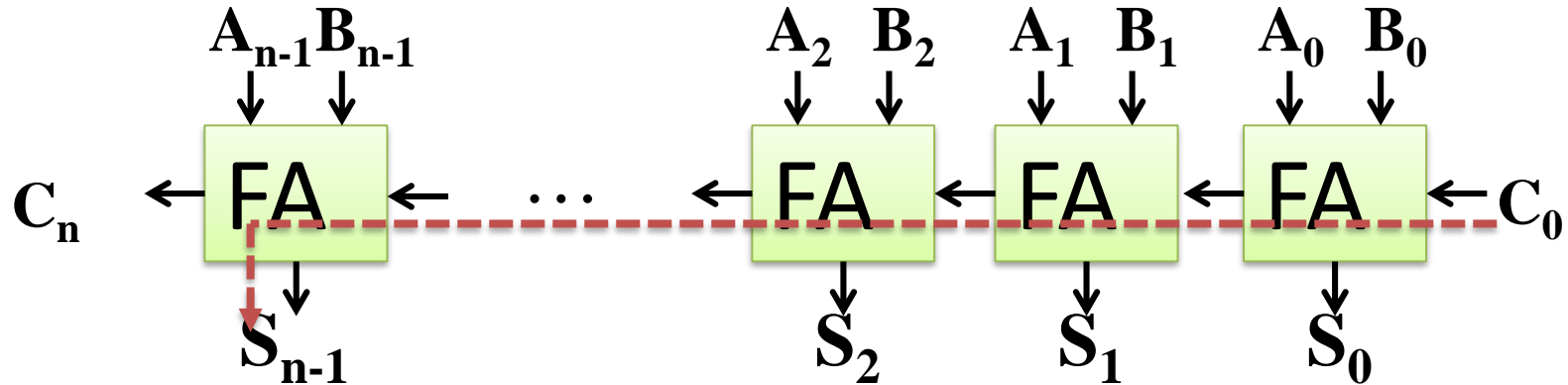

- Any point of time: only one FA is active

Do we require N Full Adder?


Serial Addition

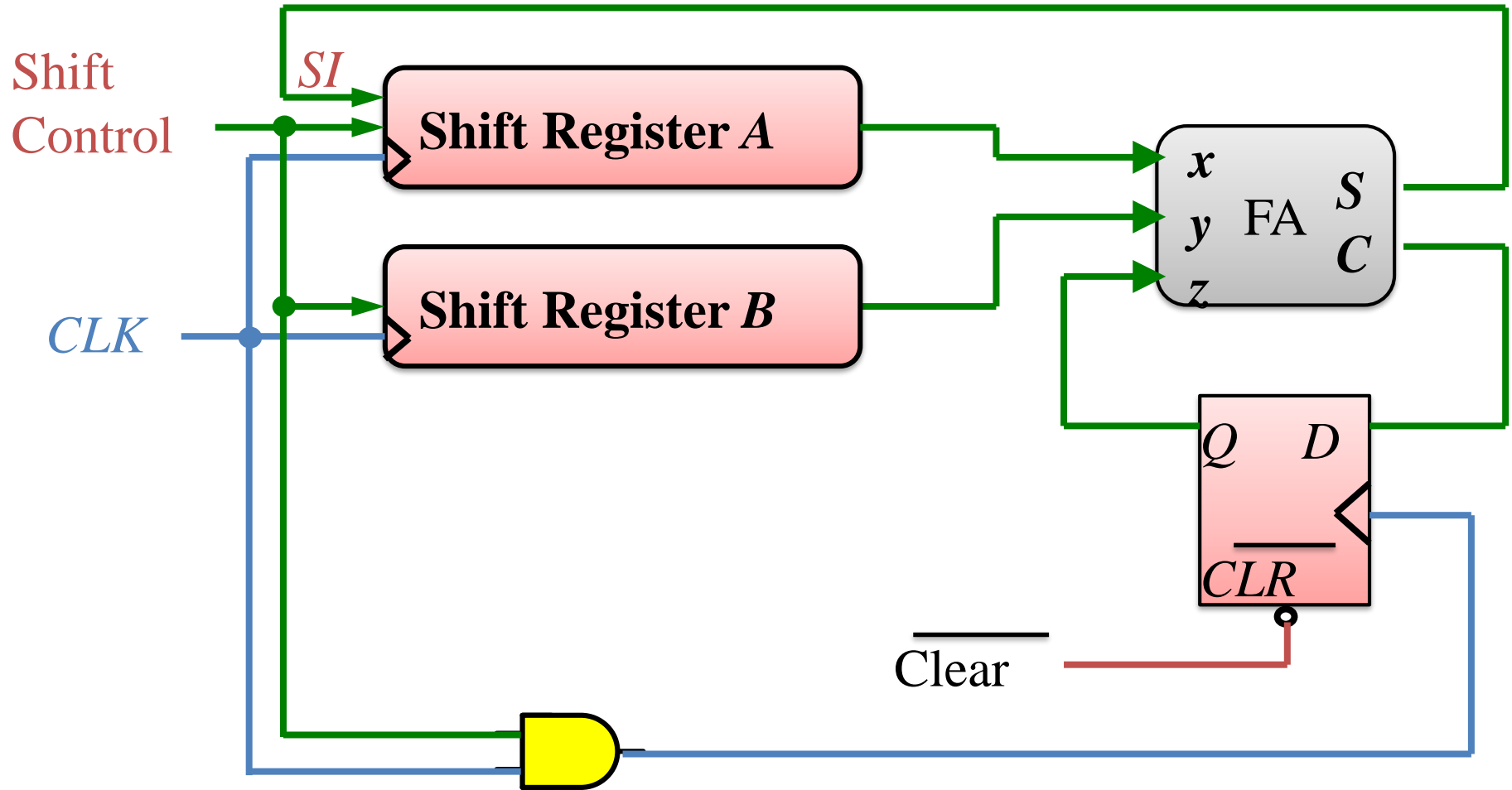


Universal Shift Register

- Parallel-in Parallel-out (PIPO)
- Serial-in Serial-out (SISO)
- Serial-in Parallel-out (SIPO)
- Parallel-in Serial-out (PISO)

Universal Shift Register

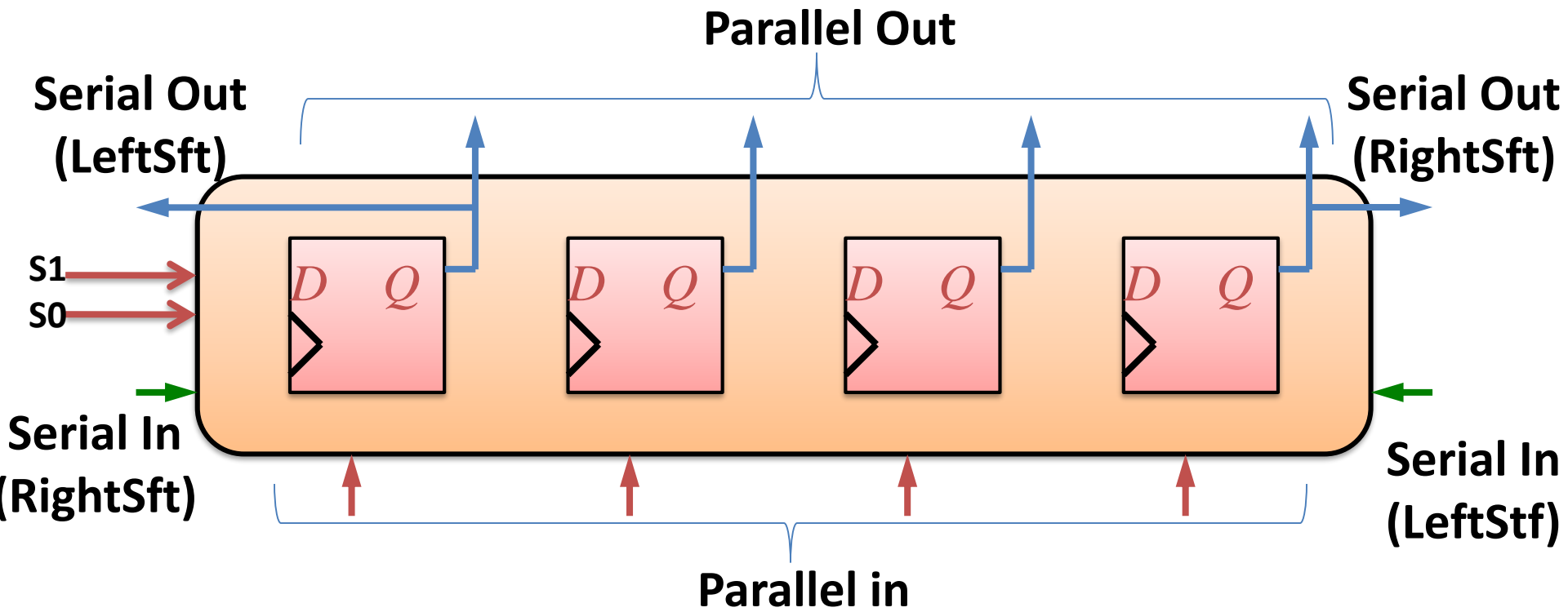


Universal Shift Register

 


Operation Table for USR

S1	S0	Register Operation
0	0	No Change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load


Universal Shift Register: $S_1S_0=00$

 


Universal Shift Register: $S_1S_0=01$

 

Universal Shift Register: $S_1S_0=10$

 

Universal Shift Register: $S_1S_0=11$

 


Design of Multifunction Register

- M function N bit Register
 - Last example : 4 functions and 4 bits register
- N number of **$\text{ceil}[\text{Log}_2 M] \times 2^{\text{ceil}[\text{Log}_2 M]}$** size Multiplexor (Mux)
 - For 4 function 2x4 Mux (**4 to 1 Mux**), 2 select line
 - For 5 function 3x8 Mux (**8 to 1 Mux**), 3 select line
- Extra functions of Mux need to shunted (ignored) to do no work
 - For 5 function need a 3x8 Mux, we need to shunt $8-5=3$ lines shunted (ignored) to do no work


Memory

- Universal register : One register with many functionality
- Many registers clubbed with less functionality
 - No Shift
- Parallel load (In) or Parallel Out to a specific register
- Multiplexors used for selection of registers


Register(PIPO)

 


Register(PIPO)

 

Tri-state Buffer

 

Register with Read and write control

 


If $S = 0$, TS1 and TS2 will be open


$S=1$, $RW=1$, Write to Register 4 bit of data

$S=1$, $RW=0$, Read data from Register


Register with Read and write control

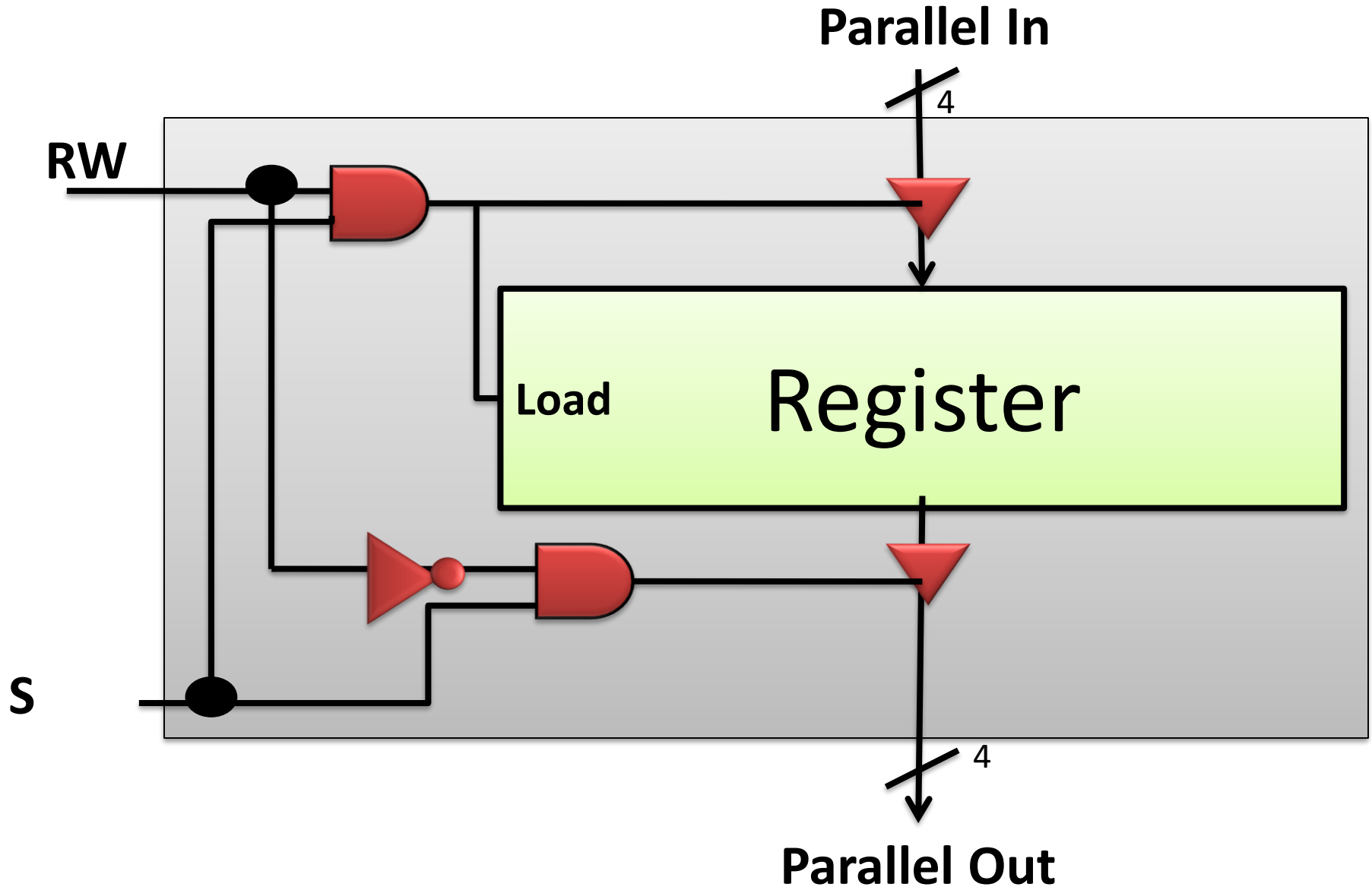


Many Register with RW control

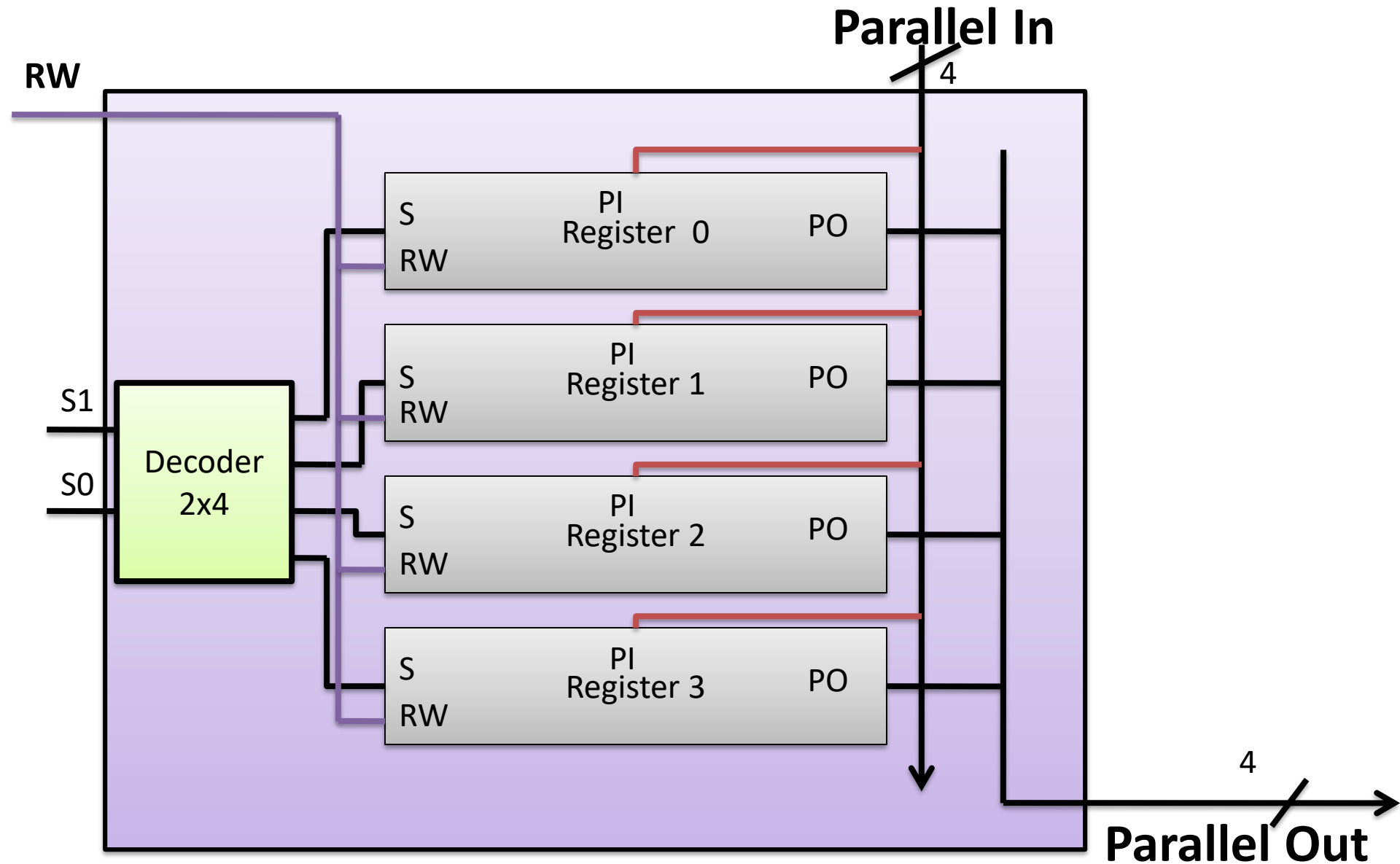


Memory with MAR and MDR

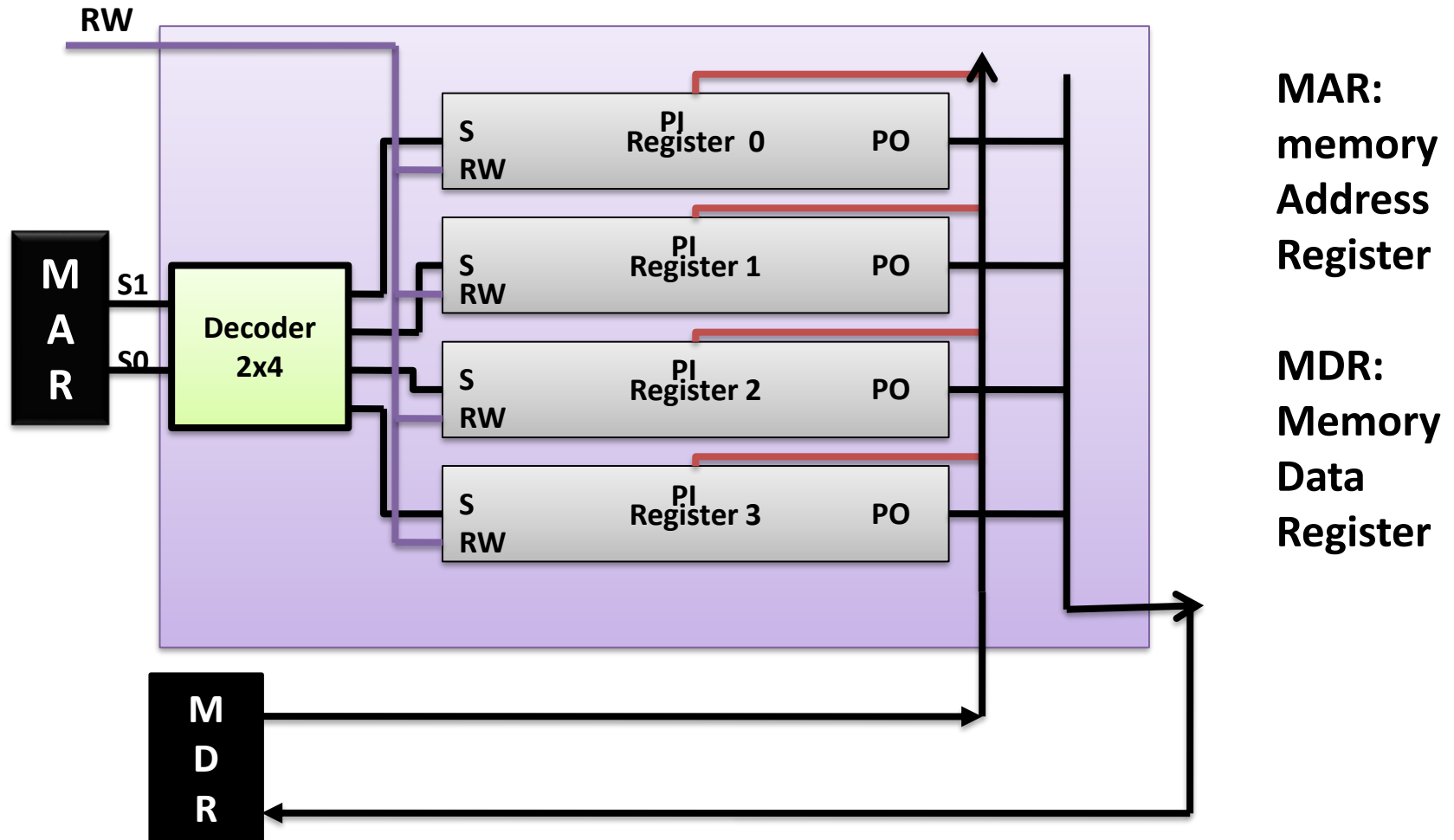

 Many Register with RW control: 4 four bit word Memory



General Memory

 

Memory : Locations & Word size

- ADDRESS decides the number of memory location
- MDR size : decides the WordSize
- Number of registers : $2 + \text{NumLocations}$
 - $2 + 2^{\text{AddressSize}}$
 - 1 for MBR, 1 for MAR
- $\text{NumFF} = \text{MARsize} + \text{MDRsize} + \text{NumLoc} * \text{MDRSize}$

Designing 1KB Mem using two 1KN Mem

