

CS221: Digital Design

Finite State Machine (Examples)

A. Sahu


Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

FSM Example 6:
Counter that repeat 0,1,1,1,


FSM Example: 0,1,1,1,repeat

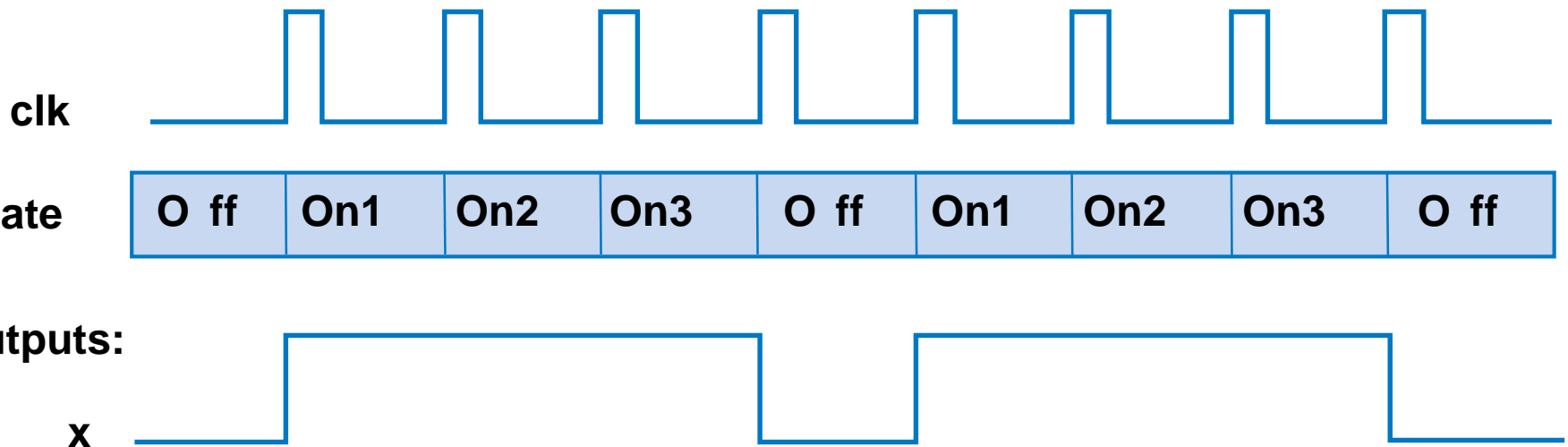- Want 0, 1, 1, 1, 0, 1, 1, 1, ...
 - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state




FSM Example: 0,1,1,1,repeat

 - Want 0, 1, 1, 1, 0, 1, 1, 1, ...
 - Each value for one clock cycle
- Can describe as FSM: Four states, Transition on rising clock edge to next state



FSM Example: 0,1,1,1,repeat

 - Can describe as FSM: Four states, Transition on rising clock edge to next state



PS	NS	X
00	01	0
01	10	1
10	11	1
11	00	1


Require two FF to store states

Controller of FSM Example:

0,1,1,1,repeat

Input		Output		
CLK	PS $P_1 P_0$	NS $N_1 N_0$	X	
RE 1	0 0	0 1	0	
RE 1	0 1	1 0	1	
RE 1	1 0	1 1	1	
RE 1	1 1	0 0	1	

D-FF used to store the Present state

 

$$X = P_1 + P_0$$

$$N_1 = P_0 \text{ xor } P_1$$

$$N_0 = P_0'$$


Rising Edge: Clock implicit

FSM Example 7: Three-Cycles High Laser Timer


Extend FSM to Three-Cycles High Laser Timer

- Four states: Wait in “Off” state while b is 0 (b')
- When $b=1$ (& rising clock edge), transition to On1
 - Sets $X=1$
 - On next two clock edges, transition to On2, then On3, which also set $x=1$
- So $x=1$ for three cycles after button pressed

 Extend FSM to Three-Cycles High Laser Timer



 
Extend FSM to Three-Cycles High Laser Timer



FSM Simplification: Rising Clock Edges Implicit

- Showing rising clock on every transition: cluttered
- Make implicit -- assume every edge has rising clock
- What if we wanted a transition *without* a rising edge
 - **Asynchronous FSMs -- less common, and advanced topic**
 - We consider *synchronous* FSMs
 - ***All* transition on rising edge**

 
FSM Simplification: Rising Clock Edges Implicit



Value of $b=1$: 0111..repeat, **Is this FSM is complete?**

FSM Simplification: Rising Clock Edges Implicit


Inputs: b ; Outputs: x

 


Value of $b=1$: 0111..repeat, **Is this FSM is complete?**

FSM Simplification: Rising Clock Edges Implicit

Inputs: b ; Outputs: x

 

 
FSM Implementation : Three-Cycles High Laser Timer



PS	b	NS	x
00	0	00	0
00	1	01	0
01	x	10	1
10	x	11	1
11	x	00	1

FSM Implementation : Three-Cycles High Laser Timer

PS	b	NS	X
00	0	00	0
00	1	01	0
01	x	10	1
10	x	11	1
11	x	00	1

 

**Once we specify FSM for a
problem/system**


==>

Implementation is not difficult

FSM Example 8: Parity Encoder

FSM Example 8: Parity Encoder

 - Input: 1 or 0 // entering as stream
- Output: output a 1 when total number of 1 is even





T- FF :
designed using
D-FF

FSM Example 9: Button Press Synchronizer

  
Example 9 : Button Press Synchronizer

- English Language Specification
- All most all the keyboards use this method
- We want simple sequential circuit
 - Converts button press to single cycle duration
 - Regardless of length of time that button actually pressed



FSM Example 9 : Button Press Synchronizer

FSM inputs: bi ; FSM outputs: bo

 

I am Off
When $B=0$

I am On in First
CLK and
When $B=1$


I am Off
Even if $B=1$

Step 1: Design FSM

FSM Example 10: Sequence generator


FSM Example 10: Sequence generator

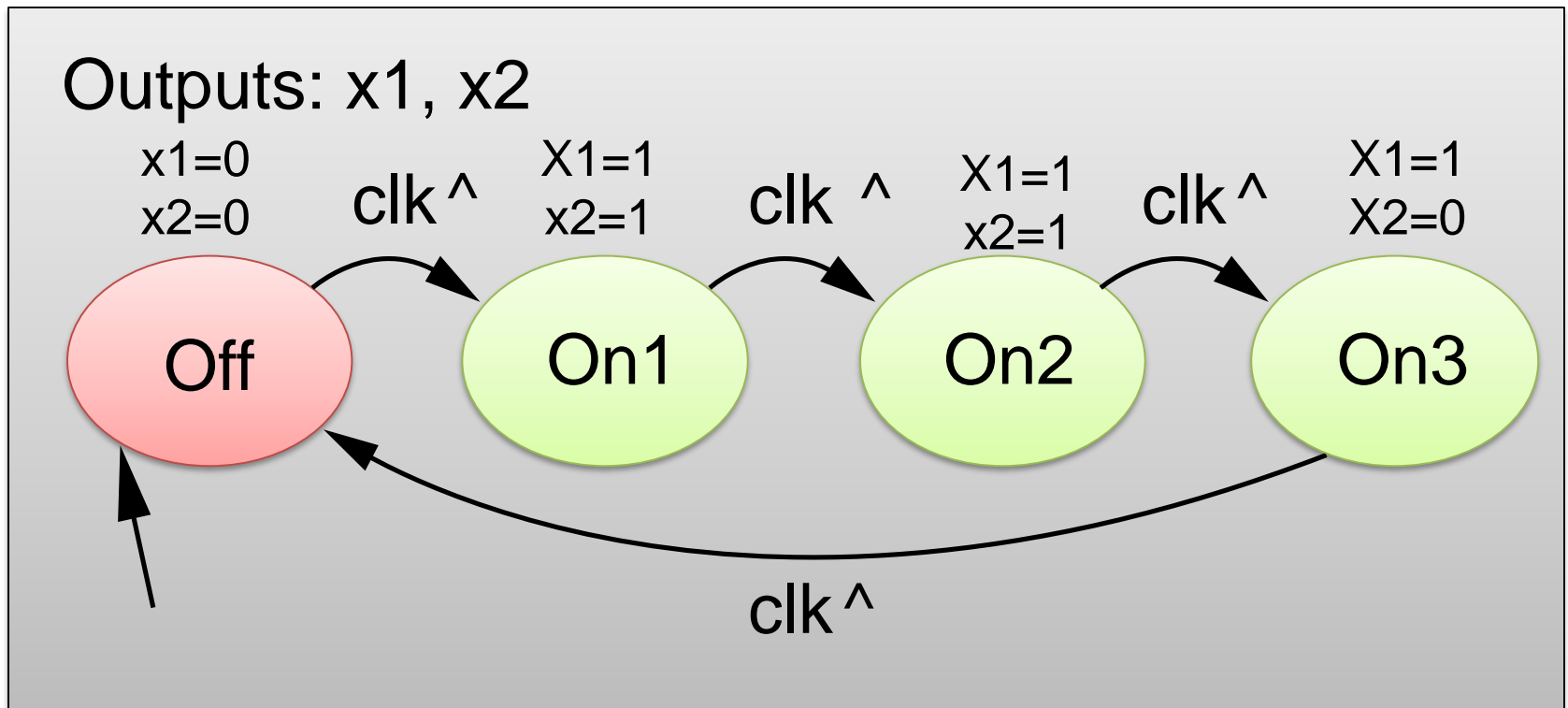- Generate two output sequence
 - $X1 = 0111\dots$ repeat
 - $X2 = 0110\dots$ repeat




FSM Example 10-E1: Sequence generator

 - Generate 4 bit integer output sequence
 - $X = 0, A, 7, 5 \dots$ repeat
 -





FSM Example 10-E2: Sequence generator

 - Generate 8 bit integer output sequence
 - $X = 72, 53, 11, 192, \dots$ repeat
 -



FSM Example 10-E2: Sequence generator

  - Generate 8 bit integer output sequence
 - $X = 72, 53, 11, 192, \dots$ repeat



A,B,C,D values can be stored in 4 registers
(With Mux it acts as memory)

FSM Output logic may be simpler than Register and Mux

Simpler to Implement
Output logic: Eight 2 input binary function