

# Combinational Logic Design



Dr. Chandan Karfa  
CSE IIT Guwahati

- Adder

# Half Adder

**Table 4.3**  
*Half Adder*

$x$	$y$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

  

## Full adder

- For example, addition of the binary numbers 1011 and 0011




$$\begin{array}{r} 0\ 1\ 1\ \text{carry-in} \\ 1\ 0\ 1\ 1\ \text{augend} \\ 0\ 0\ 1\ 1\ \text{addend} \\ \hline 1\ 1\ 1\ 0\ \text{sum} \end{array}$$

- The carry-out produced in the addition of the  $i$ th significant digits must be incorporated, as a carry-in, in the addition process for the  $(i + 1)$ th significant digit.


# Full Adder

**Table 4.4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  
 


(a)  $S = x'y'z + x'yz' + xy'z' + xyz$

 

(b)  $C = xy + xz + yz$

# Full Adder – area optimized design

 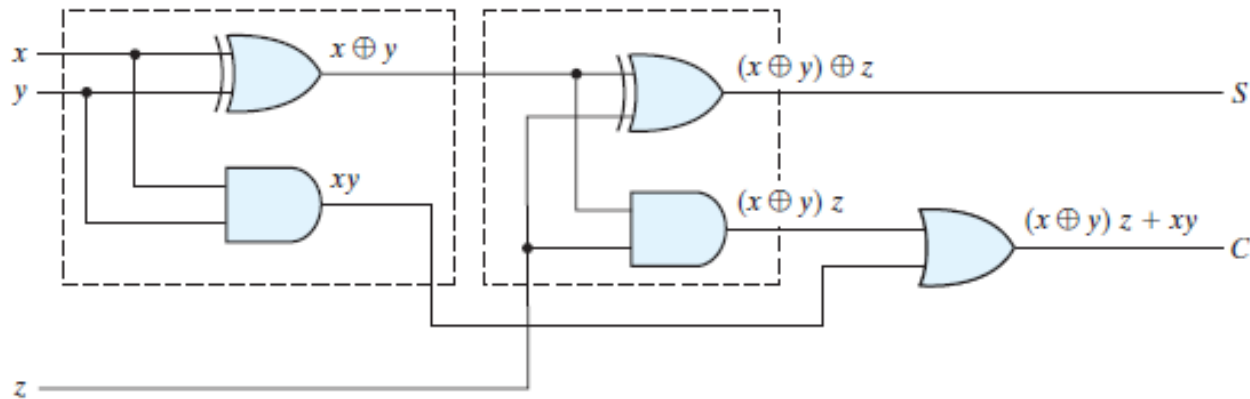

(b)  $C = xy + xz + yz$

**Table 4.4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$= xy'z' + x'yz' + xyz + x'y'z$$


$$= z'(xy' + x'y) + z(xy + x'y')$$

$$= z'(xy' + x'y) + z(xy' + x'y)'$$

$$S = z \oplus (x \oplus y)$$

$$C = z(xy' + x'y) + xy = xy'z + x'yz + xy$$


# Four bit binary adder

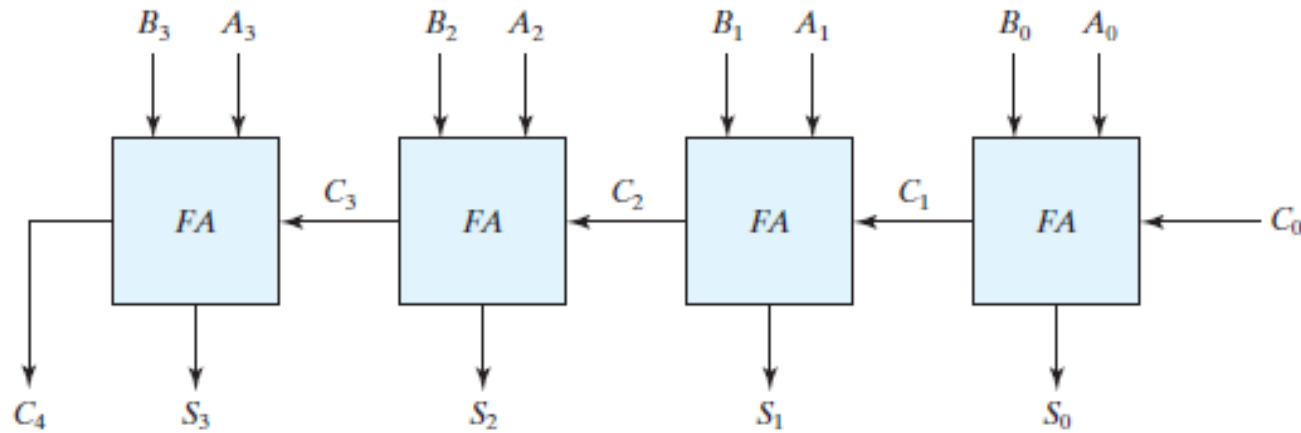

- Also known as ripple carry adder.
- Large combinational/propagation delay
  - $2n$  for normal design for  $n$  bits addition
  - $2n$  for area optimized design for  $n$  bits addition as well

# Carry Look ahead adder

- $G_i$  is called a *carry generate*, and it produces a carry of 1 when both  $A_i$  and  $B_i$  are 1, regardless of the input carry  $C_i$ .

 

**Table 4.4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



# Carry Look ahead adder

- $P_i$  is called a *carry propagate* because it determines whether a carry into stage  $i$  will propagate into stage  $i + 1$  (i.e., whether an assertion of  $C_i$  will propagate to an assertion of  $C_{i+1}$  )


 


Table 4.4  
Full Adder

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
 
# Carry Look ahead adder


$$\begin{aligned}P_i &= A_i \oplus B_i \\G_i &= A_i B_i \\S_i &= P_i \oplus C_i \\C_{i+1} &= G_i + P_i C_i \\C_0 &= \text{input carry} \\C_1 &= G_0 + P_0 C_0\end{aligned}$$



$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

# Carry Look ahead adder

 


$C_0 = \text{input carry}$

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

 
# Four bit adder with carry Look ahead adder



What is the delay of a n-bit adder?

**Constant 4**
 
# Area overhead of Carry look ahead adder



$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

- It requires a very large number of gates.
- For each stage of the adder it is necessary to have an OR gate with  $n$  inputs and  $n$  AND gates with 1 through  $n$  inputs
- Modern day computer is 64-bit word

# Carry look ahead adder

- The limitation can be overcome, though at the expense of computation speed.
- By dividing the  $n$  stages of the adder into groups such that within each group a full carry look ahead is achieved while a ripple carry is maintained between groups.
- For group of size  $k$ -stages, delay:  
 **$4 + (2n/k)$**
- Area overhead:

