

CS221: Digital Design

Latches and FF

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Reference

VahidBook: Frank Vahid, Digital Design (Preview Edition), Wiley India Edition, 2005 [*FF and Register design*]


Outline

- Combinational Vs Sequential Logic Design
- Design a **Latch**, that stores one bit
 - RS latch, **Race condition**
- Stabilizing RS latch : Level Sensitive
- Clocked Latch : Flip Flop- Edge Sensitive
- JK-Latches (**Race in JK Latch**), JK-FF, T flip flops
- Characterization Table and Equation
 - RS, D, JK and T Flip flop

SR Latch Race Condition

Problem with SR Latch: $SR=11$




 
- Problem
 - If $S=1$ and $R=1$ simultaneously, we don't know what value Q will take (Unpredictable)



Race Condition :-

**Who will win 0 or 1?
Eventually, what will be the
value of Q?**

Problem with SR Latch

   
 


Action 1: $S=1, R=1$: Q and Q' both settled at 0

Action 2: Then change to $S=0, R=0$





Problem: After changing to $S=0, R=0 \implies$ Non Predictable behavior : Q should be 0, but it do not

R-S Latch Feedback Different View

  


Looks compact, can be drawn
in small space, proper cross
coupled view

Problem with SR Latch

    


 Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.



Solution to Race Condition

 - We try to avoid $S=1$ and $R=1$ by the following circuit





- Can we ensure value $S=1$ and $R=1$ will not happen at the same time?

Problem with SR Latch

- Problem not just one of a user pressing two buttons at same time
- Can also occur even if SR inputs come from a circuit that supposedly never sets $S=1$ and $R=1$ at same time
 - But does, due to different delays of different paths

Problem with SR Latch



- $X=1$ and $Y=1$ set

  

The longer path from X to R than to S causes $SR=11$ for short time – could be long enough to cause oscillation



Solution: Level-Sensitive SR Latch

  - Add enable input “C or En”
 - Only let S and R change when $C = 0$: Ensure circuit in front of SR never sets $SR = 11$, except briefly due to path delays
 - Change C to 1 only after sufficient time for S and R to be stable
 - When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch’s S1 R1 inputs.





Level-sensitive SR latch symbol

Level Sensitive: SR Latch with NAND Gate

  


Level-sensitive SR
latch symbol

 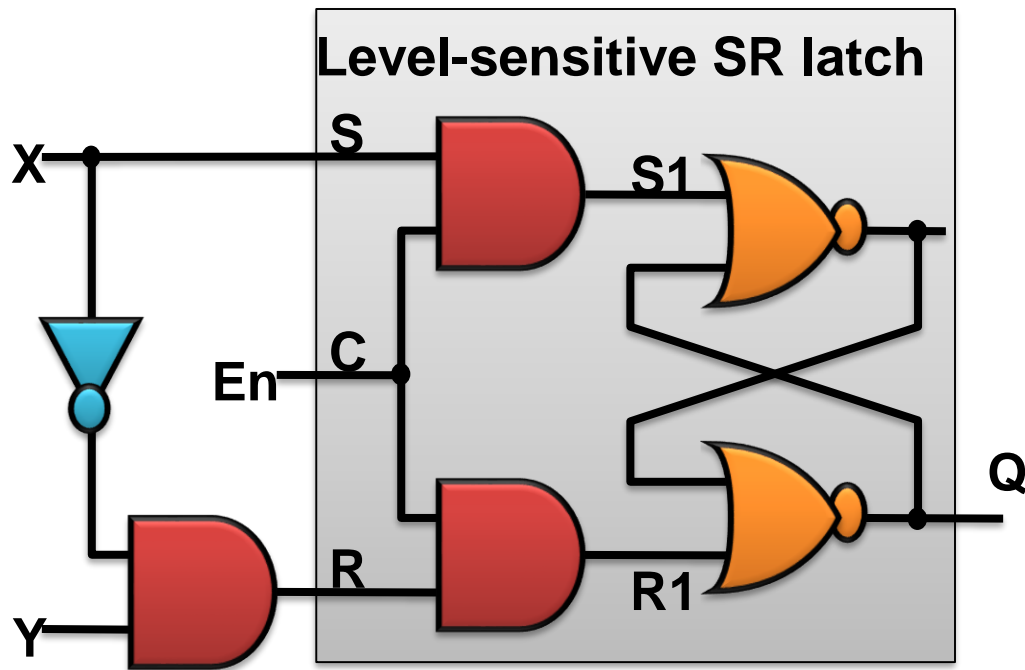Ensure $S=1$ and $R=1$ should not happened to Level-Sensitive SR Latch



Solution: Ensure, Stabilize, Store

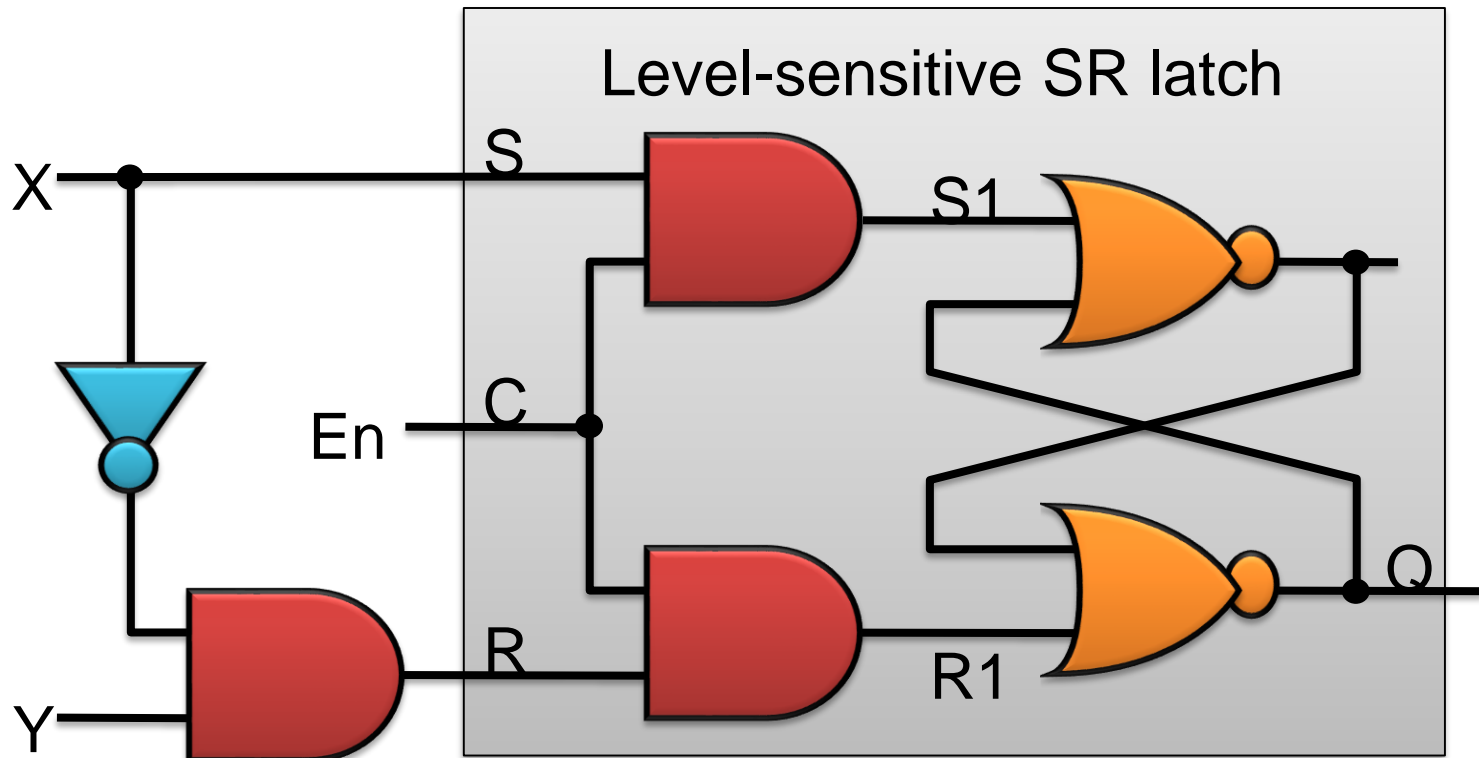

Ensure
Stage

Never Happens
SR=11


Stabilize
Stage

When C=0
Stabilize SR and
Use when C=1

Store
Stage

Store bit

Clocks

 



- ***Clock period***: time interval between pulses
- ***Clock cycle***: one such time interval
- ***Clock frequency***: $1/\text{period}$

– frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$

- $1 \text{ Hz} = 1/\text{s}$


Freq	Period
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

Clock Signal for RS latch

  




Clock Signals for a RS Latch

 - How do we know when it's safe to set $C=1$?
 - Most common solution – make C pulse up/down
 - $C=0$: Safe to change X, Y $C=1$: Must *not* change X, Y
 - **Clock** signal -- Pulsing signal used to enable latches
 - Because it ticks like a clock
 - Sequential circuit whose storage components all use clock signals: **synchronous** circuit



Level-Sensitive D Latch

   
- SR latch requires careful design to ensure $SR=11$ never occurs
- D latch relieves designer of that burden
 - Inserted inverter ensures R always opposite of S



D latch symbol

Level-Sensitive D Latches

 
- Suppose D FFs are arranged in linear fashion connected using a single clock signal Clk
- Every clock we want to shift one bit to right
 - Right shift one bit per cycle



**Does this circuit (with level sensitive D latch)
Shift one bit per cycle ?**

 
Problem with Level-Sensitive D Latch

- D latch still has problem (as does SR latch)
 - When $C=1$, through how many latches will a signal travel?
 - Depends on for how long $C=1$
 - Clk_A -- signal may travel through multiple latches
 - Clk_B -- signal may travel through fewer latches
 - **Hard to pick C that is just the right length**




 Problem with Level-Sensitive D Latch

- We want do the work: one per clock cycle
 - Independent of length of clock (1 time)



 - Can we design bit storage that only stores a value on the rising edge of a clock signal?
 - There is exactly one rising edge per clock cycle
 - There is exactly one falling edge per clock cycle



Make Edge Sensitive Bit Storage

- Latch : Level sensitive storage
- Flip-Flop : Edge sensitive storage
 - Value get changed only at edges of clock




How to make a
Flip Flop out of
Latch?

Master -Slave D Flip-Flop

- **Two latches**, output of first goes to input of second, master latch has inverted clock signal
- So master loaded when $C=0$, then servant when $C=1$
- When C changes from 0 to 1, master disabled, servant loaded with value that was at D just before C changed
 - i.e., Value at D during rising edge of C

Master -Slave D Flip-Flop


 
- ***Flip-flop***: stores on clock edge, not level




Master loaded when $C=0$, then servant when $C=1$

When C changes from 0 to 1, master disabled, servant loaded with value that was at D just before C changed -- i.e., value at D during rising edge of C


D Flip-Flop (Rising & Falling Edges)

  

Rising edges

 


Falling edges

 

D Flip-Flops

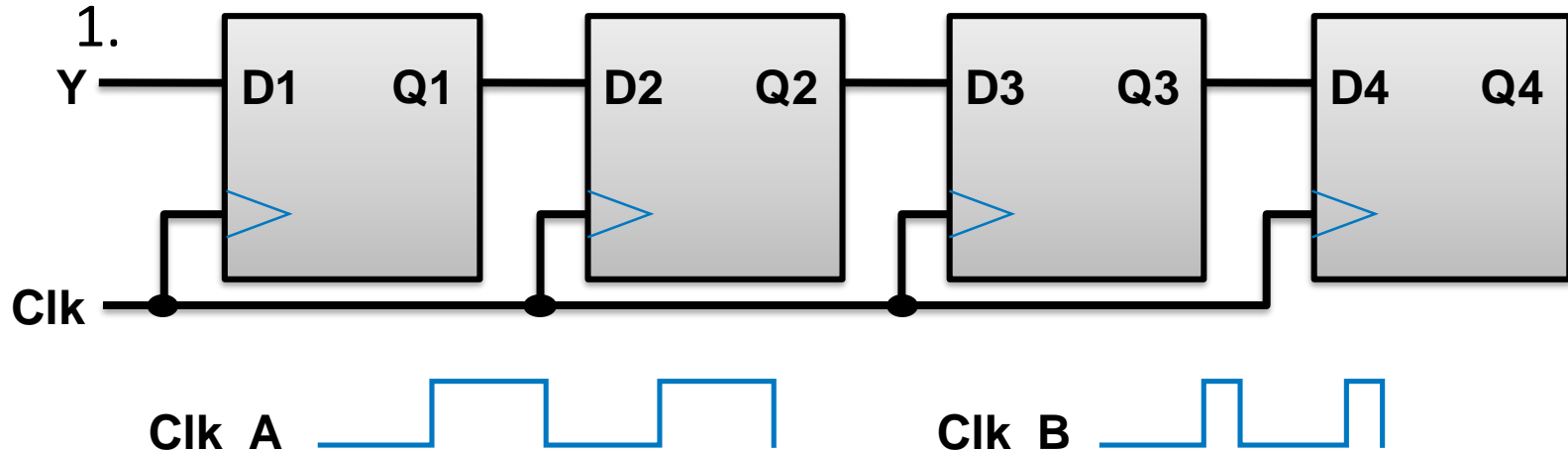- Solves problem of not knowing through how many latches a signal travels when $C=1$
 - Signal travels through exactly one FF, for Clk_A or Clk_B. **Why?**
 - Because on rising edge of Clk, all four flip-flops are loaded simultaneously -- then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is




Two latches inside each flip-flop

D Latch vs. D Flip-Flop


- Latch is level-sensitive: Stores D when C=1
- Flip-flop is edge triggered: Stores D when C changes from 0 to 1
 - Saying “level-sensitive latch,” or “edge-triggered flip-flop,” is redundant
 - Two types of flip-flops -- rising or falling edge triggered.

 Positive Edge Triggered D-Flip Flop: Optimization



GATE COUNT: 10
4 NOR, 4 AND
and 2 NOT

Remember: SR Latch with NAND Gates

 


S	R	Q+
0	0	1*0* (Unpredictable)
0	1	1
1	0	0
1	1	Q

Opposite to SR Latch with NOR Gates

Set will do $Q=0$ and Reset will $Q=1$


Positive-Edge Triggered D-FF: Economical

 - When $CLK=0$, $S'R'=11$, $Q^+=Q$ (Independent of D)




Positive-Edge Triggered D-FF: Economical

- When $\text{CLK}=1$, $D=0$, $Q^+=0$

 


Positive-Edge Triggered D-FF: Economical

 - After that When $CLK=1$, $D=1$: No changes to $R'S'$:
 $Q^+=0$ It locked



Positive-Edge Triggered D-FF: Economical

 


GATE COUNT: 6
6 NAND, Same types

**Transistor level optimization
is
out of syllabus**

But showing two slides 😊 😊 😊


Master-Slave Edge-Triggered Flip-Flop

2 x 8 = 16 Transistors

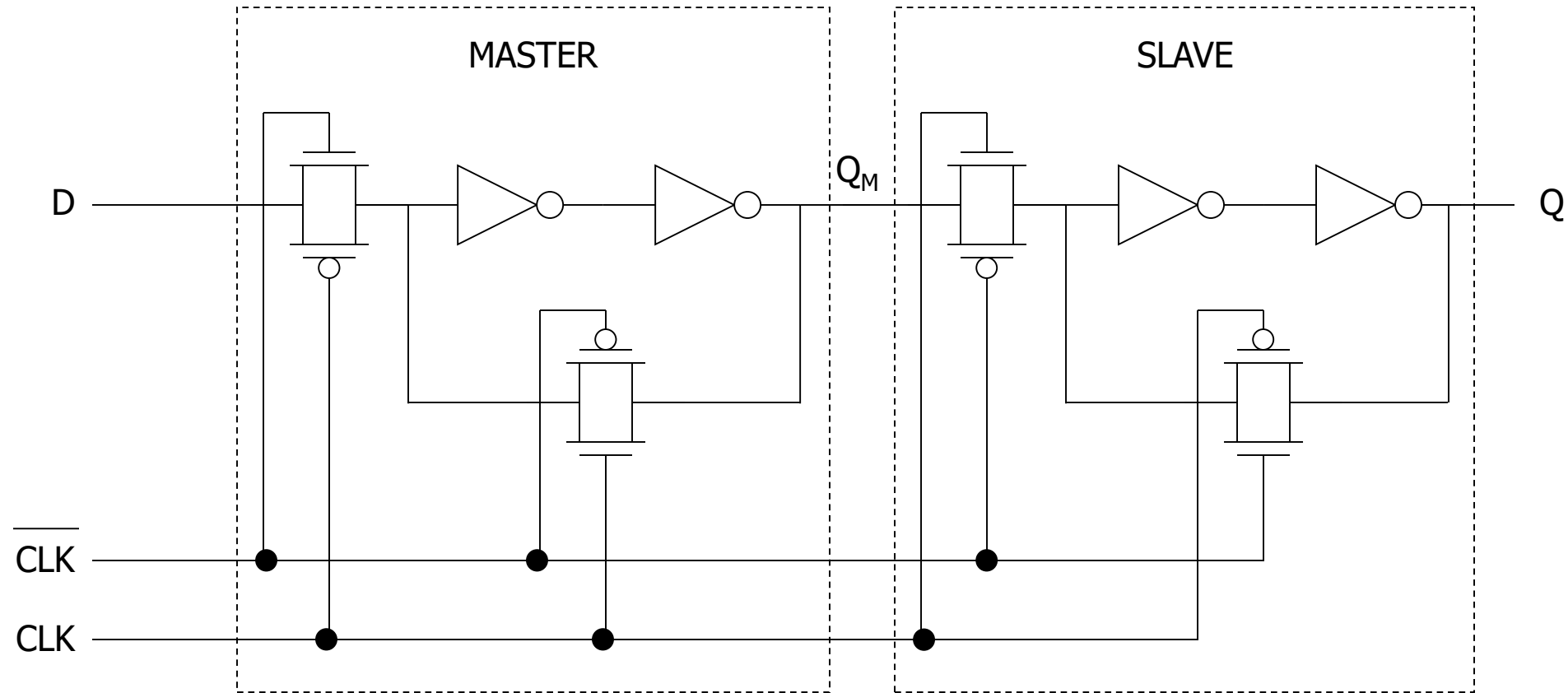

More Efficient Master-Slave Edge-Triggered Flip-Flop

- Called a C²MOS (Clocked CMOS) design

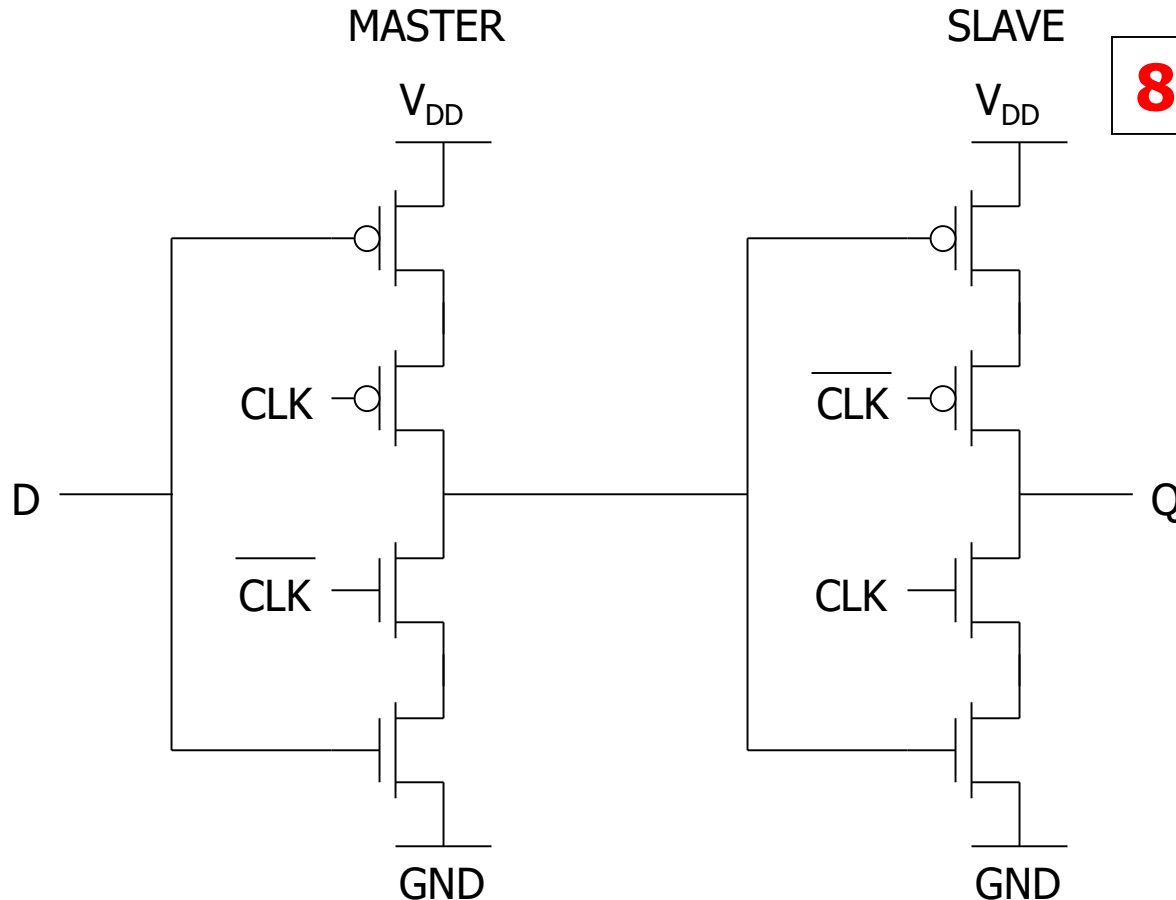


8 Transistors

Problem handled in Designing FF

- ✓ OR Gate : worked just like a ringing bell
- ✓ OR gate with Feed back : ($Q=1$ can never be changed)
- ✓ Two NOR gates with cross coupled out put and input : Solved to store a bit but Race condition
- ✓ Ensure $RS=11$ will not happed by adding Not and AND gate
- ✓ Stabilize: Enable Signal to put remove : delay of added Ckt
- ✓ RS Latch to D-Latch : Ensure no $SR=11$
- ✓ Master Slave Latches to make a Flip Flop (or edge triggered Latch)
- ✓ Optimized D-FF (using only NAND Gates)
- ✓ Further optimized lower level using only 8 transitors

J-K Latches

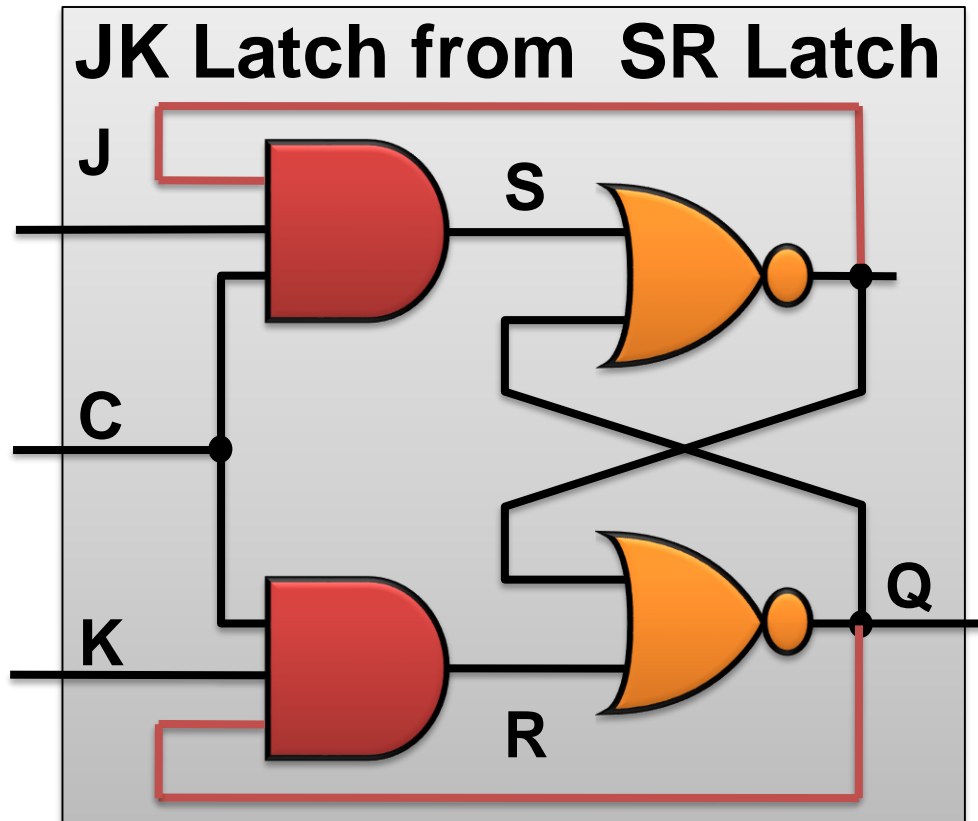
- The JK flip-flop augments the behavior of the SR flip-flop (J=Set, K=Reset) by interpreting the $S = R = 1$ condition as a "flip" or toggle command.



J	K	Q^+
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

$$Q^+ = K'Q + JQ'$$

J-K Latches: Problem

 

**Q Oscillate
between when C=1**

