
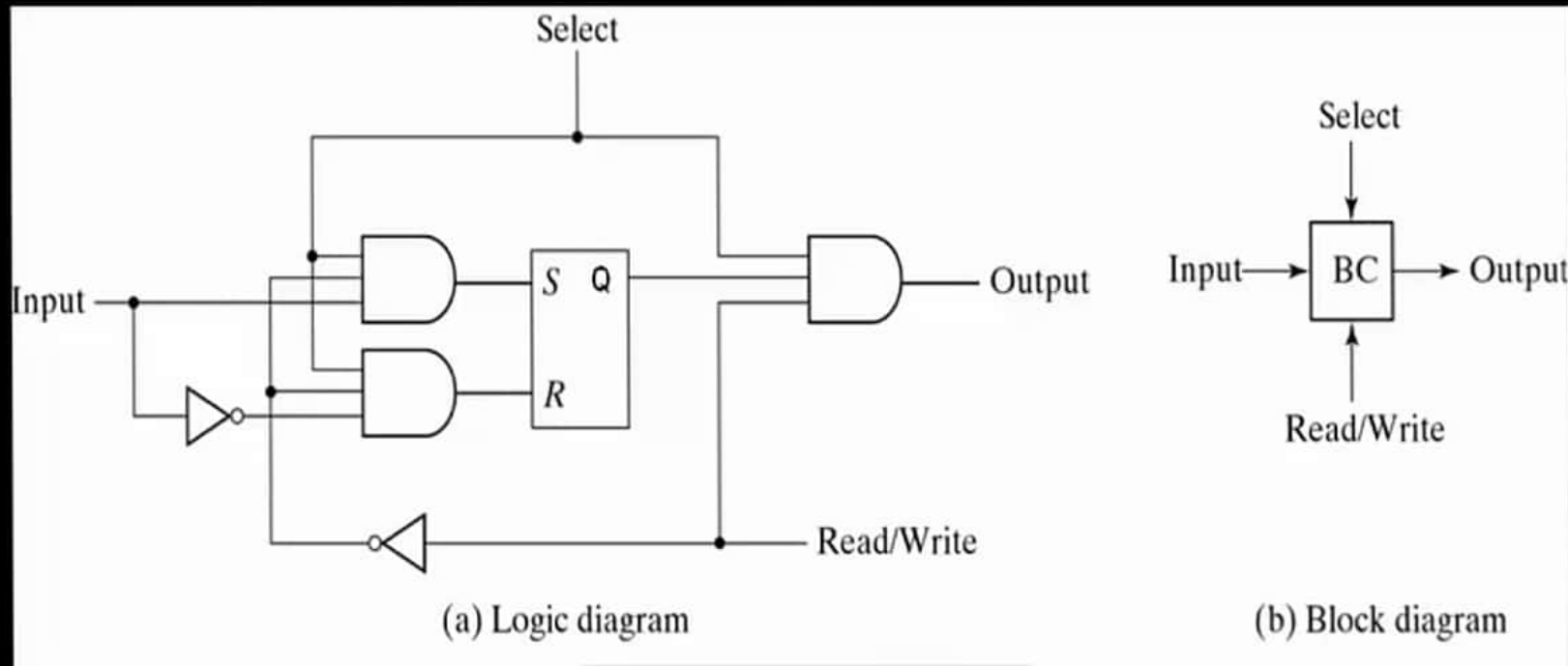
 


1

CS101-2021
INTRODUCTION TO COMPUTING
LEC – 6
MEMORY MEMORABILIA (CONTD.)




RAM: ONE BIT

 - Basis of each RAM cell is an S-R latch
- Note that data goes to both S and R
- Select enables operation
- Read/write enables read **OR** write, but not both





RAM: ONE BIT

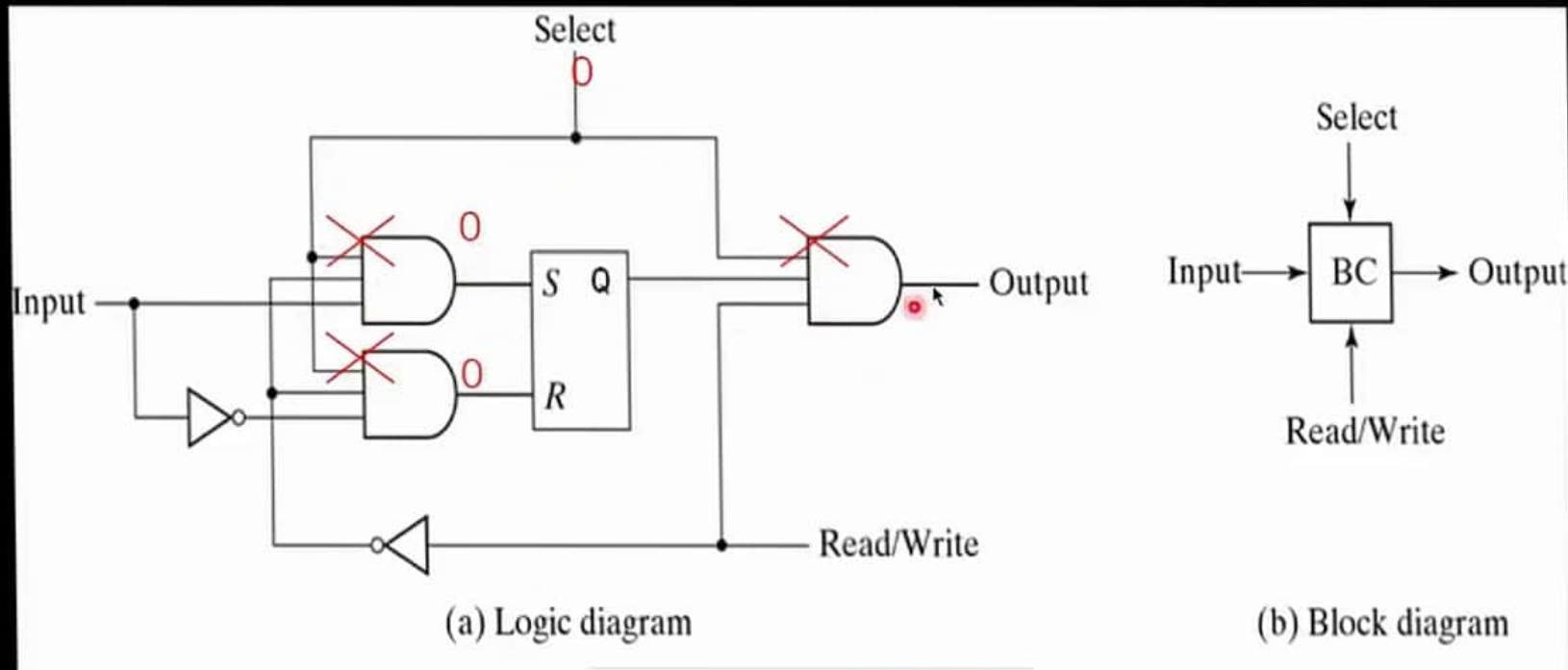  - Basis of each RAM cell is an S-R latch
- Note that data goes to both S and R
- Select enables operation
- Read/write enables read **OR** write, but not both






RAM: ONE BIT

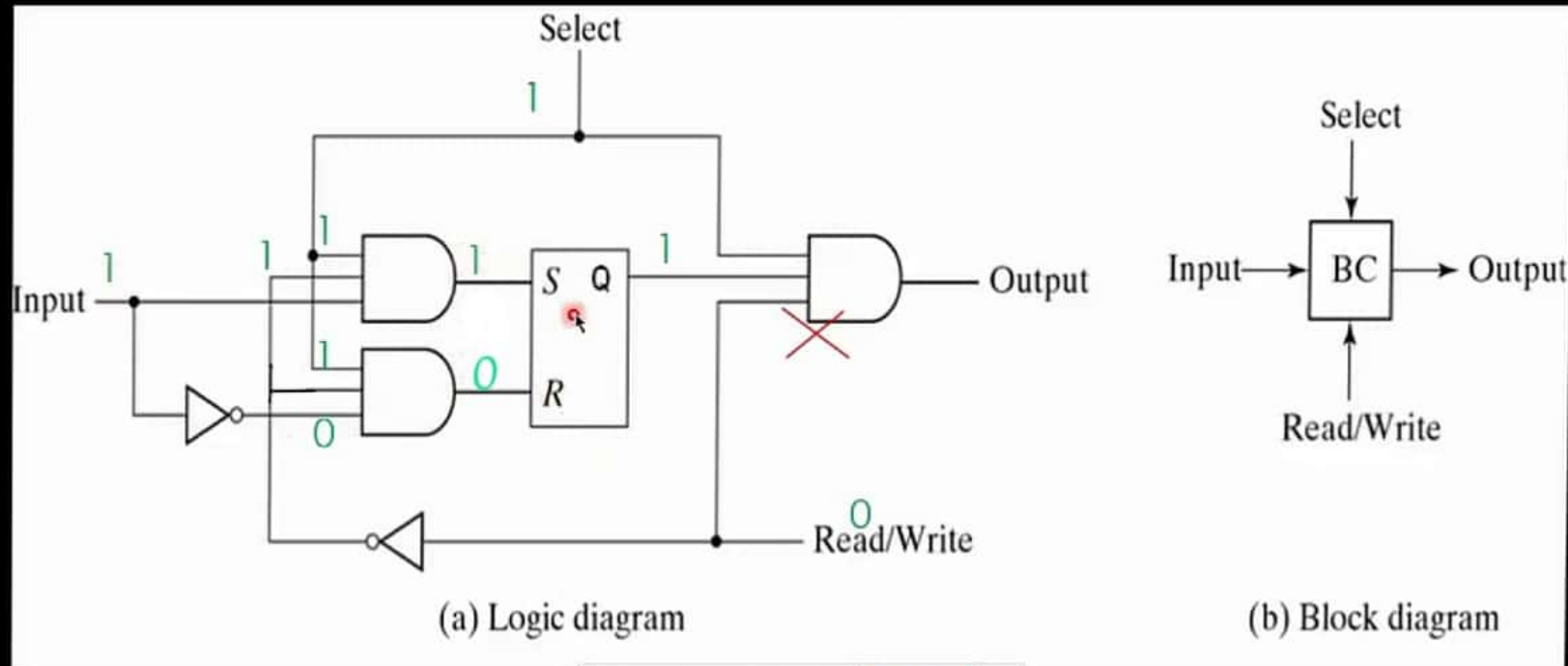 - Basis of each RAM cell is an S-R latch
- Note that data goes to both S and R
- Select enables operation
- Read/write enables read **OR** write, but not both






RAM: ONE BIT

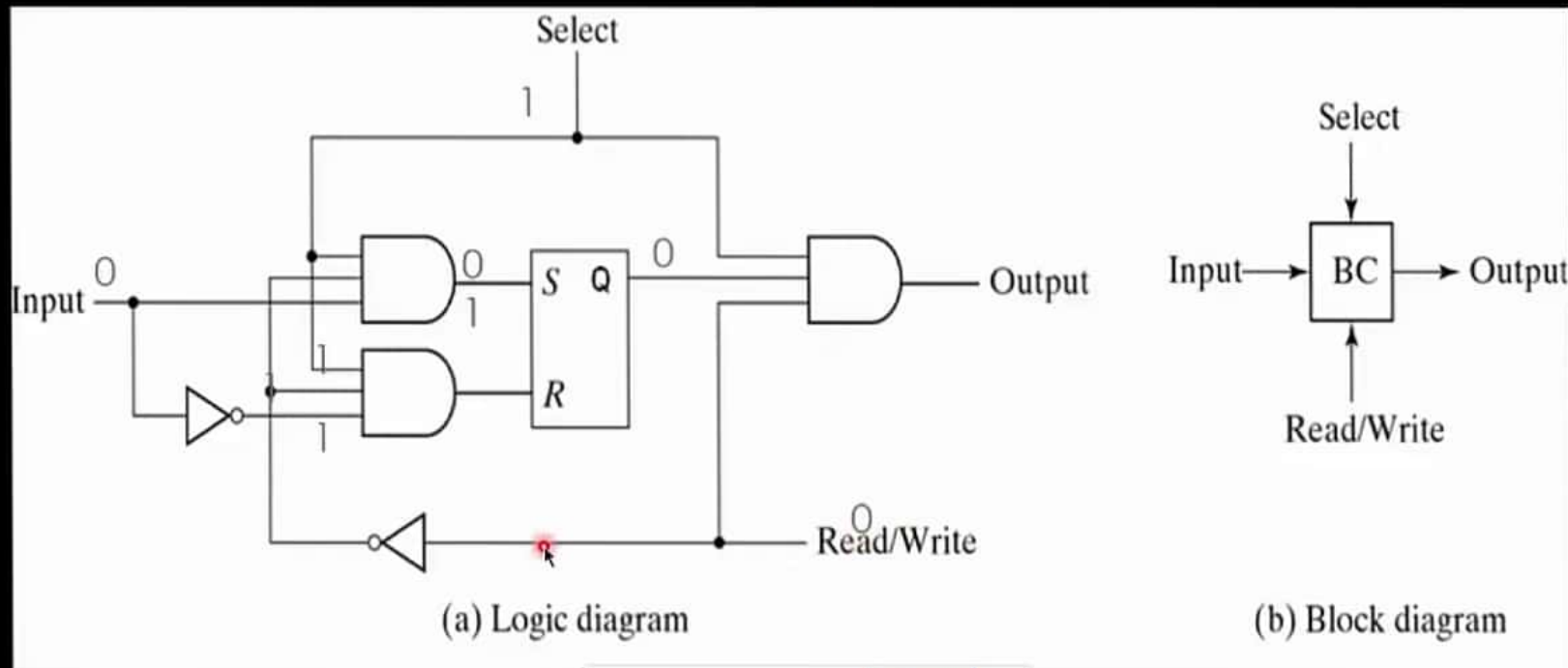  - Basis of each RAM cell is an S-R latch
- Note that data goes to both S and R
- Select enables operation
- Read/write enables read **OR** write, but not both



RAM: ONE BIT

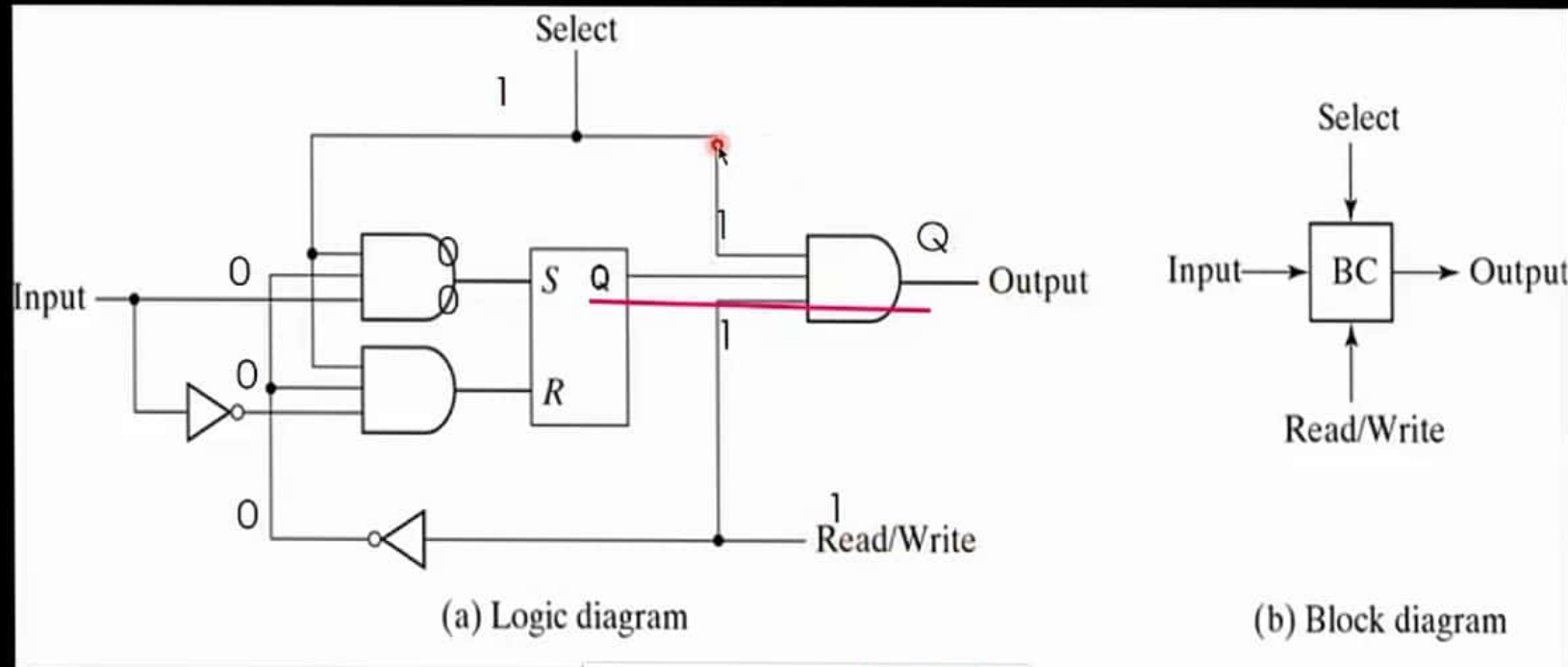  - Basis of each RAM cell is an S-R latch
- Note that data goes to both S and R
- Select enables operation
- Read/write enables read **OR** write, but not both




2-to-4 decoder **RECAP**

3

2 inputs and 2^2 outputs

S1	S0		Q ₃	Q ₂	Q ₁	Q ₀
0	0		0	0	0	1
0	1		0	0	1	0
1	0		0	1	0	0
1	1		1	0	0	0

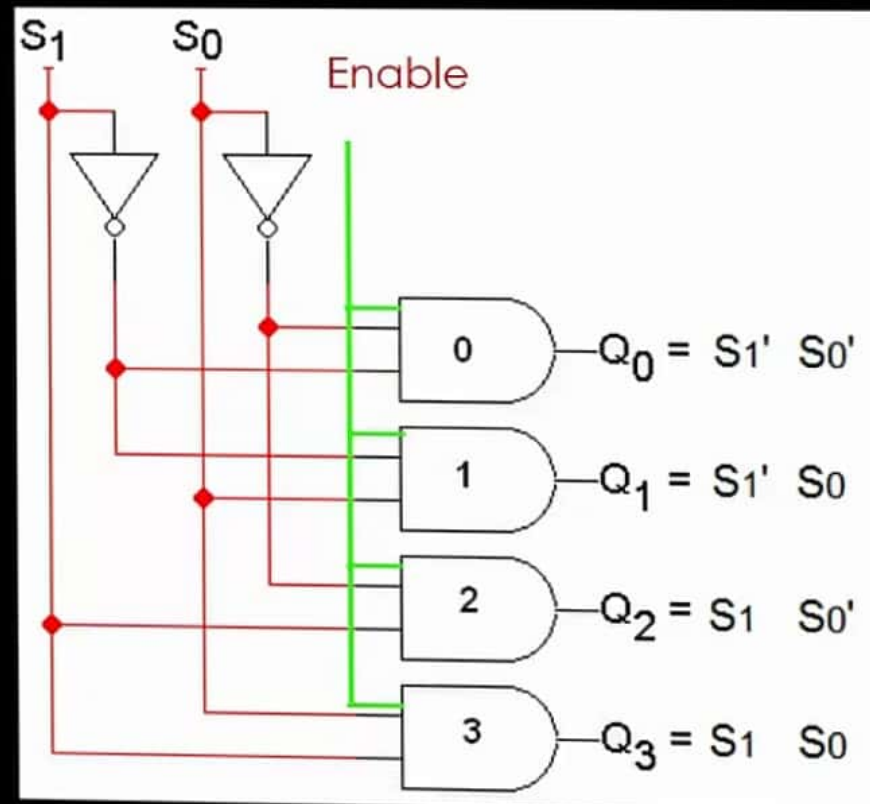

**When Enable = 0 all outputs are 0 irrespective of S0 and S1.
The circuit behaves as a decoder only when Enable = 1
Enable can be used to switch ON or switch OFF decoding.**

3/17/2021

Shivashankar B. Naik CS101, 2021


RAM (R/W MEMORY)

Data input

One Word
Word

Address Bus

Control Bus

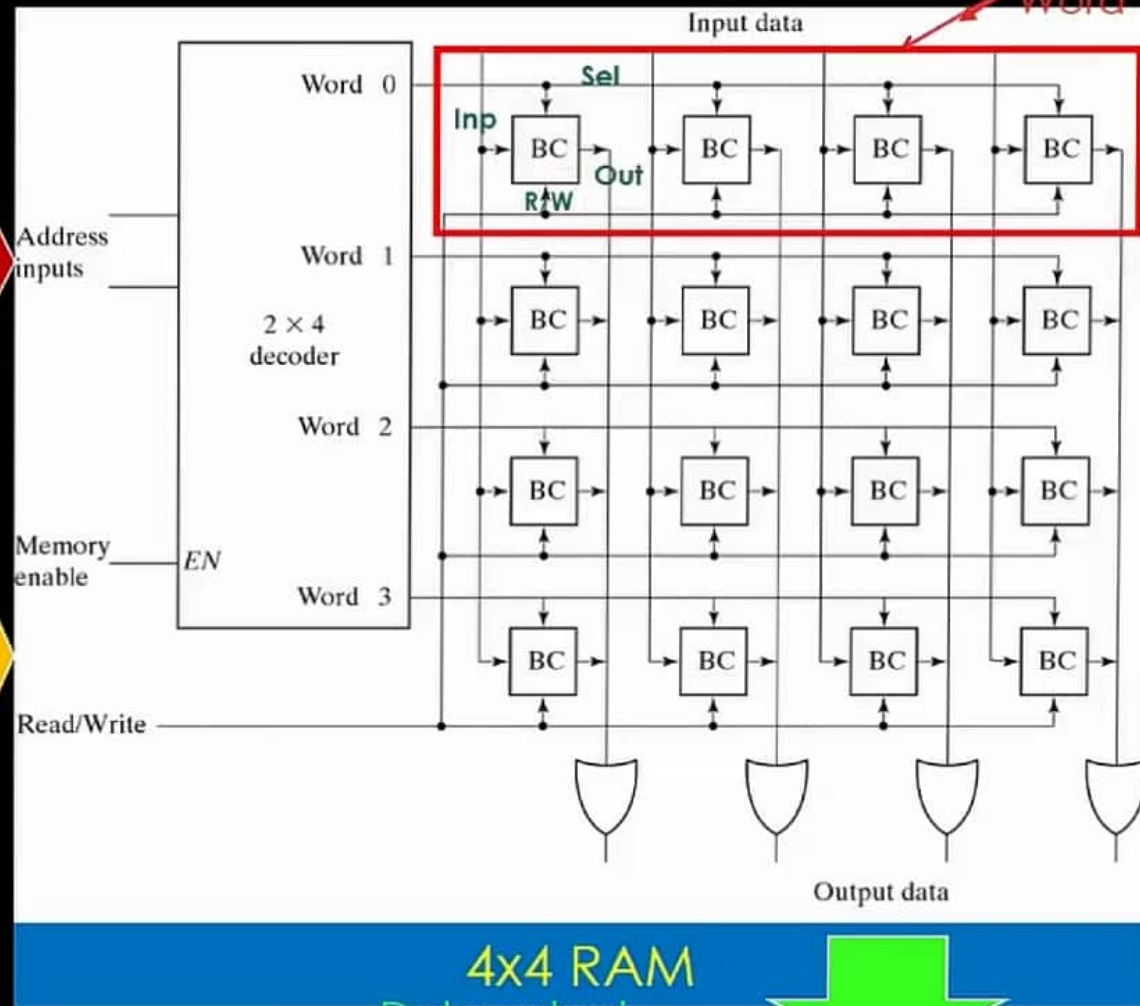

4x4 RAM
Data output


3/17/2021

Shivashankar B Nair CS101-2021

RAM

5

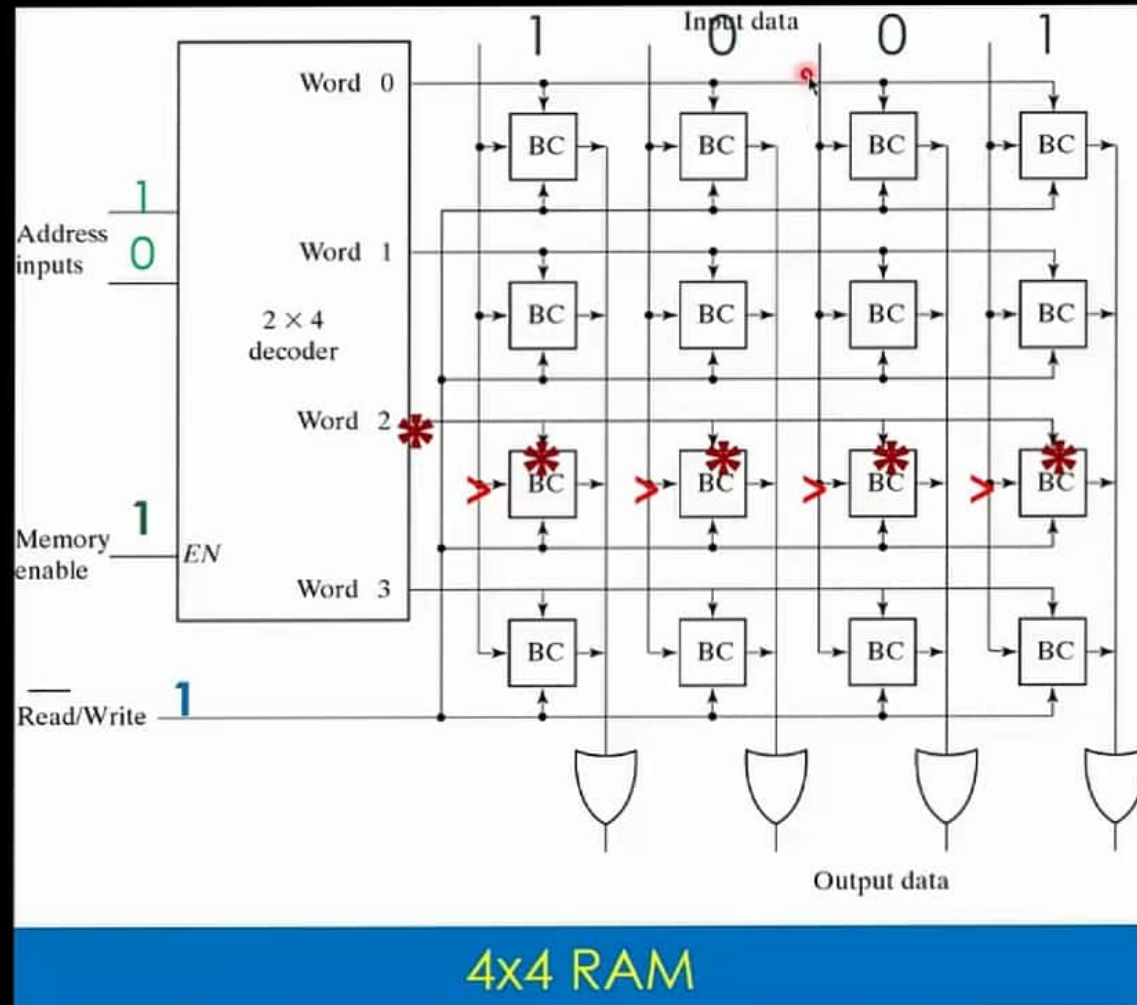- Address inputs go into decoder
 - Only one output active
- Word line selects a row of bits (word)
- Data passes through OR gate
- Each binary cell (BC) stores one bit
- Input data stored if Read/Write is 0
- Output data driven if Read/Write is 1



4x4 RAM


3/17/2021

Shivashankar B Nair CS101-2021

RAM


5

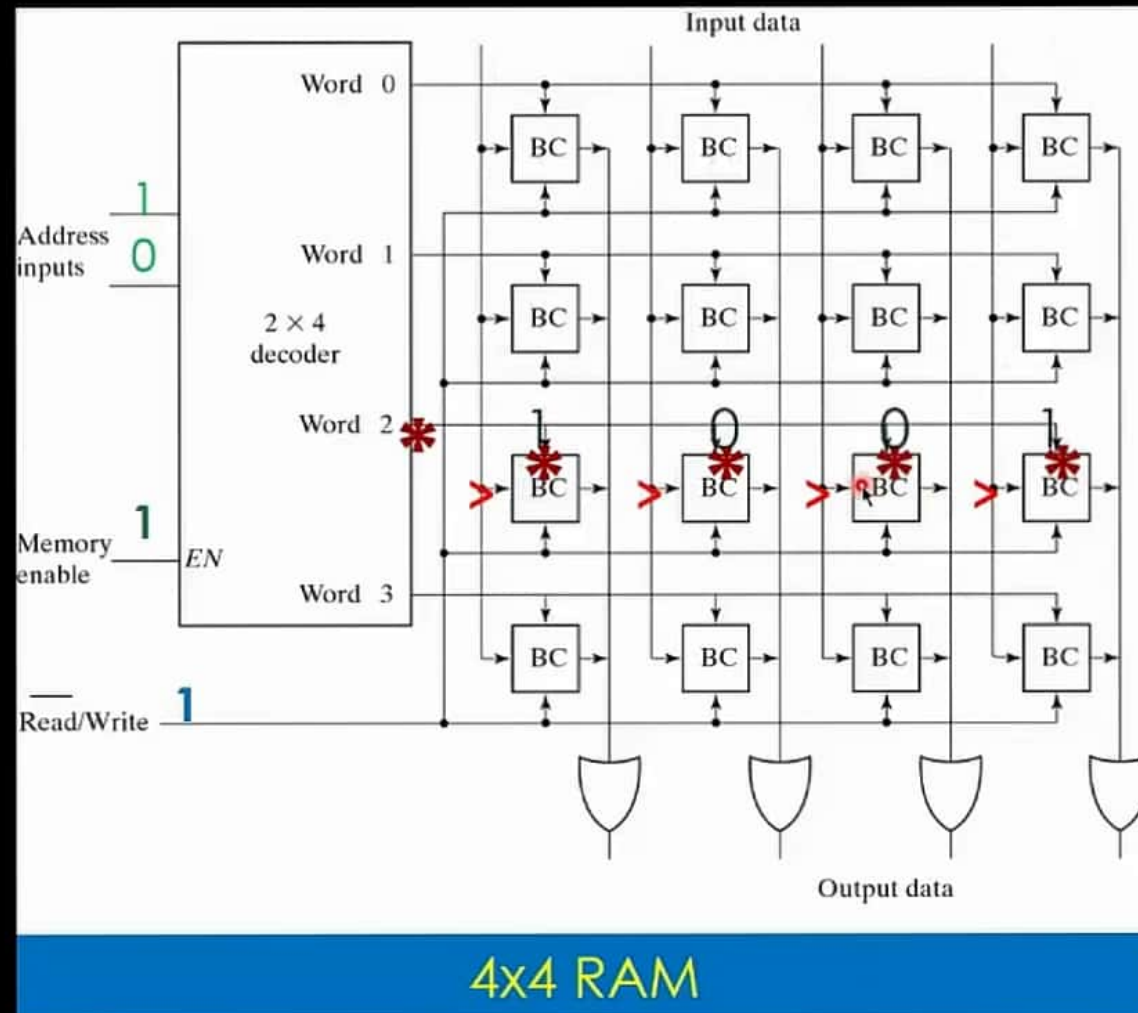- Address inputs go into decoder
 - Only one output active
- Word line selects a row of bits (word)
- Data passes through OR gate
- Each binary cell (BC) stores one bit
- Input data stored if Read/Write is 0
- Output data driven if Read/Write is 1



RAM READING

6

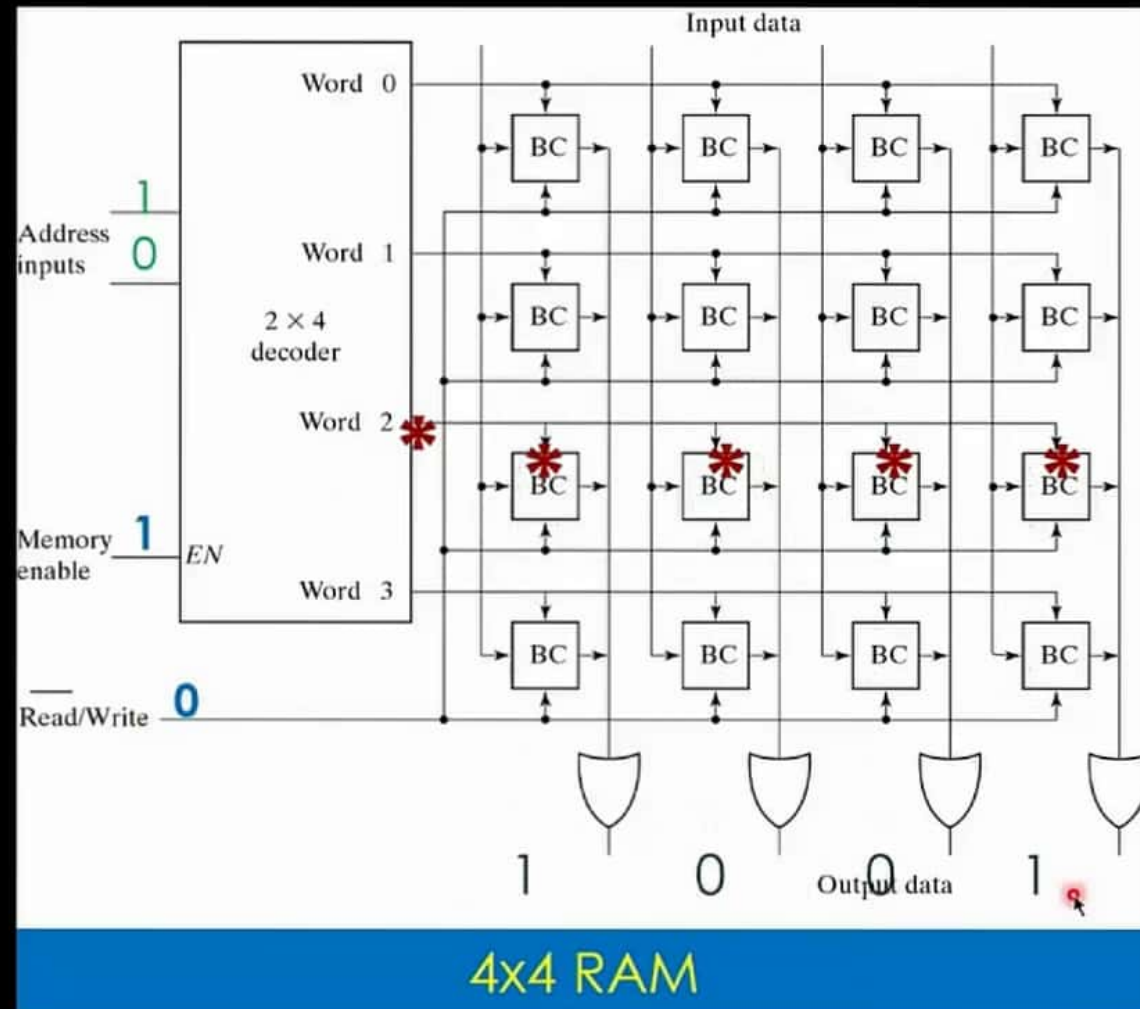


3/17/2021

Shivashankar B Nair CS101-2021

- Typical →
 - Data input bus
 - Data output bus
 - Address
 - Read/Write control
 - Chip Select

Size: $m \times n$

where m = no. of words & n = bits/word

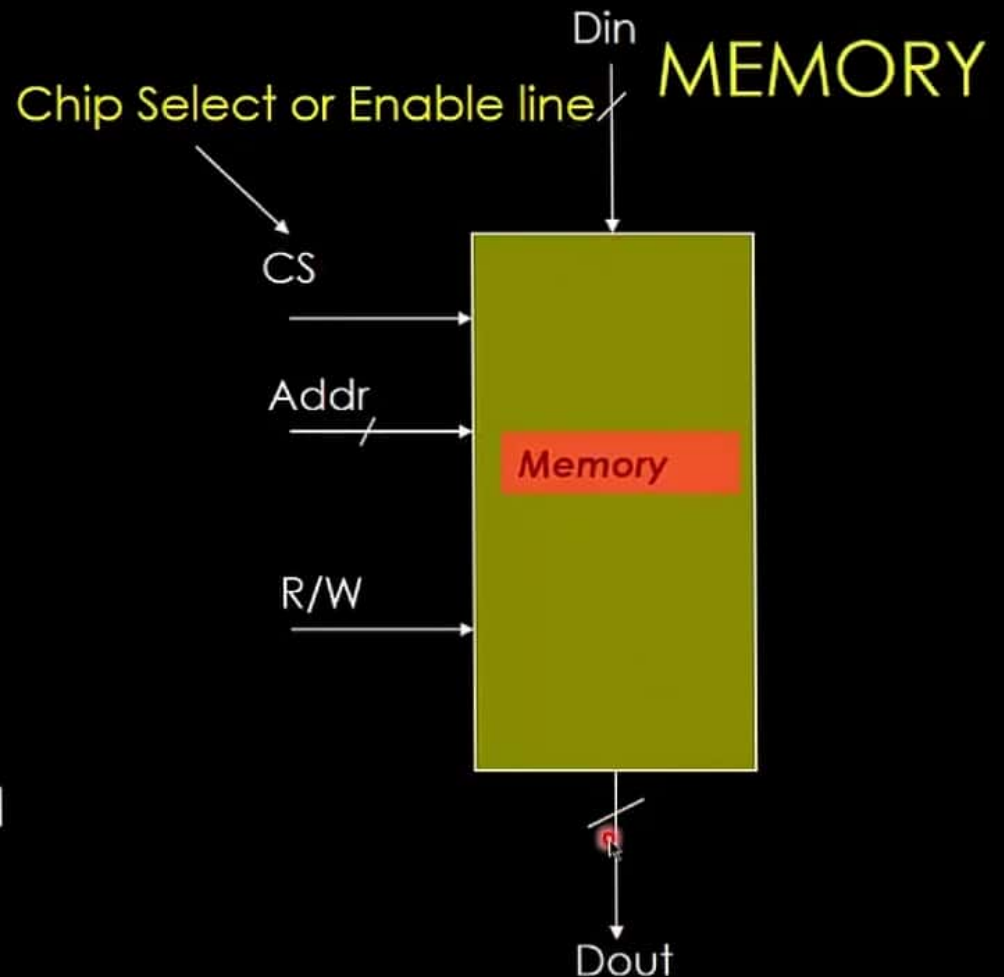

ORGANIZING LEVELS OF MEMORY (STORAGE)

8




Storage	Almirah	Rack	Study Table
Capacity (books stored)	High	Medium	Small
Speed of Access	Slow	Medium	Fast
Transfers done in one stroke	Several Books	One book	Page

3/17/2021

Shivashankar B Nair CS101-2021

LEVELS OF THE MEMORY HIERARCHY

9

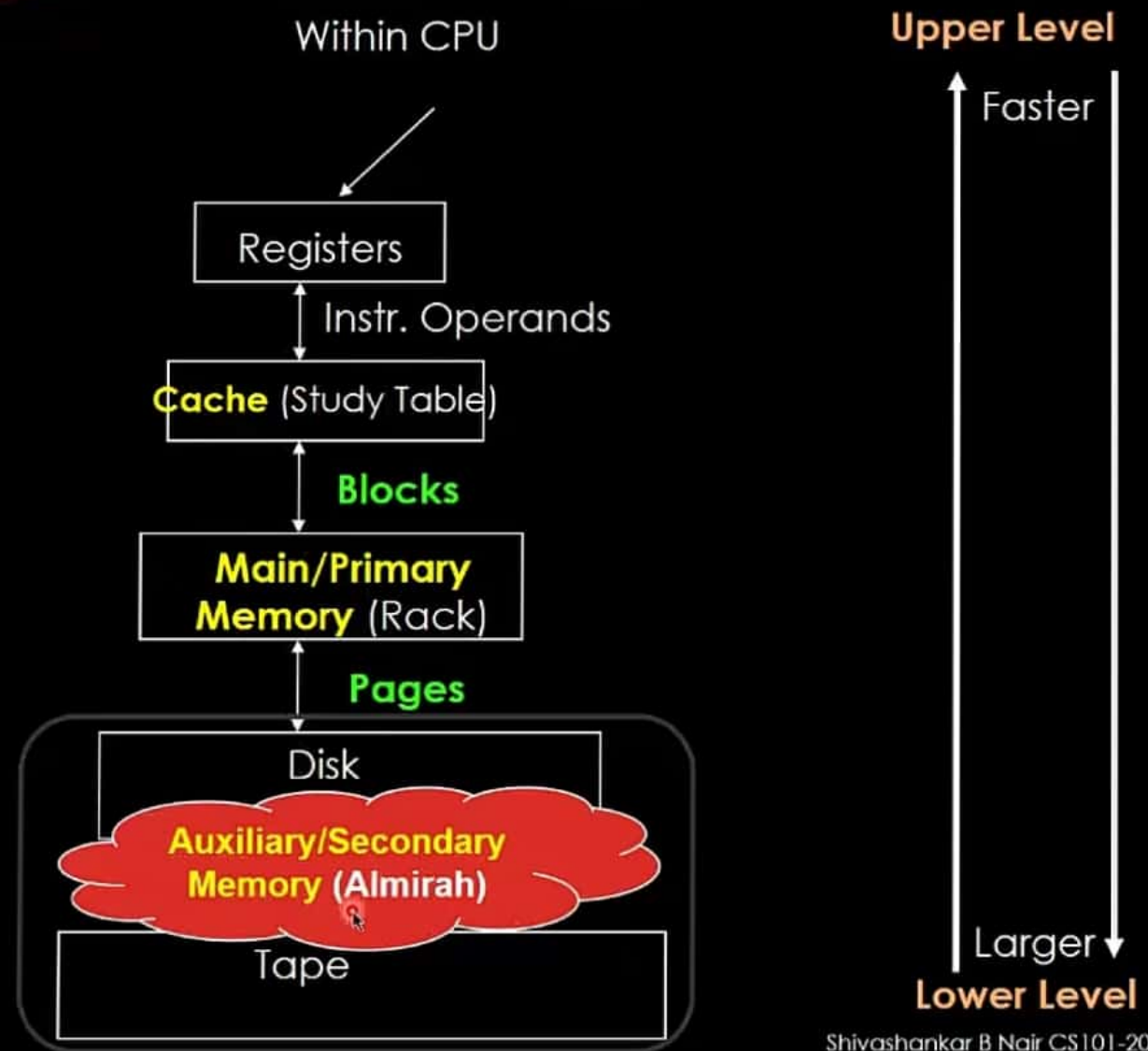

3/17/2021

Shivashankar B Nair CS101-2021