

Multi-level logic Synthesis

Dr. Chandan Karfa

CSE IIT Guwahati



Text Book

- Chapter 6, Z. Kohavi and N. Jha, Switching and Finite Automata Theory, 3rd Ed., Cambridge University Press, 2010.

Objective

- Introduction to Multilevel logic synthesis
- Technology-independent synthesis
 - Factoring
 - Decomposition
 - Extraction
 - Substitution
 - Elimination

Two-level vs Multi-level Logic

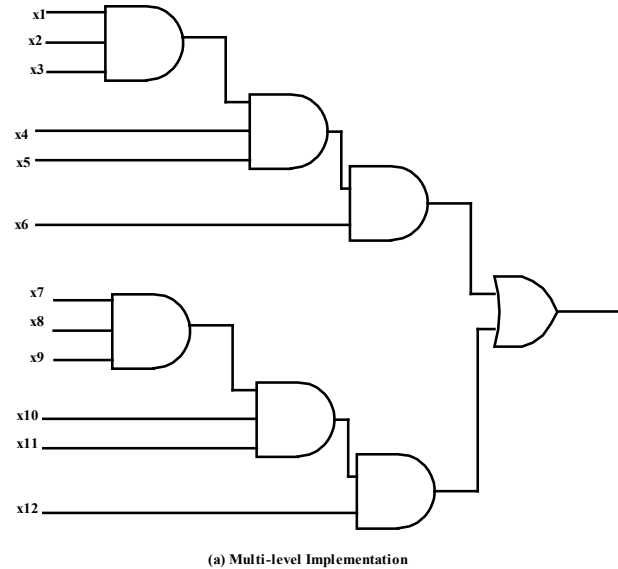 

- Multi-level logic realization contains more than two levels of logic gates.
- Circuits in which an arbitrary number of gates may lie on any path between a primary input and a primary output.

$$xyz + wxz + yz$$

Need for Multi-level Logic Synthesis

- In some cases SoP representation is impractical
 - Example: Parity bit generator, multiplication

| 4-bit received message | | | | Parity error check C_p |
|------------------------|---|---|---|--------------------------|
| A | B | C | P | |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

| CP | | 00 | 01 | 11 | 10 |
|----|----|-----------------------|-----------------------|-----------------------|-----------------------|
| AB | 00 | 0 ⁰ 0 | 1 ¹ 1 | 3 ³ 0 | 2 ² 1 |
| | 01 | 4 ⁴ 1 | 5 ⁵ 0 | 7 ⁷ 1 | 6 ⁶ 0 |
| | 11 | 12 ¹² 0 | 13 ¹³ 1 | 15 ¹⁵ 0 | 14 ¹⁴ 1 |
| | 10 | 8 ⁸ 1 | 9 ⁹ 0 | 11 ¹¹ 1 | 10 ¹⁰ 0 |

Exponential number of implicants in SoP form for parity bit generator

Need for Multi-level Logic Synthesis

- **Advantage:**

- Multi-level logic circuits require less area and delay compared to the corresponding two-level realizations and hence are more practical.

- **Disadvantage:**

- It is difficult to obtain provably optimal multi-level realizations because of the much larger design space available for exploration.


Phases Of Multi-level Logic Synthesis

- Technology Independent Synthesis
- Technology Dependent Synthesis

Objectives

- Reduces the number of literal in expression
 - No of transistors is twice of no of literals
- Identifying common sub-expression within an Boolean Expression (for single output) or between multiple Boolean expressions (for multiple outputs)

$$\begin{aligned}
 PEC &= \bar{A} \bar{B} (\bar{C} D + \underline{C \bar{D}}) + \bar{A} B (\bar{C} \bar{D} + C D) + A B (\bar{C} D + C \bar{D}) + A \bar{B} (\bar{C} \bar{D} + C D) \\
 &= \bar{A} \bar{B} (C \oplus D) + \bar{A} B (\overline{C \oplus D}) + A B (C \oplus D) + A \bar{B} (\overline{C \oplus D}) \\
 &= (\bar{A} \bar{B} + A B) (C \oplus D) + (\bar{A} B + \underline{A \bar{B}}) (\overline{C \oplus D}) \\
 &= (A \oplus B) \oplus (C \oplus D)
 \end{aligned}$$

 



| CP \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 1 | 0 | 1 |
| 01 | 1 | 0 | 1 | 0 |
| 11 | 0 | 1 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |

Representation

- As Logic Network

$$x = ab$$

$$y = c + ab$$

  

Logic Network

- input variables (a, b, c, d, e)
- primary output variables (**w, x, y, z**).

$$p = ce + de$$

$$q = a + b$$

$$r = p + a'$$

$$s = r + b'$$

$$t = ac + ad + bc + bd + e$$

$$u = q'c + qc' + qc$$


$$v = a'd + bd + c'd + ae'$$

$$w = v$$

$$x = s$$

$$y = t$$


$$z = u$$

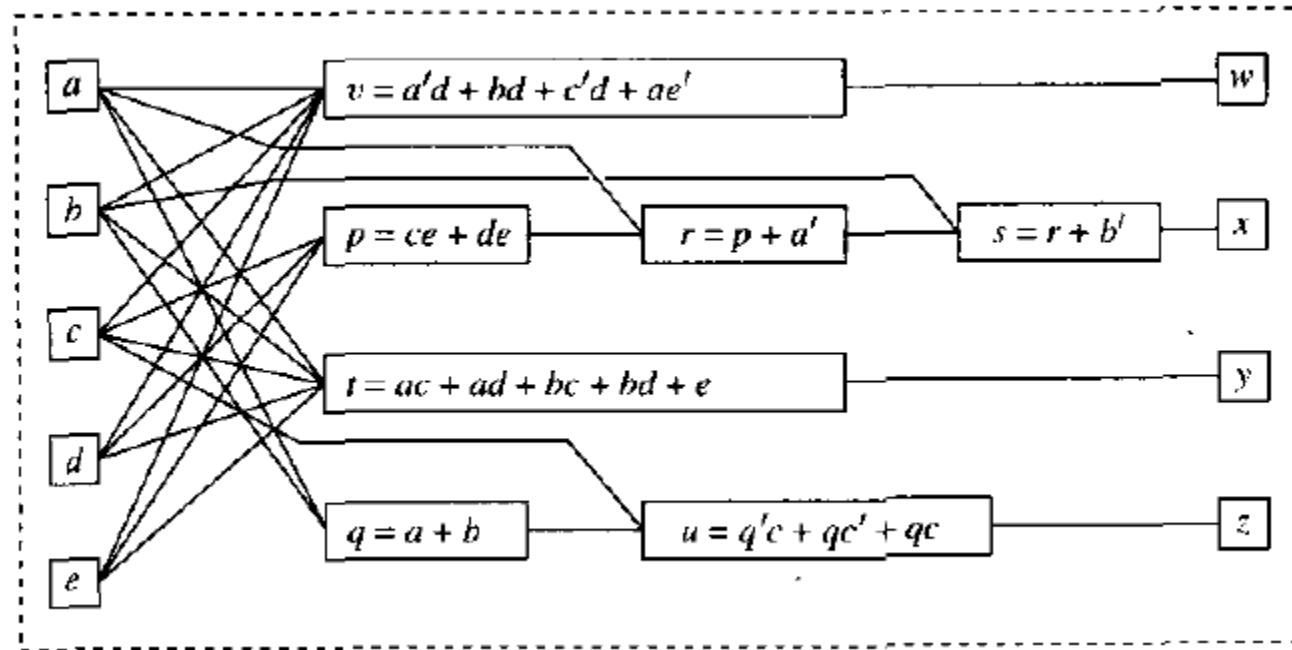




Technology Independent Synthesis

- We design the circuit without keeping in mind we have to map that circuit to certain technology.
- The problem is intractable.
 - Primarily the heuristic based approaches are used.
- Technology-independent multi-level logic synthesis is carried out with the help of various logic transformations.


FPGA Technology Mapping

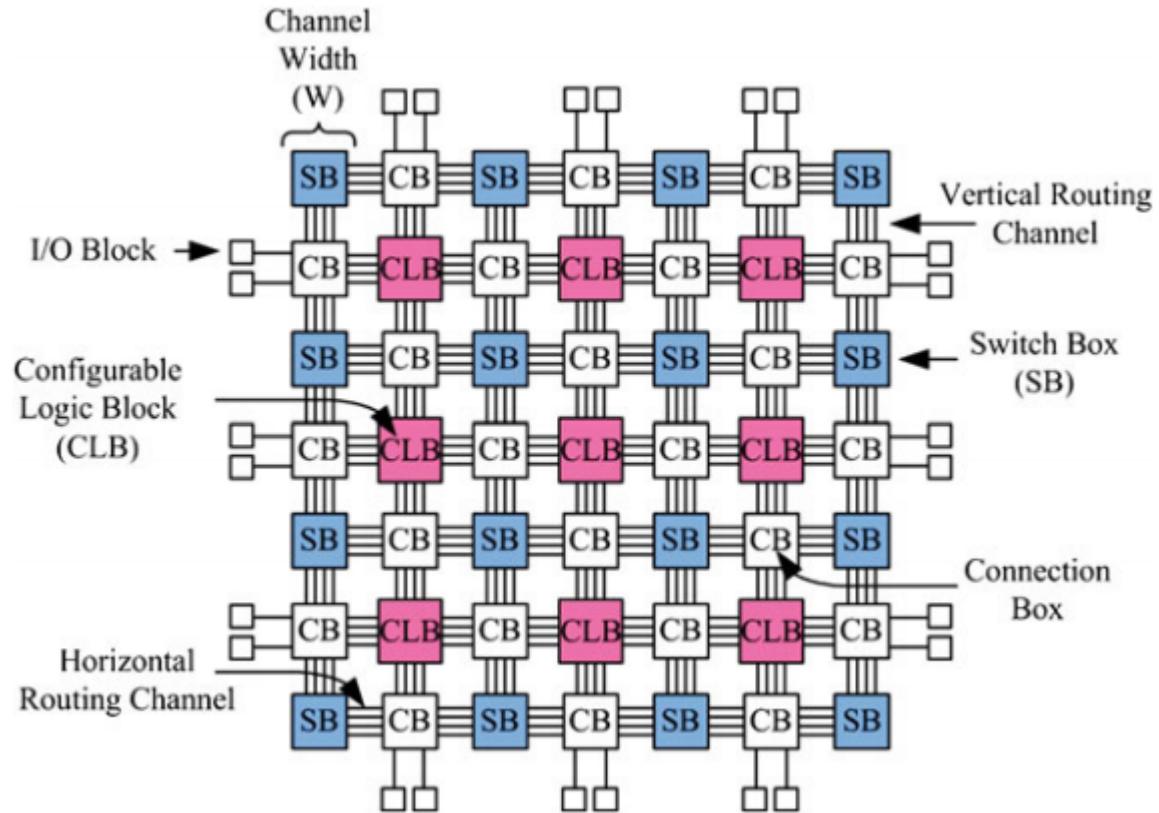

FPGA Components

 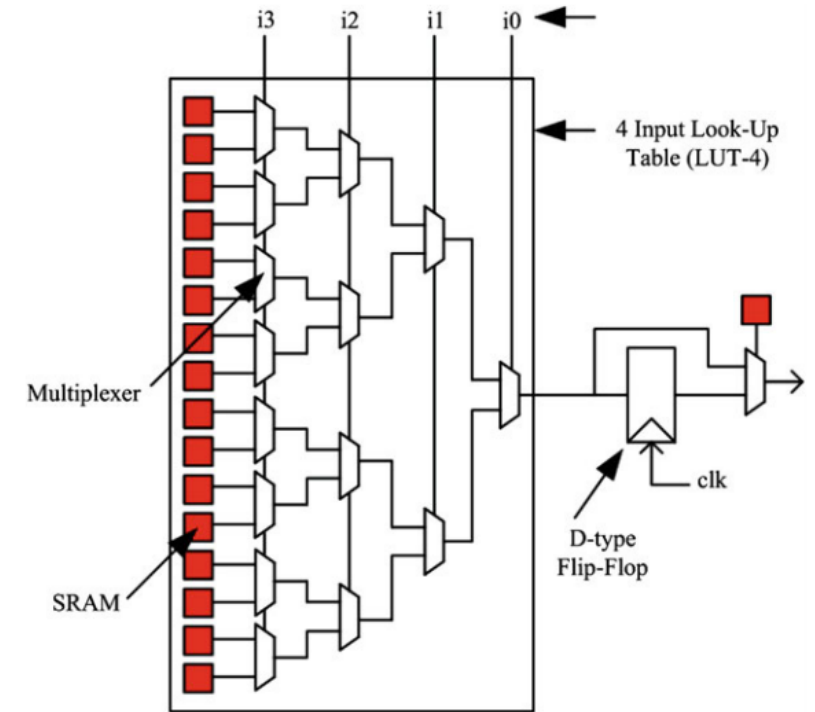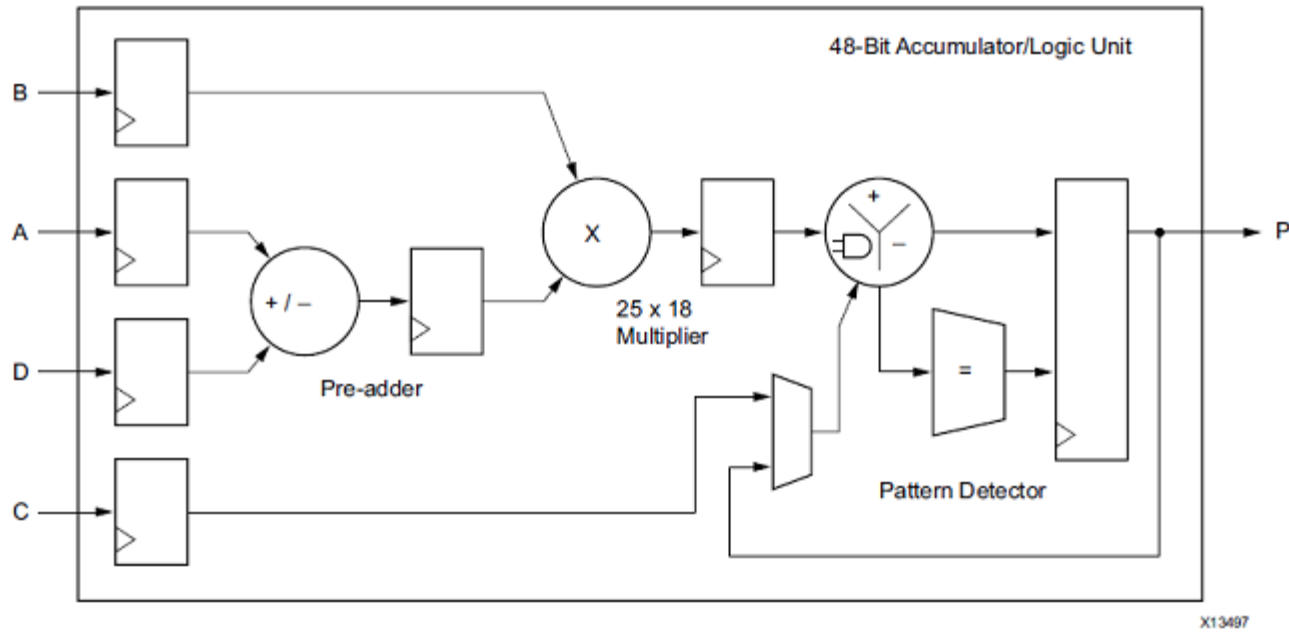

Interconnections

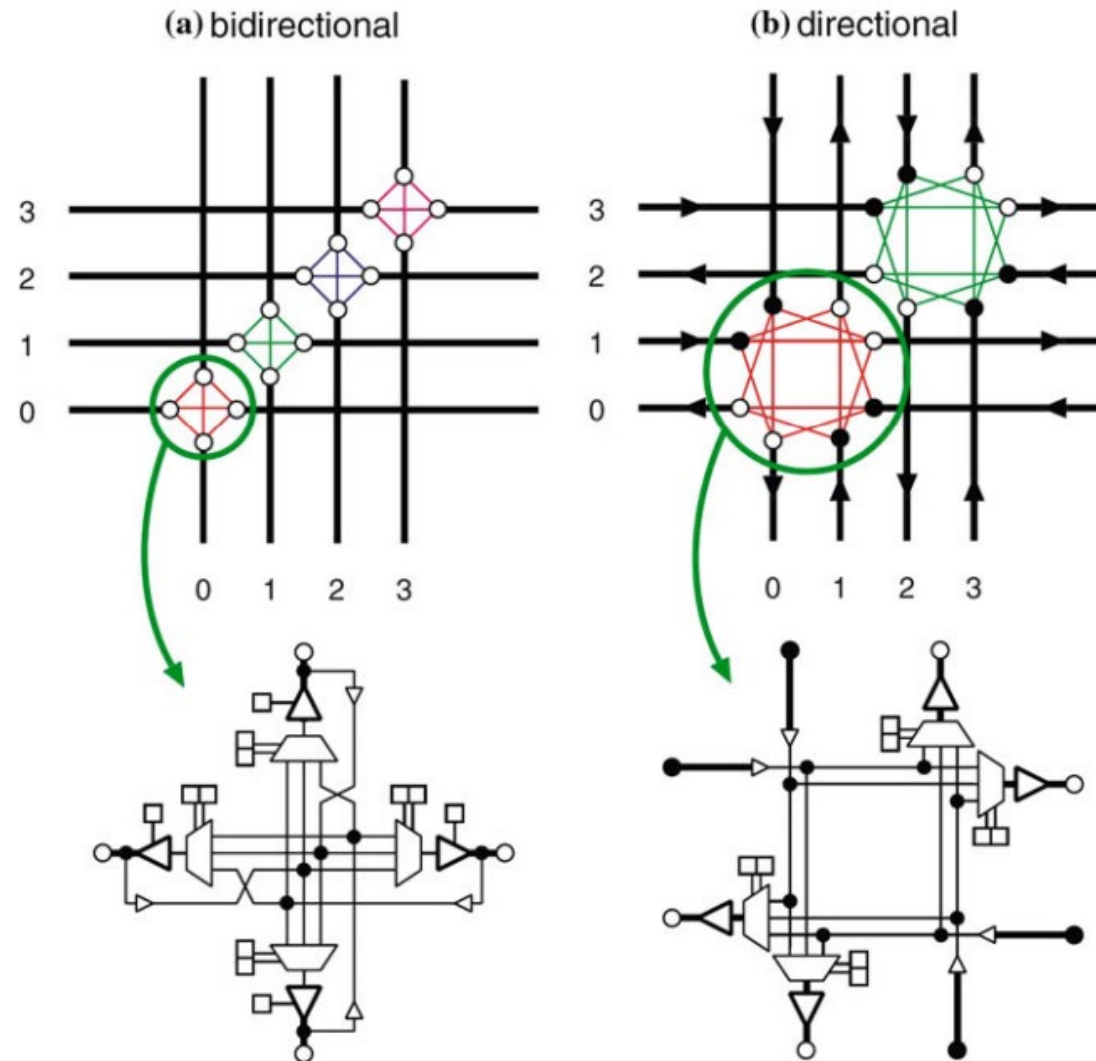

FPGA Technology Mapping

- Technology Mapping:
- ASIC – Cell Library (e.g., NAND, NOT, FF)
- FPGA – fixed architecture
 - LUT
 - DSP
 - RAM/ROM
- In FPGA:
 - Gate level design → LUTs
 - Multiplier/MAC → DSP
 - Memory/Large Registers → RAM/ROM



LUT Mapping

Look Up Table

2^k SRAM bits

A k-LUT can implement any Boolean function having k-variable,

$B: 2^k \rightarrow \{0,1\}$

  


2 inputs LUTs

$$F = ab + a'b'$$

| a | b | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

LUT Mapping

 

Introduction to logic transformations

- There are various methods of logic transformations. The methods are as follows:
 1. Factoring
 2. Decomposition
 3. Extraction
 4. Substitution
 5. Elimination.

Factoring

- A *factored form* is a recursive sum-of products representation in which the products themselves can consist of a sum of products
- In factoring, an expression in sum-of-products form is converted into an expression with multiple levels without introducing any sub-functions.

Example Consider the following sum-of-products expression:

$$f = uvxz + wxz + u'y'z + v'x'z' + v'y'z'.$$

One way to factor it is shown below:

$$f = z(x(uv + w) + u'y') + (x' + y)v'z'.$$

Factoring cont'd...

- The above expressions can be represented by logic network graphs
- the multi-level circuit has six levels of logic.

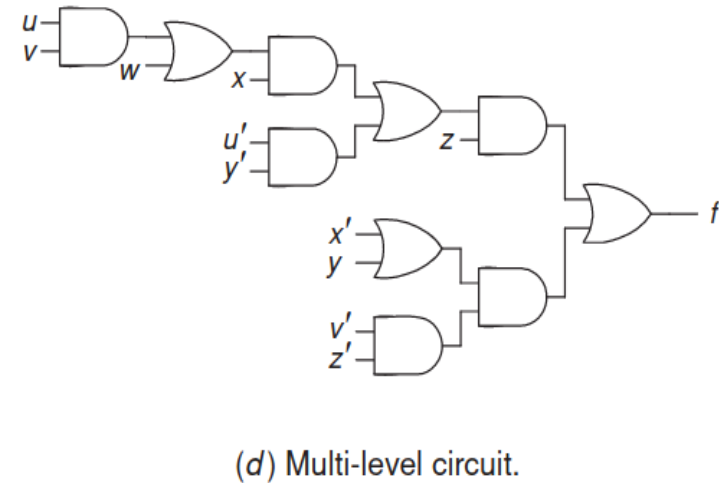
 
 
 


Fig. 6.1 Network graphs and corresponding circuits.

Factoring cont'd...


- Factoring makes expression more compact.
- The minimal sum-of-products expression has 16 literals whereas its factored form has only 11 literals.
- The number of transistors in the complex CMOS-gate implementation of an expression is twice its literal-count.
- As the number of literal in the expression increases, the implementation complexity of the expression also get increases.
- Literal count is good measure of implementation complexity.

Decomposition


- In decomposition, a factored switching expression is replaced with a set of new expressions.

 Example Consider the factored expression in Eq. (6.2). It can be decomposed as follows:

$$\begin{aligned} f_1 &= uv + w, & f_2 &= x' + y, \\ f_3 &= v'z', & f_4 &= xf_1 + u'y', \\ f &= f_2f_3 + zf_4. \end{aligned}$$



(a) Network graph for sum of products.

 


(b) Network graph for factored expression.

Decomposition cont'd...

- Decomposition replaces subexpression in the expression by set of functions. These functions are said to be implemented separately.
- The literal-count after the decomposition is the sum of the literal-counts for each function. Thus, the literal count is now 15.
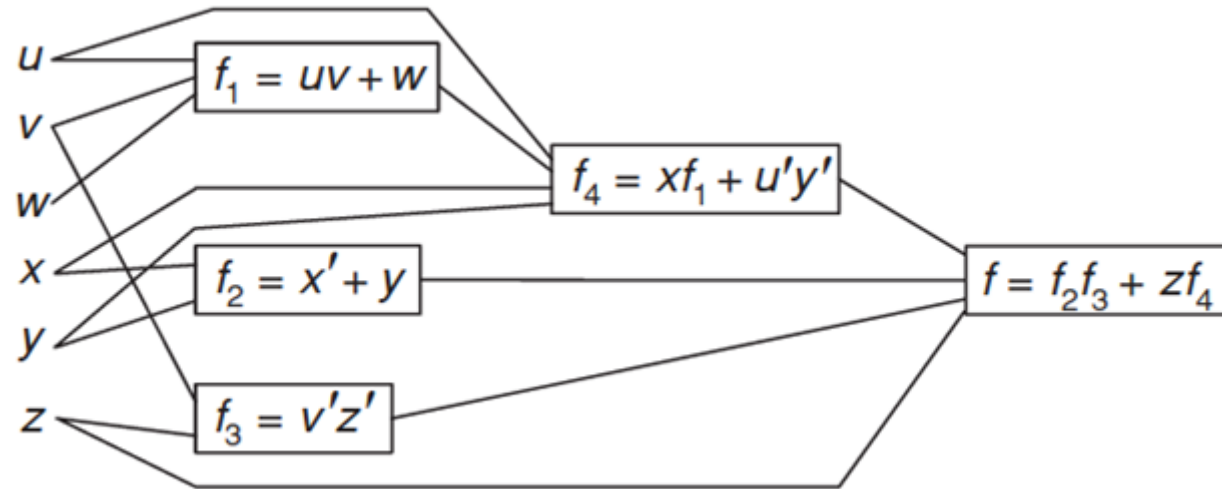
$$\begin{aligned}f_1 &= uv + w, & f_2 &= x' + y, \\f_3 &= v'z', & f_4 &= xf_1 + u'y', \\f &= f_2f_3 + zf_4.\end{aligned}$$



Extraction

- Extraction is the process of extracting common sub-expressions (CSE) from two or more expressions in factored form.
- If there is CSE between two or more expressions, then we replace CSE by a new function.

Example Consider the expressions for f_1 and f_2 below:

$$f_1 = (uv + w)x + u'y',$$


$$f_2 = (uv + w)z.$$

After extracting the subexpression $uv + w$ from the two expressions, we get the following expressions:


$$\begin{aligned} f_1 &= f_3x + u'y', & f_2 &= f_3z, \\ f_3 &= uv + w. \end{aligned}$$

Extraction Cont'd...

 - The literal count reduces from 10 to 9.



(a) Network graph before extraction.

 

(b) Network graph after extraction.

Fig. 6.3 Network graphs depicting extraction.

Substitution

- Substitution is the process of replacing a subexpression in an expression f with a variable g corresponding to a node in a network graph. In other words, g is substituted into f is expressed in terms of g .

Example Consider f_1 and f_2 below:

$$f_1 = uvx + wx + u'y',$$
$$f_2 = uv + w.$$

The expression f_1 can be given in terms of f_2 as $f_2x + u'y'$. Thus, f_2 has been substituted into f_1 . Figure 6.4 shows the network graphs for this example.

 


Fig. 6.4 Network graphs depicting substitution.

Elimination

- Elimination removes internal nodes from the network graph.
- It becomes possible if the corresponding expression replaces the variable corresponding to that node. Whenever the elimination step reduces the literal-count, it may be useful to employ it.

Example: Consider $f_1 = x + f_2$ and $f_2 = y + z$. If f_2 is not needed elsewhere in the network then it can be eliminated in the expression for f_1 by replacing it with $y + z$, thus obtaining $f_1 = x + y + z$. This reduces the literal-count from four to three.

Approach

- In multi-level logic synthesis, the above five logic transformations are applied to an initial logic network iteratively until no more improvement is possible in the targeted objective
 - They need not be applied in the given order
- Synthesis objectives are optimization of area, delay, or power.

Example

$$p = ce + de$$

$$q = a + b$$

$$r = p + a'$$

$$s = r + b'$$

$$t = ac + ad + bc + bd + e$$

$$u = q'c + qc' + qc$$


$$v = a'd + bd + c'd + ae'$$

$$w = v$$

$$x = s$$

$$y = t$$

$$z = u$$

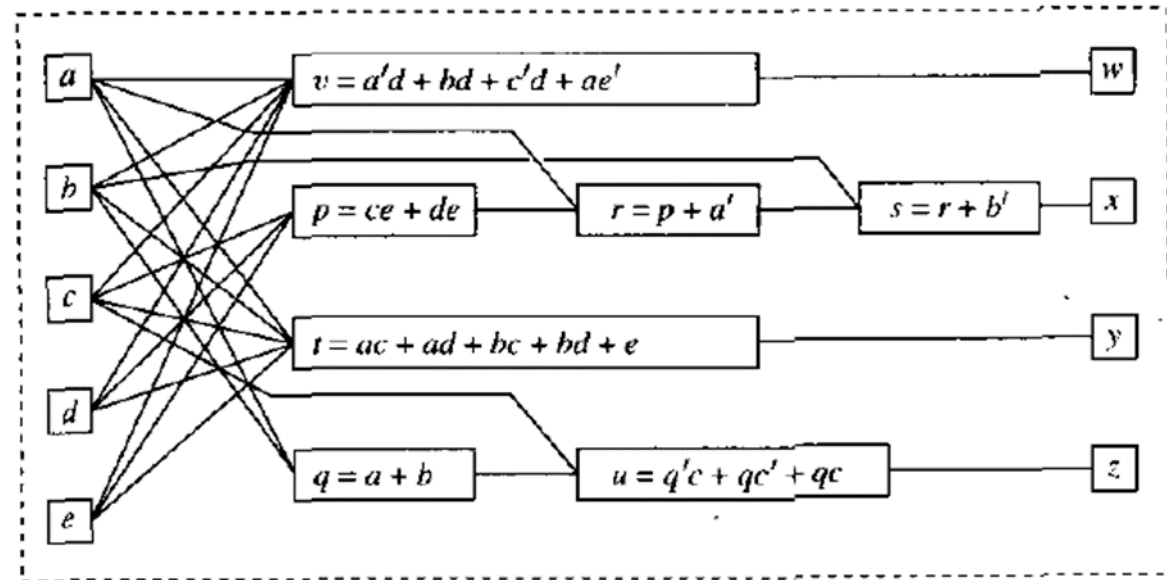

$$p = ce + de$$

$$q = a + b$$

$$r = p + a'$$

$$s = r + b'$$

$$t = ac + ad + bc + bd + e$$

$$u = q'c + qc' + qc$$

$$v = a'd + bd + c'd + ae'$$

$$w = v$$

$$x = s$$

$$y = t$$

$$z = u$$

$$j = a' + b + c'$$

$$k = c + d$$

$$q = a + b$$

$$s = ke + a' + b'$$

$$t = kq + e$$

$$u = q + c$$

$$v = jd + ae'$$

$$w = v$$

$$x = s$$

$$y = t$$

$$z = u$$

