

**CS221: Digital Design**

# **RTL Design using ASM**

A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

**Example:**

**Design a Digital Circuit to Sum of First  
N odd numbers**

It is  $N^2$  but we want to use basic  
summation method  $1+3+5+7..+(2n-1)$

# Sum of First N odd numbers

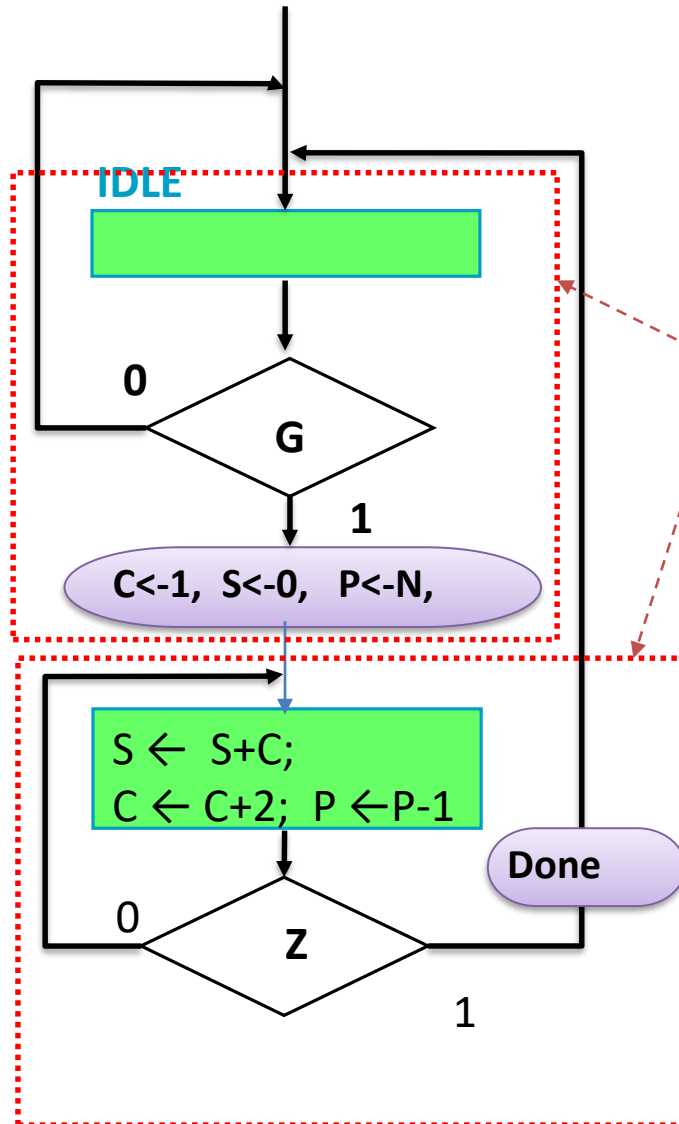


ASM  
Block

Require : two adders,  
decrement register, S reg, C reg


In state : We can put RTL like  
statement

$$\begin{aligned} S &\leftarrow S + C, & C &\leftarrow C + 2, & P &\leftarrow P - 1 \\ C &\leftarrow 1, & S &\leftarrow 0, & P &\leftarrow N \end{aligned}$$

# DP: Sum of First N odd numbers

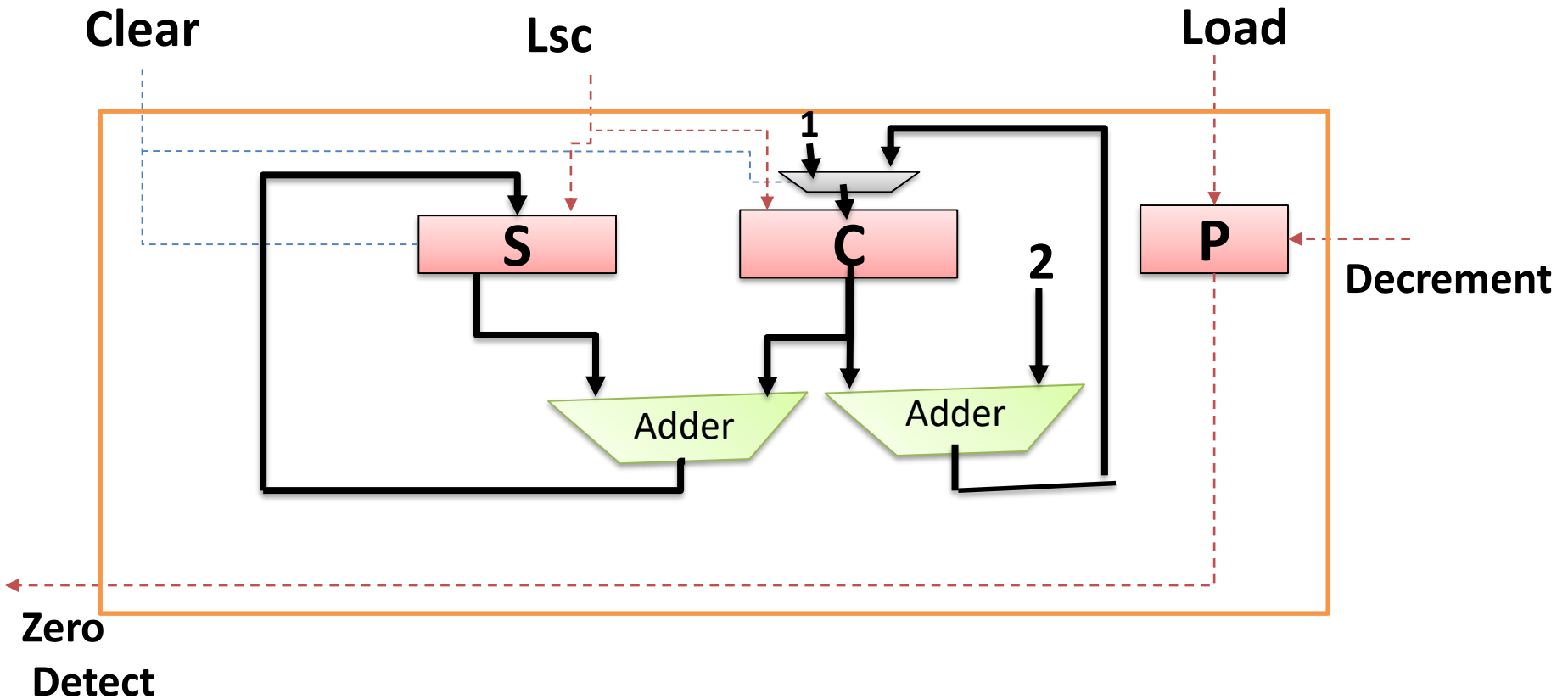


# CP: Sum of First N odd numbers

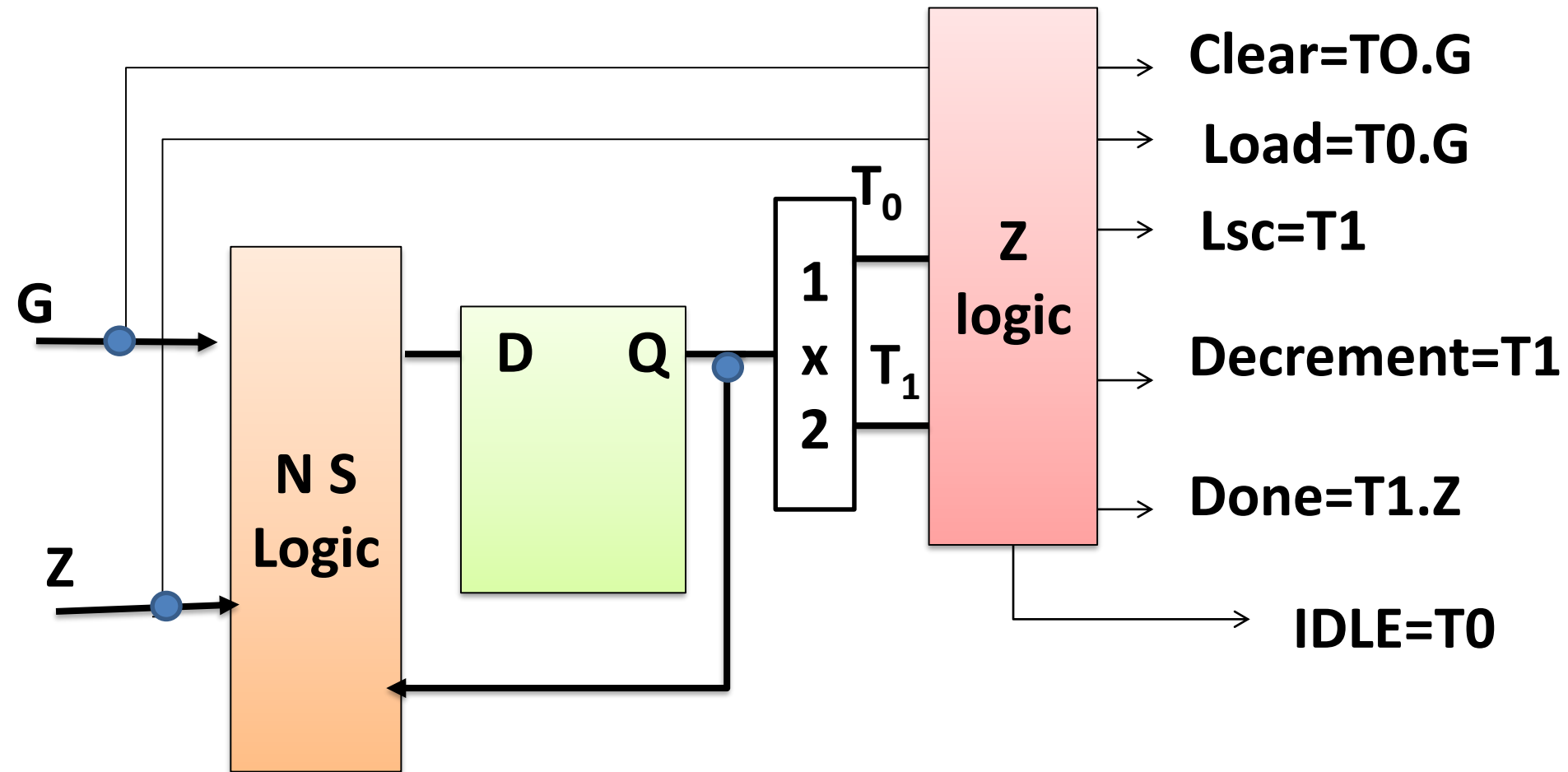

$$D = T_0.G + T_1.Z'$$

# CP+DP: Sum of First N odd numbers

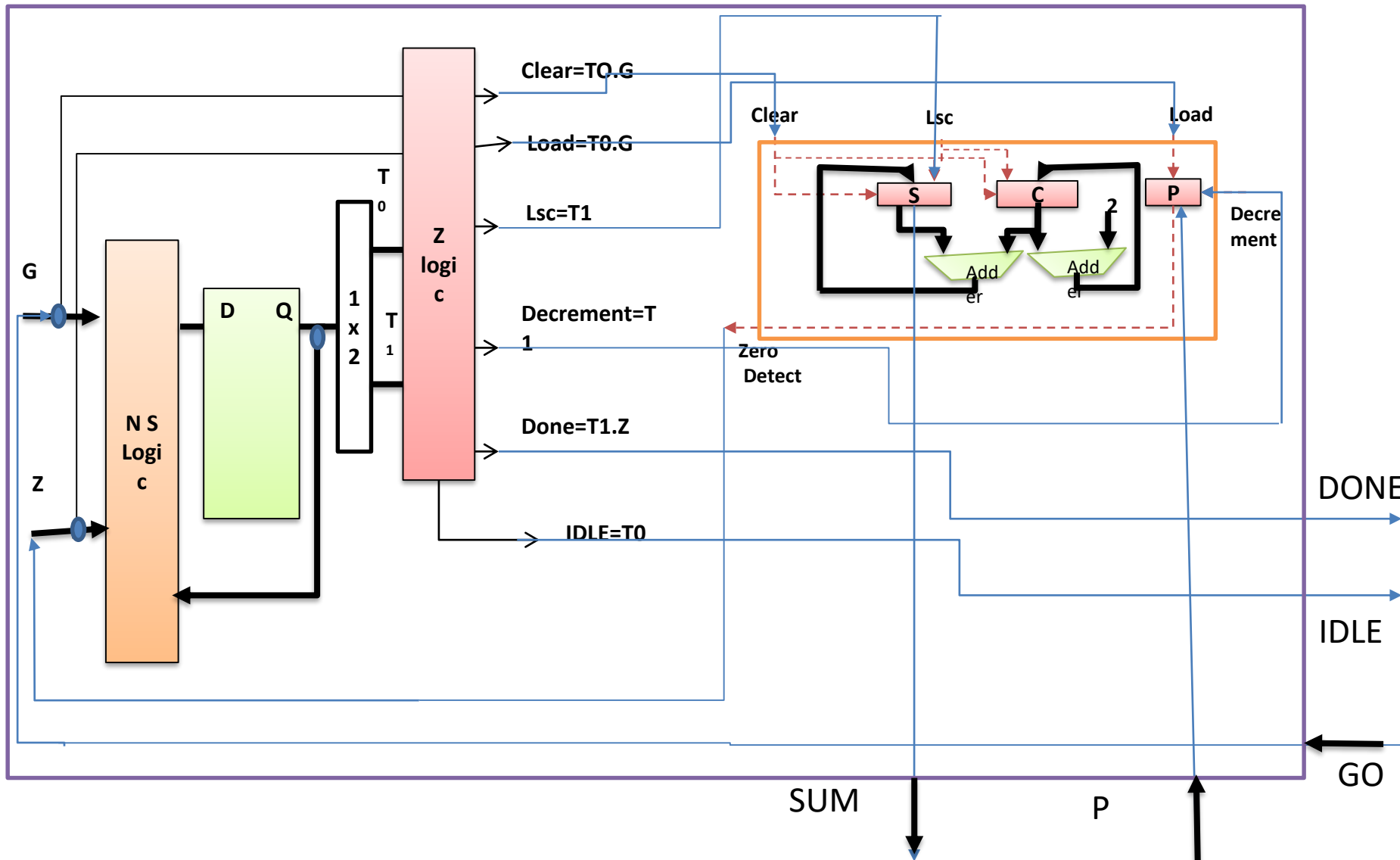


**Another Example**

# ASM Design Example

- Find the ASM chart corresponding to the following description
  - There are two states A, B
  - If in state A and input X is `0' then the next state is A
  - If in state A and input X is `1' then the next state is B
  - If in state B and input Y is `1' then the next state is B
  - If in state B and input Y is `0' then the next state is A
  - Output Z is equal to `1' while the circuit is in state B
- Solution:
  - Total States  $\rightarrow 2$
  - Two Inputs  $\rightarrow X, Y$
  - One Output  $\rightarrow Z$




# ASM Design Example

 



**Another Example**

# Another Example: From FSM to ASM

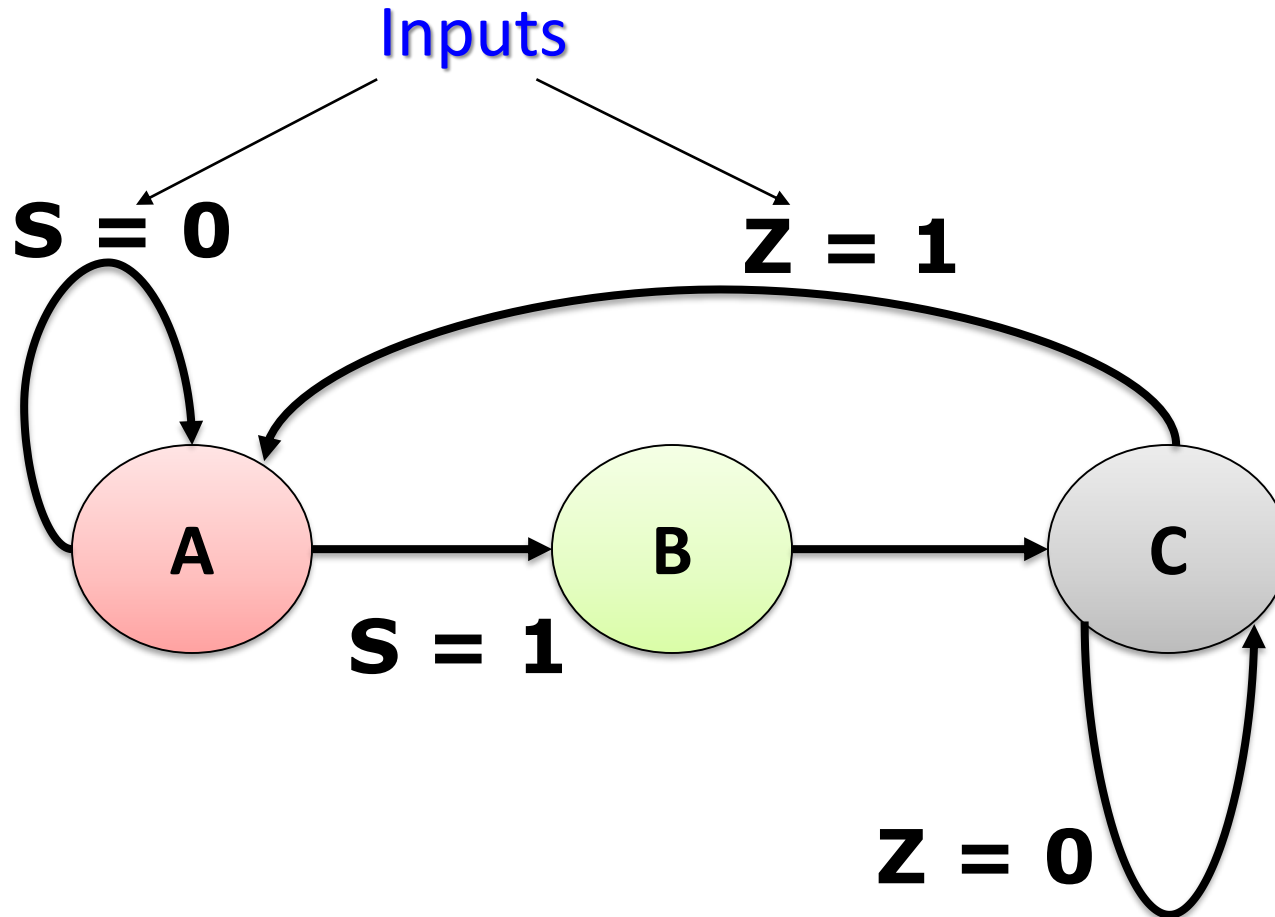

Similar to the ASM of : Sum of First N odd numbers


# Another Example: From FSM to ASM

  

**ASM Block**


# ASM Blocks

One ASM block  
execute in one  
cycle

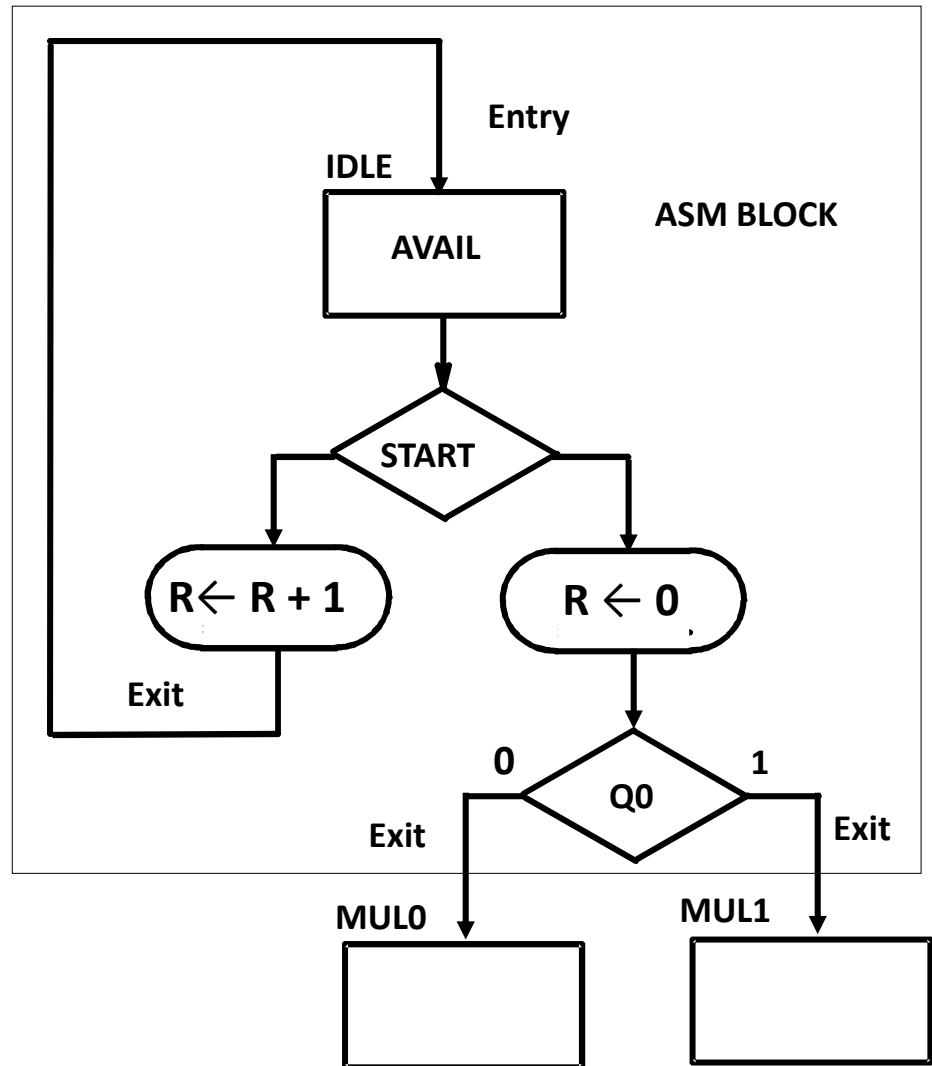
 
# ASM Timing

- Outputs appear while in the state
- Register transfers occur at the clock while exiting the state - New value occur in the next state!



**Another Example**



# ASM : DP+CP Example

- Find the Data Path and ASM for the following problem:
  - We **first** need to load two registers (R1, R2) with some value.
  - We will **then** need to add the two Registers (R1, R2) and save the result in Register R3.
  - All these operations **should occur if** a “**start**” Signal is activated.


# ASM : DP+CP Example

- Translation to Hardware:
  - We need to clear the registers first.
  - If the “**start**” signal is set to 0, I do nothing
  - Else If the “**start**” signal is set to 1, I will load R1, R2 with values
  - Next, enable R3 to be loaded (load-2) by the results of  $R1+R2$


# ASM : DP+CP Example

- Inputs/Outputs:
  - **start** is an input signal (Use a switch)
  - **clear** is an output signal generated and connected to R1, R2, R3
  - **load-1** is an output signal generated and connected to R1, R2
  - **load-2** is an output signal generated and connected to R3

# Data Path

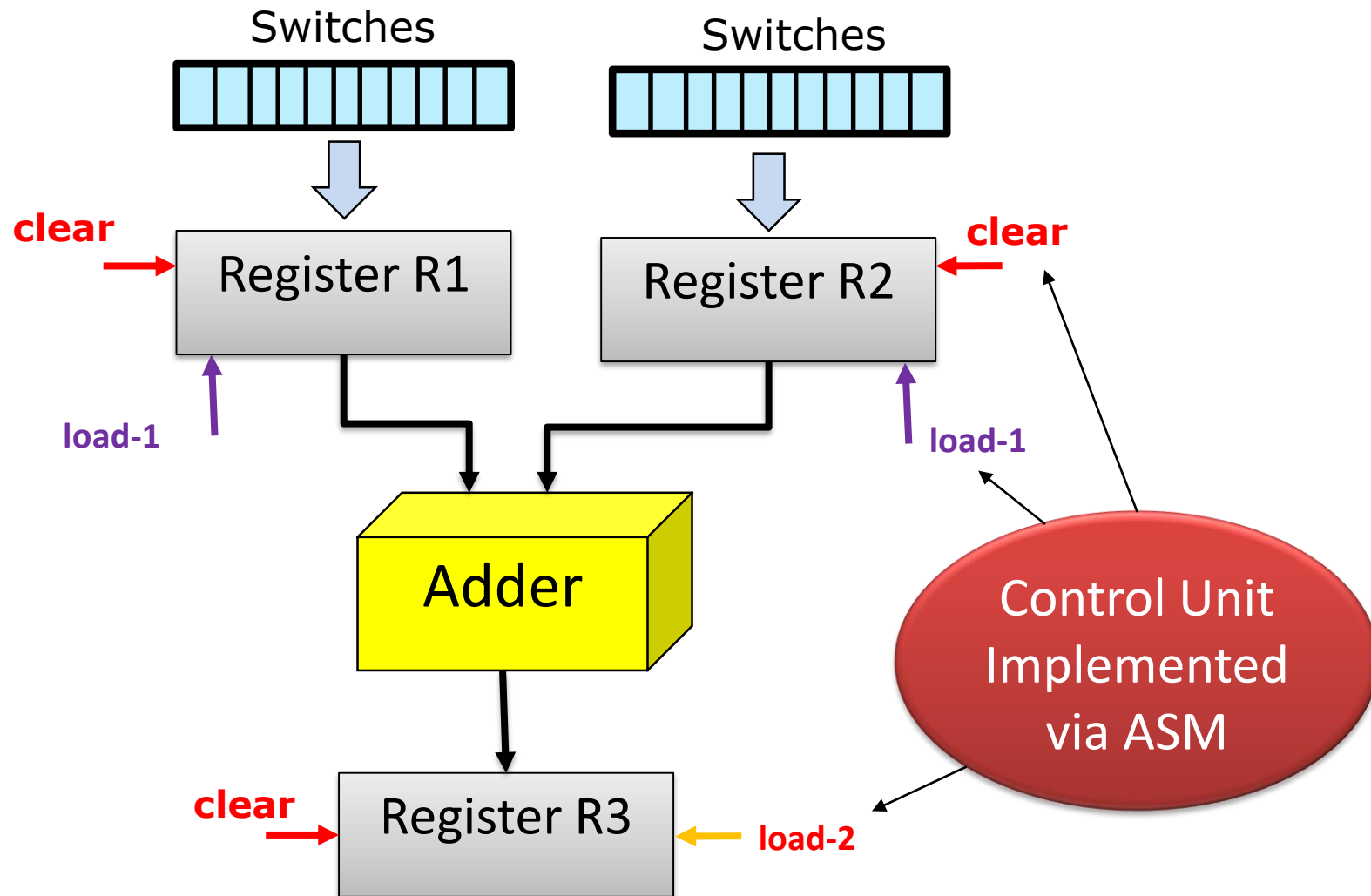

# ASM : DP+CP Example

 

# ASM : DP+CP Example

## Controller

PS		S	NS	
0	0	0	0	0
0	0	1	0	1
0	1	X	1	0
1	0	X	0	0
1	1	X	0	0

PS		CLR	L1	L2
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	X	X	X

$$D1 = Q1'.Q0 \quad D2 = S.Q1'.Q0'$$

$$CLR = Q1'.Q0' \quad L1 = Q0'.Q1 \quad L2 = Q1.Q0'$$

# Data Path

