

# Combinational Logic Design

Dr. Chandan Karfa  
CSE IIT Guwahati

- Code conversion
- Parity bit generator
- Comparator
- Multiplexer

# Source

- Chapter 4: M. M. Mano and M. D. Ciletti, Digital Design, 5th Ed., Pearson Education.
- Chapter 5: Z. Kohavi and N. Jha, Switching and Finite Automata Theory, 3rd Ed., Cambridge University Press, 2010.

# Basic

- The number of gate inputs that can be driven by the output of a single gate is limited. The maximum such number is called the **fanout** of the gate.
- The bound on the number of inputs that a single gate may have is referred to as the **fanin** of the gate.
- A finite amount of time is required to propagate a signal through a gate, or to switch a gate output from one value to another is known as the **propagation delay**.

# Logic design with integrated circuits

Integrated circuits are produced in packages, or chips, and are historically classified into four categories:

- 1. Small-scale integration (SSI)** usually refers to packages containing single gates, e.g., AND, OR, NOT, NAND, NOR, XOR, or small packages containing two or four gates of the same type.
- 2. Medium-scale integration (MSI)** refers to intermediate packages containing up to about 100 gates. They usually realize standard circuits that are used often in logic design, e.g., code converters, adders, etc.
- 3. Large-scale integration (LSI)**, may contain many hundreds or thousands of gates in a single package. Some LSI circuits are standard, e.g., subsystems for computer control or for a computer arithmetic unit, while other LSI circuits are manufactured to the specification of the logic designer.
- 4. Very-large-scale integration (VLSI)** is what we currently observe, in chips in which there may be millions of gates.

# ANALYSIS OF COMBINATIONAL CIRCUITS


A combinational circuit is analyzed by tracing the output of each gate, starting from the circuit inputs and continuing toward each circuit output.

The output, designated  $C_0$ , is given by

$$C_0 = AB + (A + B)C = AB + AC + BC$$

The second output, designated  $S$ , is found to be
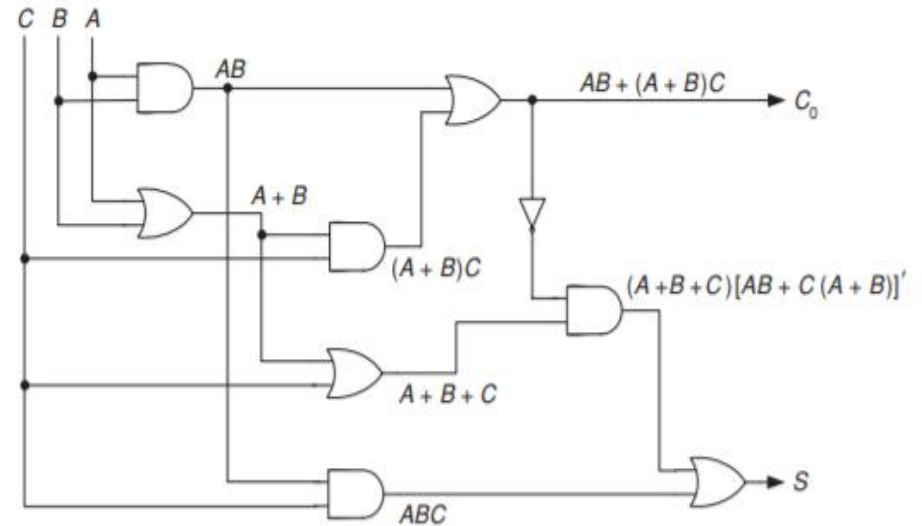
$$\begin{aligned} S &= (A + B + C)[AB + (A + B)C]' + ABC \\ &= (A + B + C)(A' + B')(A' + C')(B' + C') + ABC \\ &= AB'C' + A'BC' + A'B'C + ABC \\ &= A \oplus B \oplus C \end{aligned}$$



# Design Procedure

- From the specifications of the circuit, determine the required number of inputs and outputs and assign a symbol to each.
- Derive the truth table that defines the required relationship between inputs and outputs.
- Obtain the simplified Boolean functions for each output as a function of the input variables.
- Draw the logic diagram and verify the correctness of the design (manually or by simulation).

# Code Conversion Example : BCD to Excess-3

Truth Table for Code Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0





$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$$


$$= B'(C + D) + B(C + D)'$$

$$w = A + BC + BD = A + B(C + D)$$

    



# Code Conversion Example

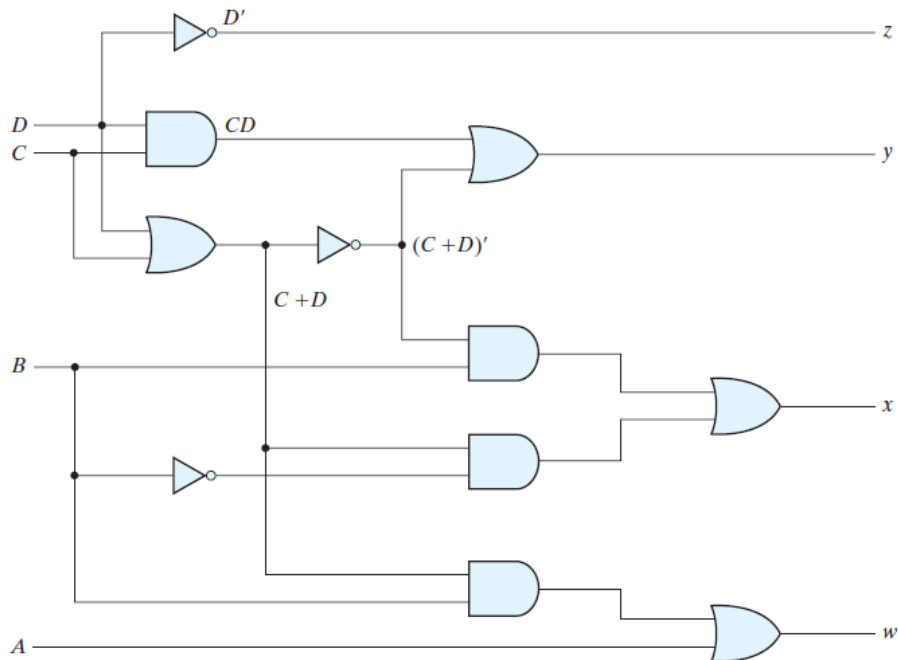

$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$$

$$= B'(C + D) + B(C + D)'$$


$$w = A + BC + BD = A + B(C + D)$$

# Parity-bit generator

- Produce an output value 1 if and only if **an odd number of its inputs have the value 1**.
- $p = x'y'z + x'yz' + xy'z' + xyz$ .

$xy \backslash z$					
		00	01	11	10
$z$	0	0	1	0	1
	1	1	0	1	0

(a) Map.

 

(b) Implementation.

# COMPARATORS

An **n-bit comparator** is a circuit that compares the magnitude of two numbers X and Y . It has three outputs  $f_1$ ,  $f_2$ , and  $f_3$ , such that:

$f_1 = 1$  iff (if and only if )  $X > Y$ ;


$f_2 = 1$  iff  $X = Y$ ;

$f_3 = 1$  iff  $X < Y$ .

$$\begin{aligned} f_1 &= x_1x_2y_2' + x_2y_1'y_2' + x_1y_1' \\ &= (x_1 + y_1')x_2y_2' + x_1y_1', \end{aligned}$$


$$\begin{aligned} f_2 &= x_1'x_2'y_1'y_2' + x_1'x_2y_1'y_2 + x_1x_2'y_1y_2' + x_1x_2y_1y_2 \\ &= x_1'y_1'(x_2'y_2' + x_2y_2) + x_1y_1(x_2'y_2' + x_2y_2) \\ &= (x_1'y_1' + x_1y_1)(x_2'y_2' + x_2y_2), \end{aligned}$$
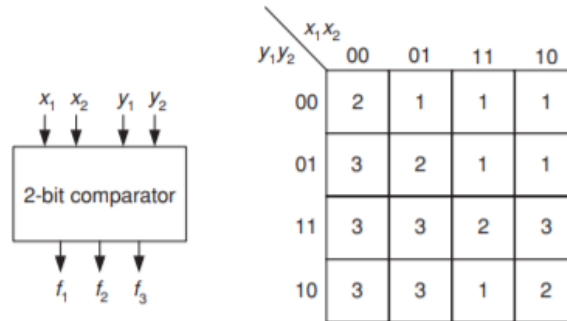
$$\begin{aligned} f_3 &= x_2'y_1y_2 + x_1'x_2'y_2 + x_1'y_1 \\ &= x_2'y_2(y_1 + x_1') + x_1'y_1. \end{aligned}$$



(a) Block diagram.

 (b) Map for  $f_1$ ,  $f_2$ , and  $f_3$ .



(c) Circuit for  $f_1$ .

2 bits comparator

# 4 bits Comparator

$A > B, A = B, \text{ or } A < B.$

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

The two numbers are equal if all pairs of significant digits are equal:  $A_3 = B_3, A_2 = B_2, A_1 = B_1,$  and  $A_0 = B_0.$

$$x_i = A_i B_i + A'_i B'_i \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$

A is greater or less than B, we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position. If the two digits of a pair are equal, we compare the next lower significant pair of digits. The comparison continues until a pair of unequal digits is reached. If the corresponding digit of A is 1 and that of B is 0, we conclude that  $A > B.$  If the corresponding digit of A is 0 and that of B is 1, we have  $A < B$

$$(A > B) = A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$$

$$(A < B) = A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$$


# 4 bits Comparator

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3$$


$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

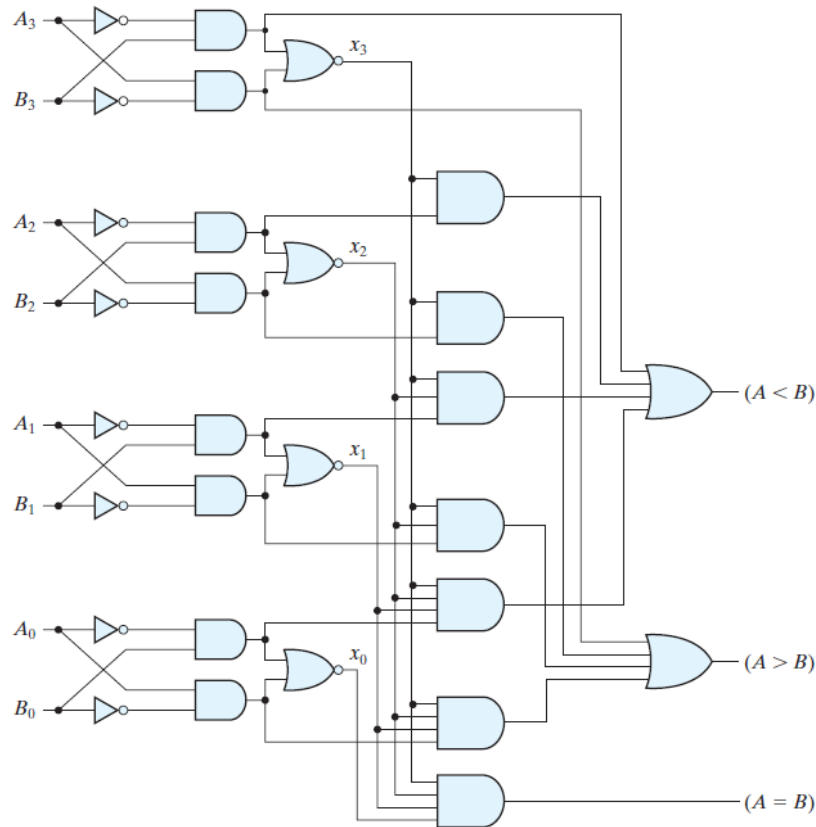
$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0'$$



# 12-bits Comparator

 

(a) A 4-bit comparator.

 


(b) A 12-bit comparator.

Initial conditions are inserted at the inputs of the comparator corresponding to the least significant bits in such a way that the outputs of this comparator will depend only on the values of its own  $x$ 's and  $y$ 's


# Data selectors/Multiplexers

- Multiplexer is an electronic switch that can **connect one out of n inputs to the output**.
- A data selector has n data input lines  $D_0, D_1, \dots, D_{n-1}$ , m select digit inputs  $s_0, s_1, \dots, s_{m-1}$ , and one output.
- The m select digits form a binary select number ranging from 0 to  $2^m - 1$ , and when this number has the value k then  $D_k$  is connected to the output.
- The number of select digits must equal  $m = \log_2 n$ , so that it can identify all the data inputs.

# 2-to-1 Multiplexer

 


(a) Logic diagram

 

(b) Block diagram



# 4-to-1 Multiplexer

 

(a) Logic diagram


$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table
 
# Implementing switching functions with data selectors


- Implementing of the arbitrary switching functions is an important application of data selectors.
- For example: we show how functions of two variables can be implemented by data selector

$$\begin{aligned} \text{if } s=0, \text{ then } z &= D_0 \\ \text{if } s=1, \text{ then } z &= D_1 \\ z &= sD_1 + s'D_0. \end{aligned}$$



- Implementation of EXCLUSIVE-OR operation  $A \oplus B$ ,  $s=A$ ,  $D_1=B'$ ,  $D_0=B$   
 $z = AB' + A'B = A \oplus B$
- Similarly, NAND operation  $z = A' + B'$ .  $S=A$ ,  $D_1=B'$ ,  $D_0=1$
- Any logic gate can be realized using a 2-to-1 MUX
 
# Implementing two variable function with data selector



$$z = sD_1 + s'D_0.$$

If  $s = A$ ,  $B = D_0$ , and  $B' = D_1$  then  $z = A \oplus B$ .

If  $s = A$ ,  $D_0 = 1$ , and  $D_1 = B'$  then  $z = A' + B'$ .

# Boolean Function Implementation


- Implementing a Boolean function of  $n$  variables with a multiplexer that has  $n - 1$  selection inputs.
- The first  $n - 1$  variables of the function are connected to the selection inputs of the multiplexer.
- The remaining single variable of the function is used for the  $2^{(n-1)}$  data inputs.
- If the single variable is denoted by  $z$ , each data input of the multiplexer will be  $z$ ,  $z'$ ,  $1$ , or  $0$

# Boolean Function Implementation

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

$x$	$y$	$z$	$F$	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 

(b) Multiplexer implementation

# Boolean Function Implementation

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

