

CS221: Digital Design


ASM/ FSMD/ RTL Design

A. Sahu


Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

Example 1: Draw ASM of D-FF

 


FSM

 


ASM

Example 2: Draw ASM of JK-FF

 


FSM

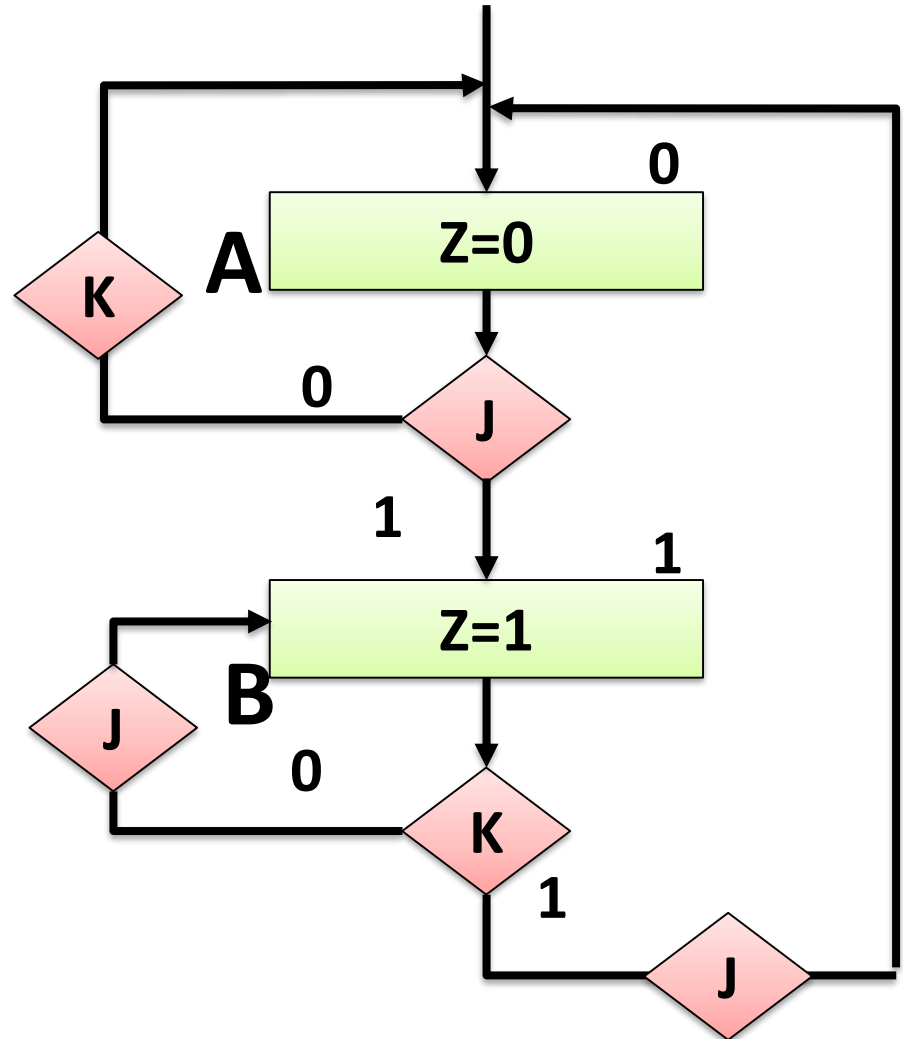

ASM

 
Moore FSM – Example 3: Sequence of two 1's




Moore FSM – Example 3: Sequence of two 1's

| Present state | Next state | | Output z |
|---------------|------------|---------|------------|
| | $w = 0$ | $w = 1$ | |
| A | A | B | 0 |
| B | A | C | 0 |
| C | A | C | 1 |

Example 3: ASM Chart for Moore FSM

 


FSM


 


ASM

 Mealy FSM –Example 4: Sequence of two 1's




ASM Chart for Mealy FSM – Example 4

  


ASM

ASM Chart : Example 5, mod 5 counter

 


FSM

 

ASM

ASM Chart : Example 6: 10 bit counter


FSM not
possible to
Draw/Tabulate

 


Require : addition, comparison data path
In state : We can put RTL like statement
 $C=C+1, X=COMPARE(C, 1023)$

Remember : Serial Addition

- Model S in terms of X, Y and Q (State)

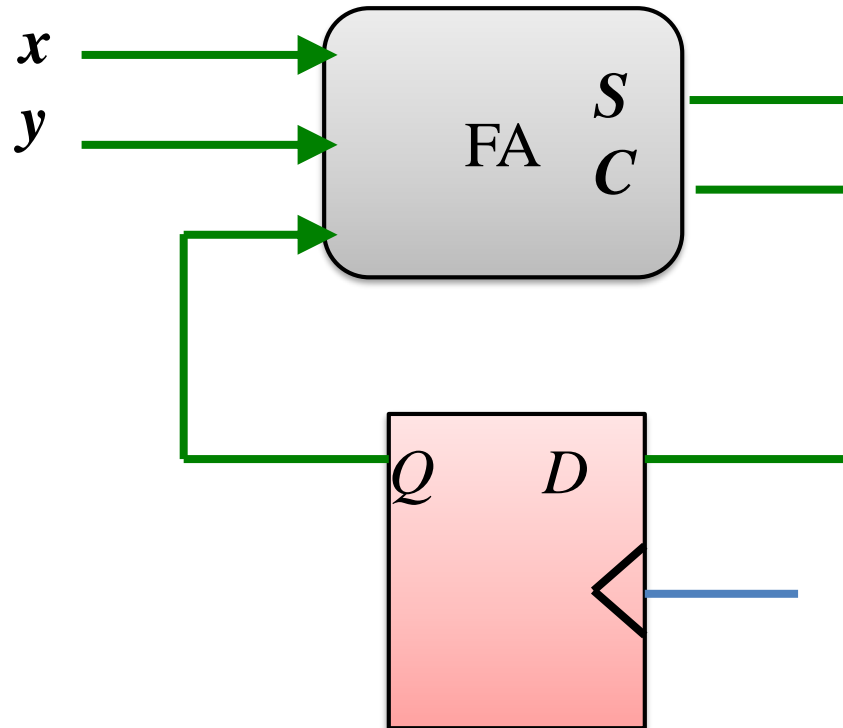


Mealy FSM for Binary Adder

 

FSM


ASM
Blocks

 

Mealy FSM for Binary Adder

- ASM Blocks
 - Two blocks in this example
- An ASM Block
 - Include a state and all its outgoing edges, condition boxes and conditional state boxes
 - All the parts of an ASM block execute in one cycle

ASM
Blocks

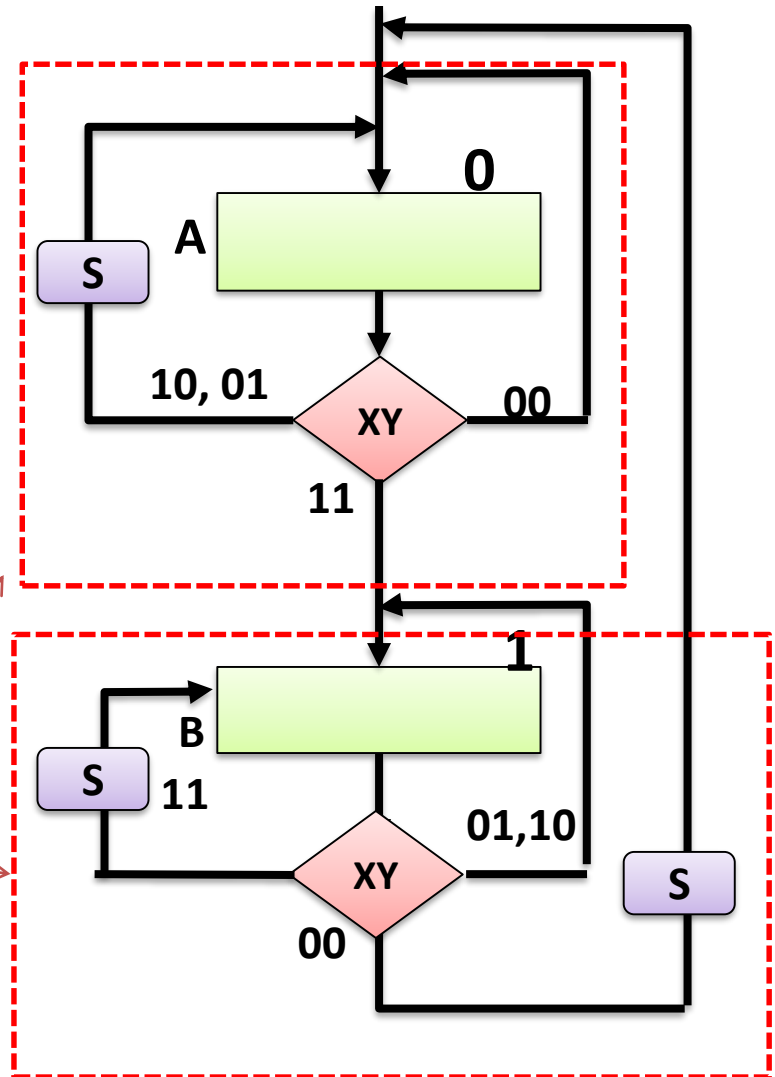

Mealy FSM for Binary Adder

