

CS221: Digital Design

Flip Flops and Register

A. Sahu

Dept of Comp. Sc. & Engg.


Indian Institute of Technology Guwahati

Outline

- ✓ Latch Stabilizing RS latch : Level Sensitive
- ✓ Clocked Latch : Flip Flop- Edge Sensitive
 - Master Slave Latches
- RS, D, JK, T flip flops
- Characterization Table and Equation
 - RS, D, JK and T Flip flop
- Excitation Table and Equation
 - RS, D, JK and T Flip flop
- Registers, MF Register and Memory

Conventions

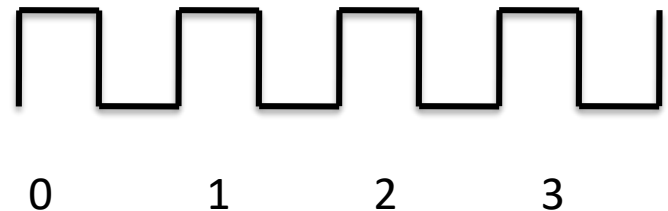
- The circuit is *set* means output = 1
- The circuit is *reset* means output = 0
- Flip-flops have two output Q and Q'
- Due to time related characteristic of the flip-flop:
 - Q_t or Q: present state
 - Q_{t+1} or Q^+ : next state



4 Type of Flip Flop

- **SR Flip Flop** : Set/Reset Flip Flop
- **D Flip Flop** : Data Flip Flop to store Bit
- **J-K Flip Flop**: Unavoidable SR=11 state to Toggle (All input values are useful)
 - The JK Flip Flop was named to honor "**Jack Kilby**" of Texas Instrument engineer who invented the concept of IC.
- **T Flip Flop**: Toggle Flip Flop

Master Slave J-K Flip Flop

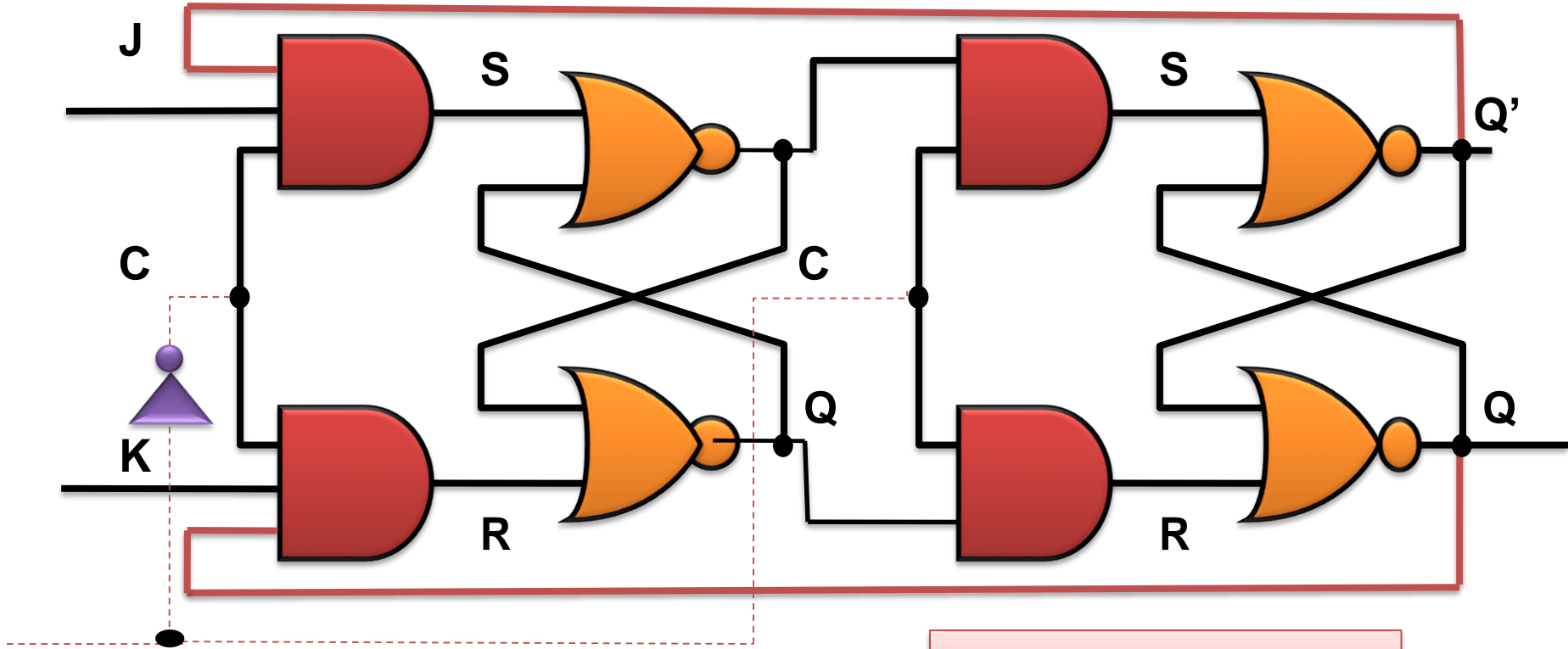

$$Q^+ = K'Q + JQ'$$

J-K Flipflop

J	K	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	Q _t '

$$\begin{aligned}Q^+ &= J'K'Q + JKQ' + JK' \\&= J'K'Q + JKQ' + JK'Q' + JK'Q \\&= J'K'Q + JK'Q' + JKQ' + JK'Q \\&= (J+J')K'Q + J(K+K')Q' \\&= (1)K'Q + J(1)Q'\end{aligned}$$

$$Q^+ = K'Q + JQ'$$

J-K Flip Flop

- To synthesize a D flip-flop, simply set K equal to the complement of J.
- **The JK flip-flop is a universal flip-flop**
 - Because it can be configured to work as any FF
 - T flip-flop or D flip-flop or SR flip-flop.



J=T	K=T	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	Q _t '

J=D	K=D'	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	Q _t '

J=S	K=R	Q+
0	0	Q _t
0	1	0
1	0	1
1	1	Q _t '

Toggle Flip-Flop: T FF

- $J=K=1$, $Q^+ = Q'$

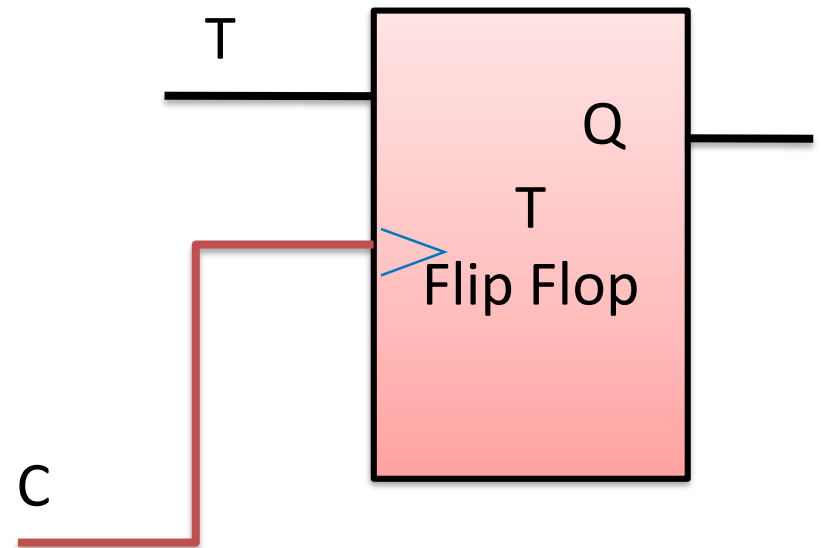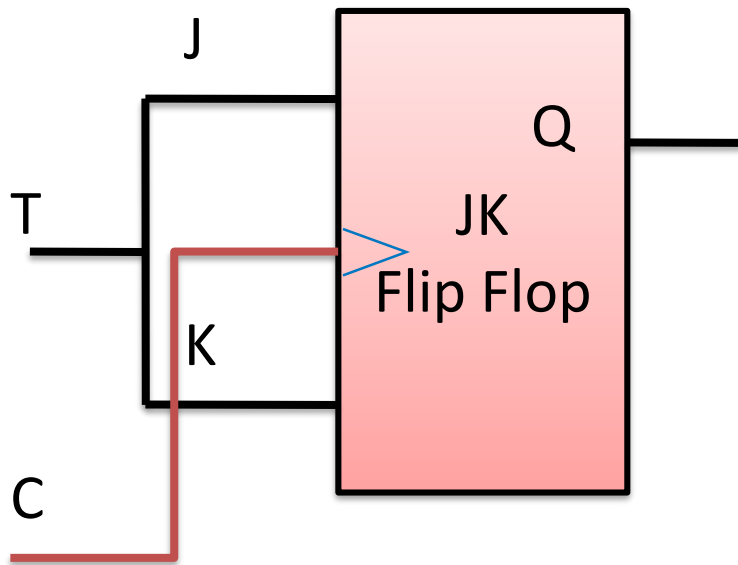

4 Types of Flip-Flops

S	R	Q+
0	0	Q_t
0	1	0
1	0	1
1	1	U



D	Q+
0	0
1	1

J	K	Q+
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'



T	Q+
0	Q_t
1	Q_t'

Characteristic Equations

- A descriptions of the next-state table of a flip-flop
- Constructing from the Karnaugh map for Q_{t+1} in terms of the present state and input

Characteristic tables

- The tables that we've made so far are called **characteristic tables**.
 - They show the next state $Q(t+1)$ in terms of the current state $Q(t)$ and the inputs.
 - For simplicity, the control input C is not usually listed.
 - Again, these tables don't indicate the positive edge-triggered behavior of the flip-flops that we'll be using.

J	K	Q+
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

D	Q+
0	0
1	1

T	Q+
0	Q_t
1	Q_t'

JK FF: Characteristic equations

- We can also write **characteristic equations**, where the next state $Q(t+1)$ is defined in terms of the current state $Q(t)$ and inputs.


J	K	Q+
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

$$\begin{aligned}Q^+ &= J'K'Q + JKQ' + \mathbf{JK'} \\&= J'K'Q + JKQ' + \mathbf{JK'Q'} + \mathbf{JK'Q} \\&= J'K'Q + \mathbf{JK'Q} + JKQ' + \mathbf{JK'Q'} \\&= (J+J')K'Q + J(K+K')Q' \\&= (\mathbf{1})K'Q + J(\mathbf{1})Q'\end{aligned}$$

$$\mathbf{Q^+ = K'Q + JQ'}$$

$$Q(t+1) = K'Q(t) + JQ'(t)$$

Given a D FF: Construct JK FF

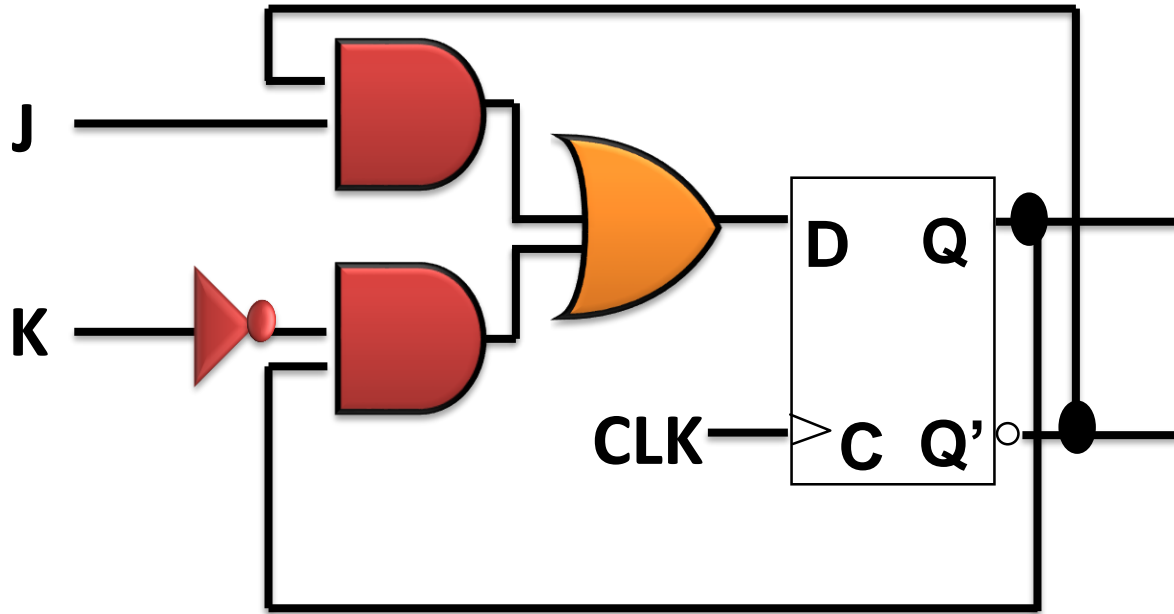

J	K	D	$K'Q + JQ'$
0	0	Q	$1Q + 0Q'$
0	1	0	$0Q + 0Q'$
1	0	1	$1Q + 1Q'$
1	1	Q'	$0Q + 1Q'$

$$D = K'Q + JQ'$$

D FF and T FF: Characteristic equations

- We can also write **characteristic equations**, where the next state $Q(t+1)$ is defined in terms of the current state $Q(t)$ and inputs.

D	Q+
0	0
1	1

$$Q^+ = D$$


$$Q(t+1) = D$$

T	Q+
0	Q_t
1	Q_t'

$$Q^+ = T'Q + TQ' = T \oplus Q$$

$$Q(t+1) = T'Q(t) + TQ'(t) = T \oplus Q(t)$$

Given a D FF: Construct T FF

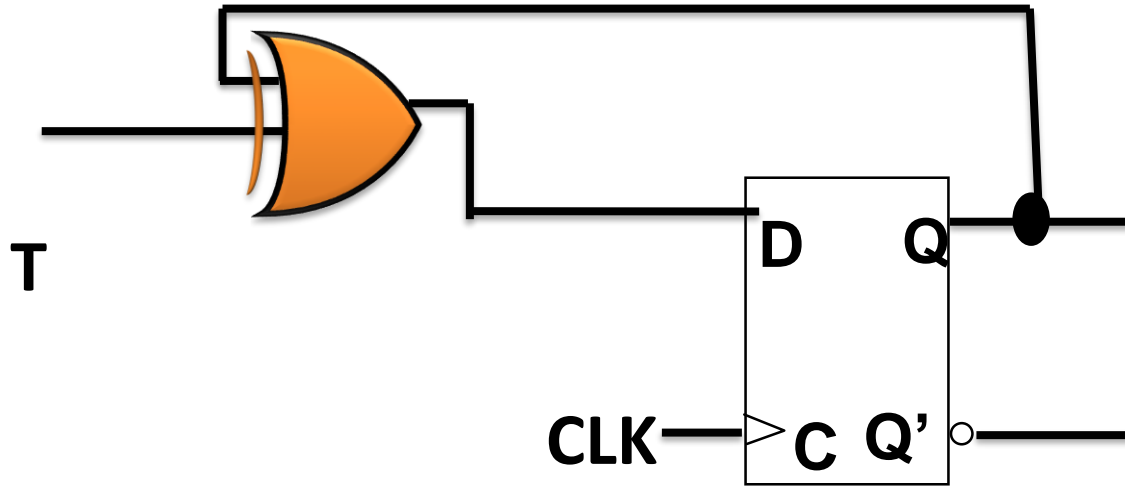

T	D	$TQ' + T'Q$
0	Q	$0Q' + 1Q$
1	Q'	$1Q' + 0Q$


$$D = TQ' + T'Q$$

RS FF: Characteristic equations

		SR			
		00	01	11	10
Q	0	0	0	—	1
	1	1	0	—	1

$$Q^+ = S + \bar{R}Q \quad (SR = 0)$$

Given a D FF: Construct RS FF

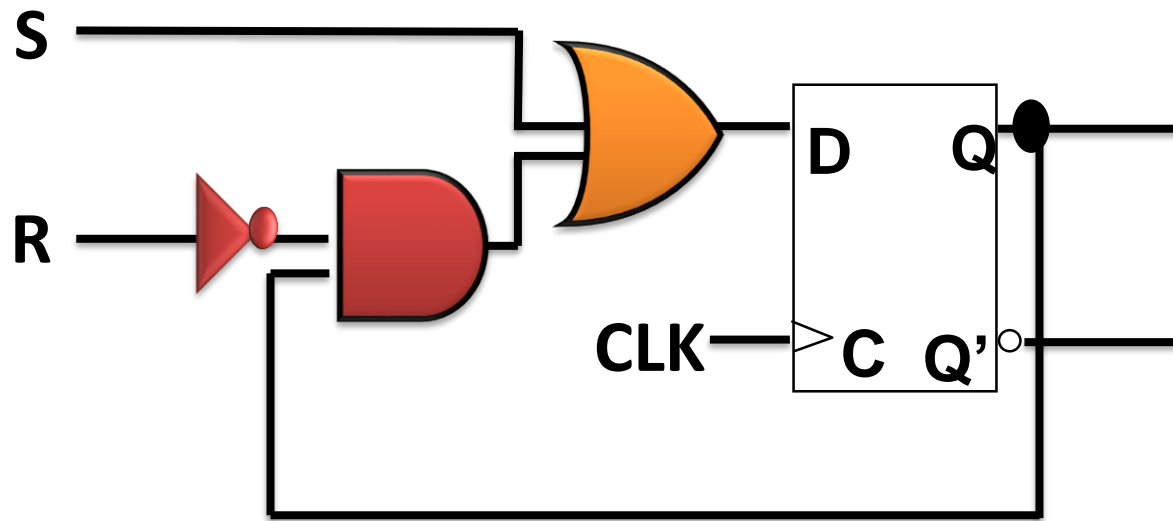

$$D = S + R'Q$$

S	R	D	$Q^+ = S + R'Q$ ($SR=0$)
0	0	Q	$1Q + 0Q'$
0	1	0	$0Q + 0Q'$
1	0	1	$1Q + 1Q'$
1	1	x	x

All FF: Characteristic equations

Flip Flop Type	Characteristic Equation
SR	$Q^+ = S + R'Q \quad (SR=0)$
JK	$Q^+ = JQ' + K'Q$
D	$Q^+ = D$
T	$Q^+ = TQ' + T'Q = T \oplus Q$

FF with Asynchronous Inputs


- S-R, D and J-K inputs are synchronous inputs
 - As data on these inputs are transferred to the flip-flop's output
 - Only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock
- Example:
 - *Preset (PRE) and clear (CLR)*
 - or *direct set (SD) and direct reset (RD)*

FF with Asynchronous Inputs

- When $PRE=HIGH$, Q is immediately set to HIGH.
- When $CLR=HIGH$, Q is immediately cleared to LOW.
- Flip-flop in normal operation mode when both PRE and CLR are LOW.

Asynchronous Inputs

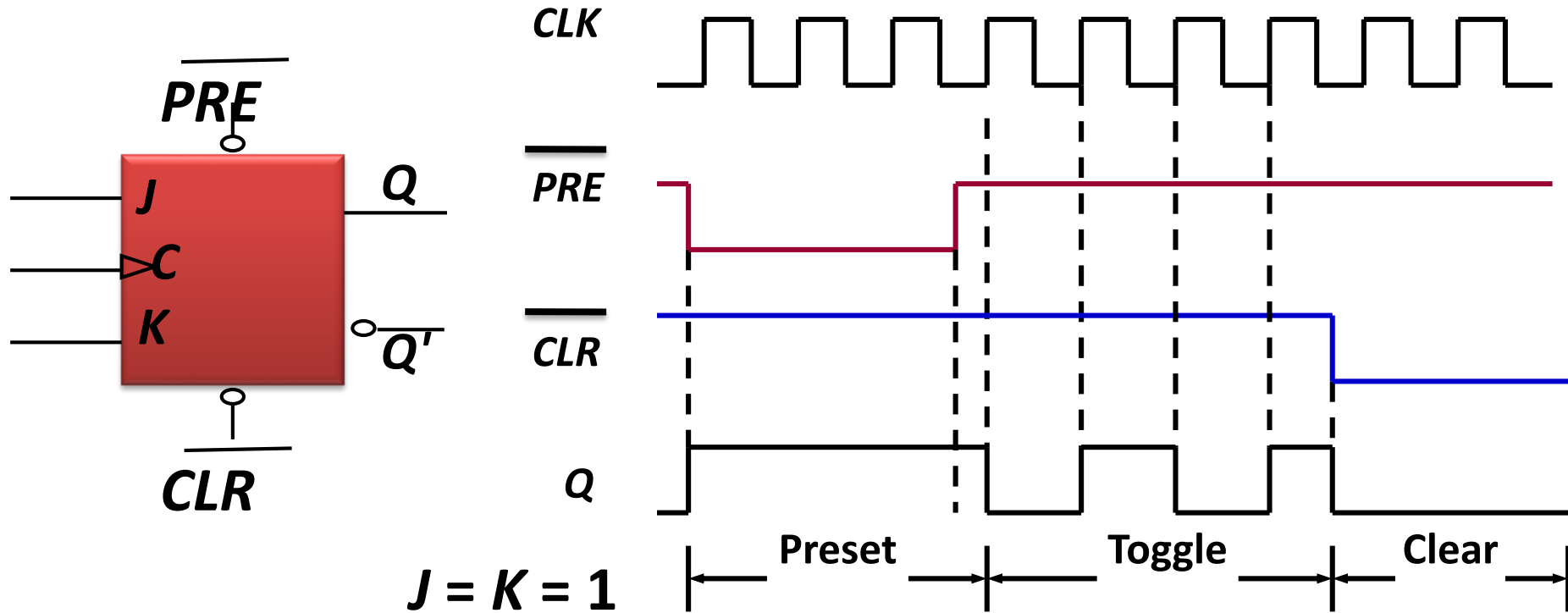- A J-K flip-flop with active-LOW preset and clear inputs.



Register

- D FF store one bit
- Register : Store multiple bit simultaneously

Register


- Register
 - Parallel Load, Parallel out : (PIPO)
 - Serial Load, Wrap around load, Serial out (SISO)
 - PISO, SIPO Register
- Multifunction Register : How to design?
- Memory Design using array of PIPO registers

Important point in register

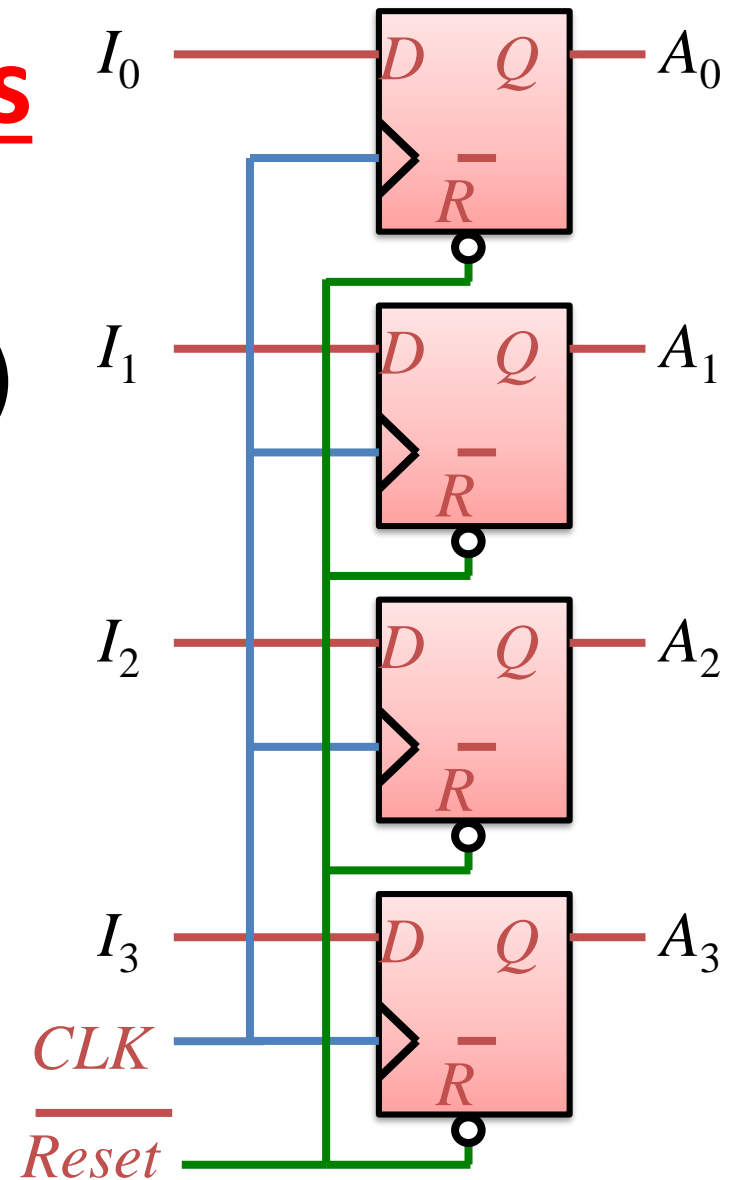
1. Input get reflected to output : Just before rising edges
2. Don't play with clock, it will add delay to clock and disturbed the other circuit
3. Use Mux for multiple inputs to D-FF of registers

Registers


- Group of D Flip-Flops
- **Synchronized (Single Clock)**
- Store Data



Registers

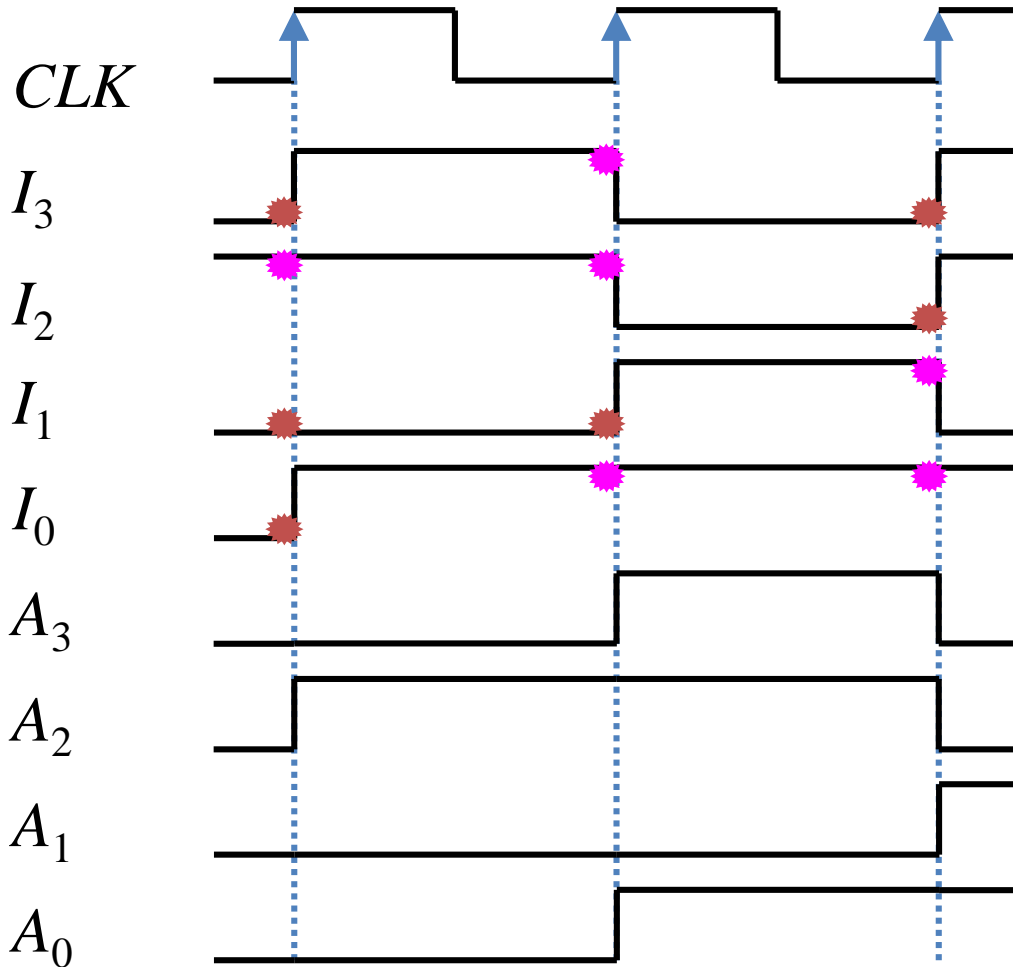

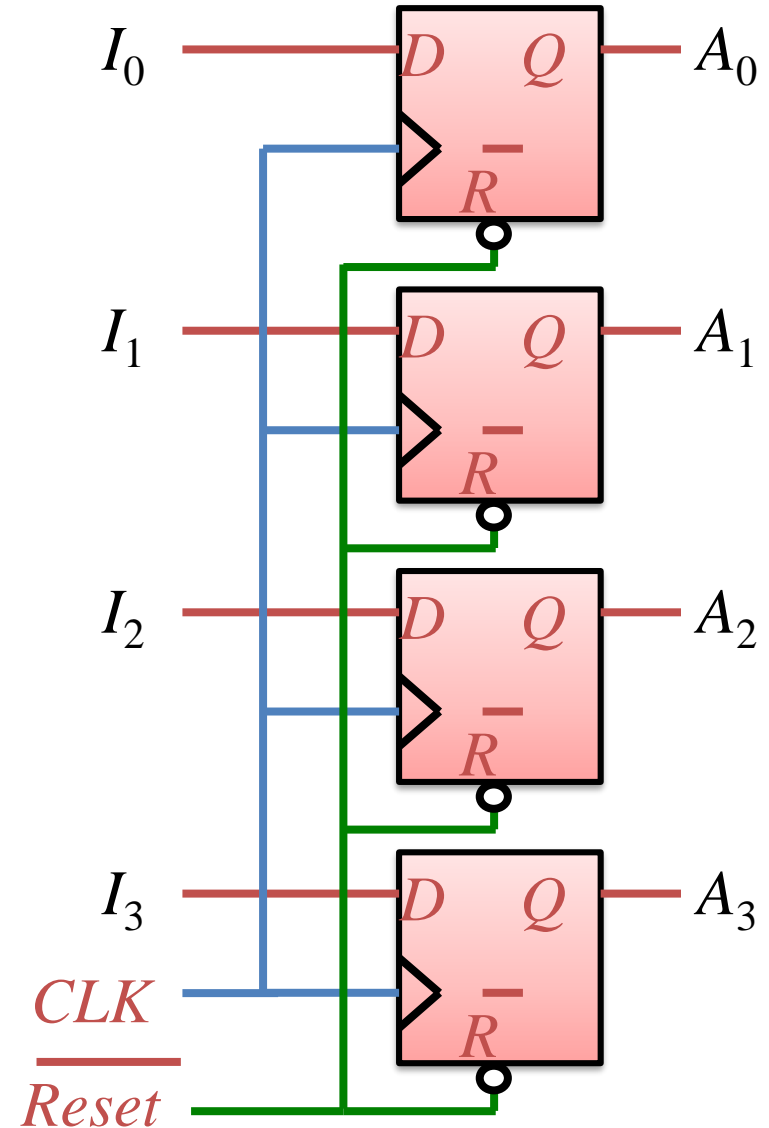
Note: New data has to go in with every clock



See carefully: Input at the dotted will be reflected to output : Just before rising edges

Registers with Parallel Load

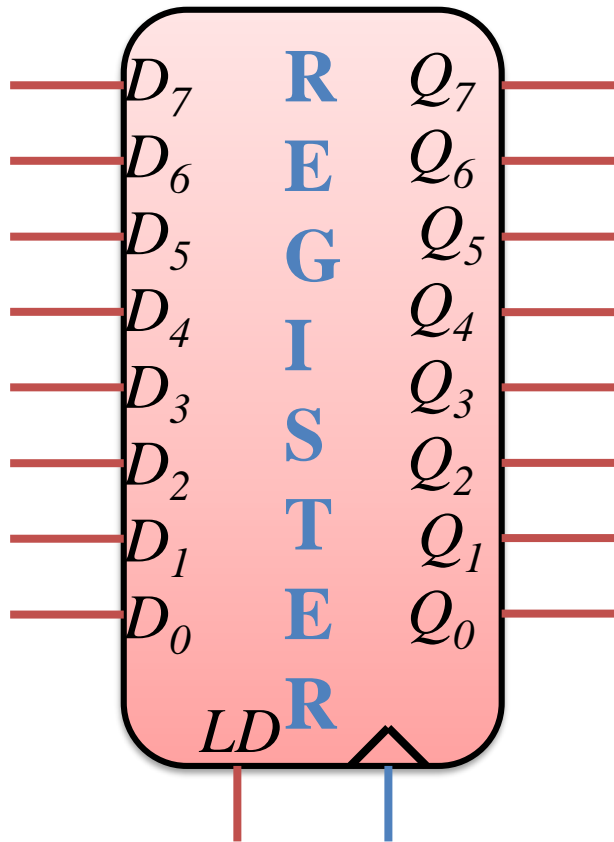
- Control **Loading** the Register with New Data



LD	$Q(t+1)$
0	$Q(t)$
1	D


Registers with Parallel Load

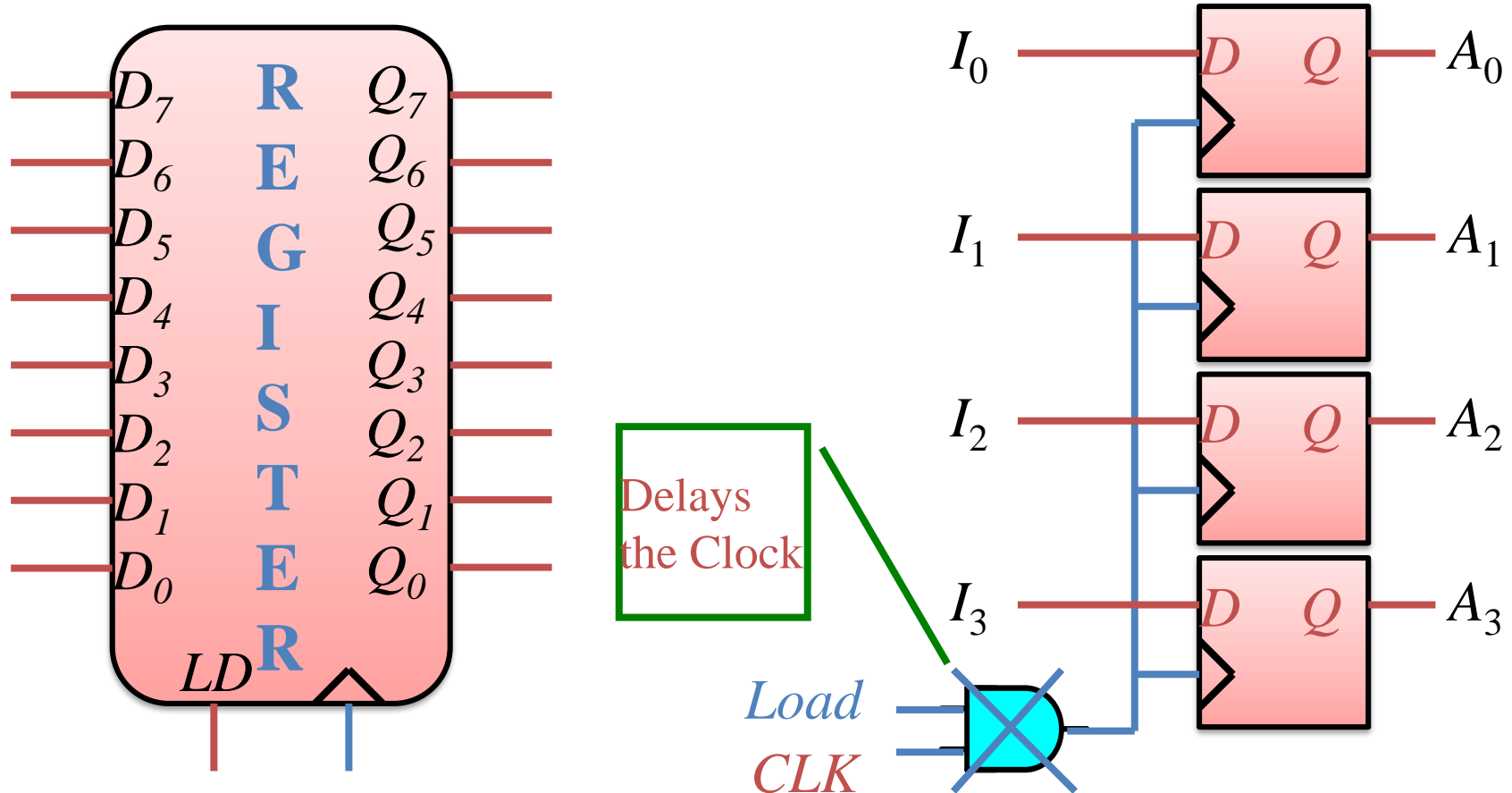- Should we block the “Clock” to keep the “Data”?



Registers with Parallel Load

- Circulate the “old data”

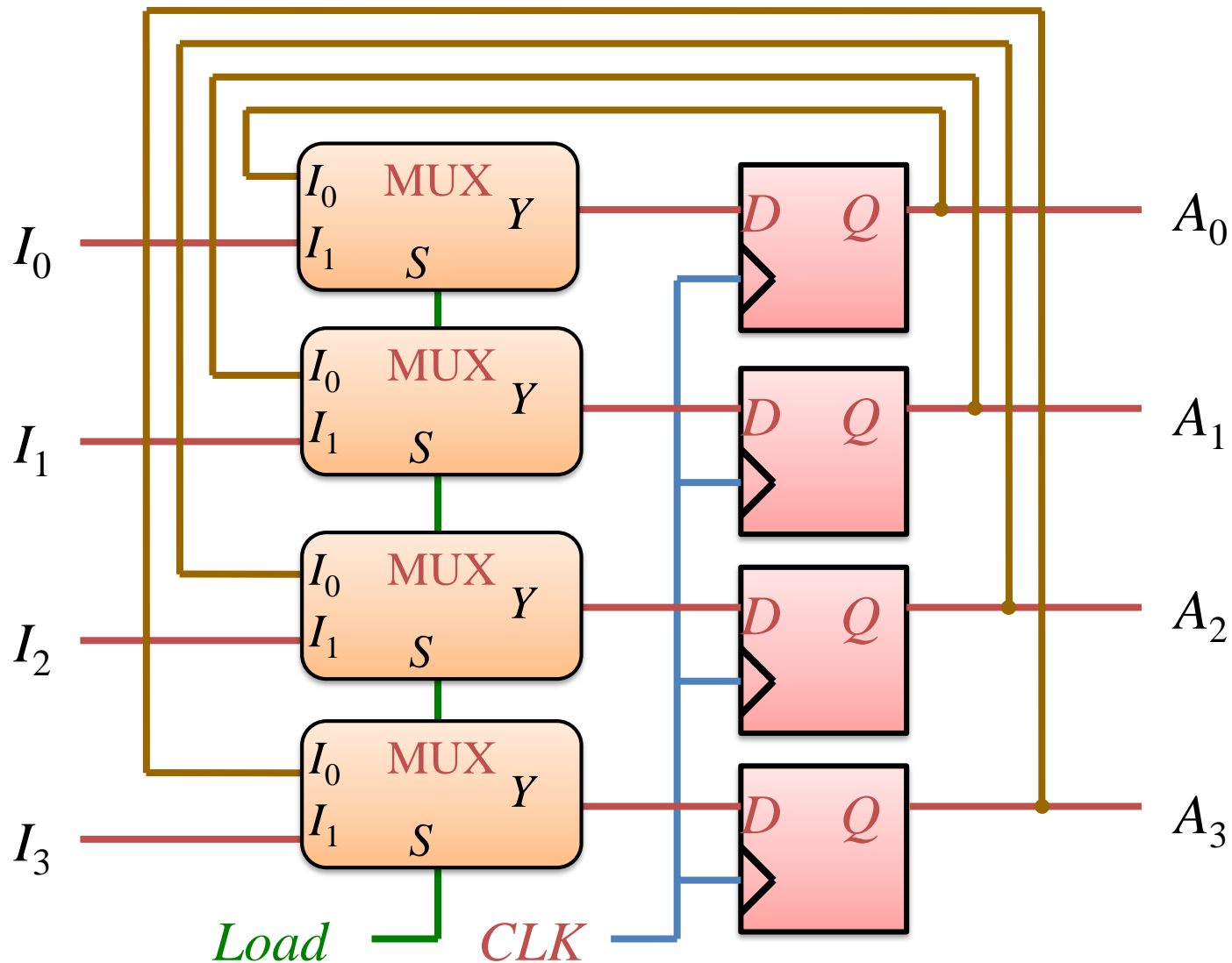

Shift Registers

- Register (Set of FFs)
- 4-Bit Shift Register (Example)
- Serial in Serial Out (SISO)

Shift Register

- Right Shift Example (Left shift is similar)
 - Move each bit one position right
 - Shift in 0 to leftmost bit

Q: Do four right shifts on 1001, showing value after each shift


A: 1001 (original)

0100


0010

0001


0000

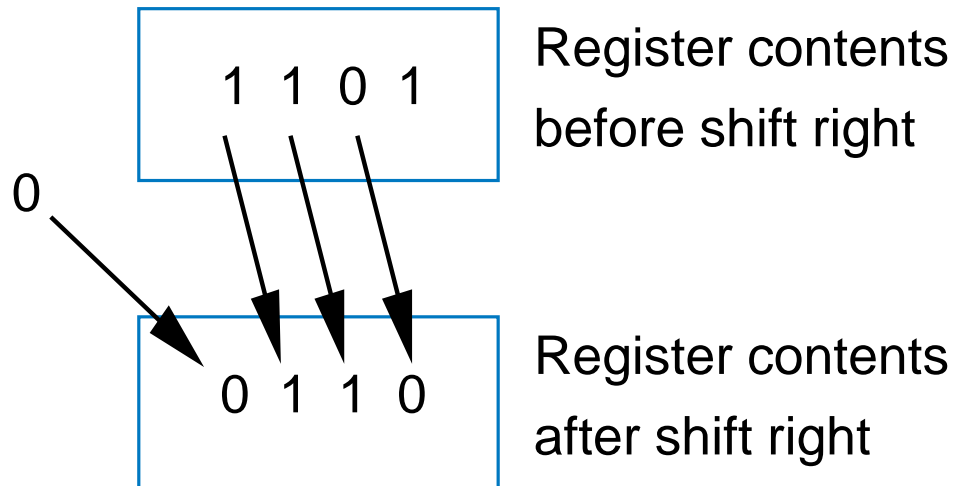

Shift Register

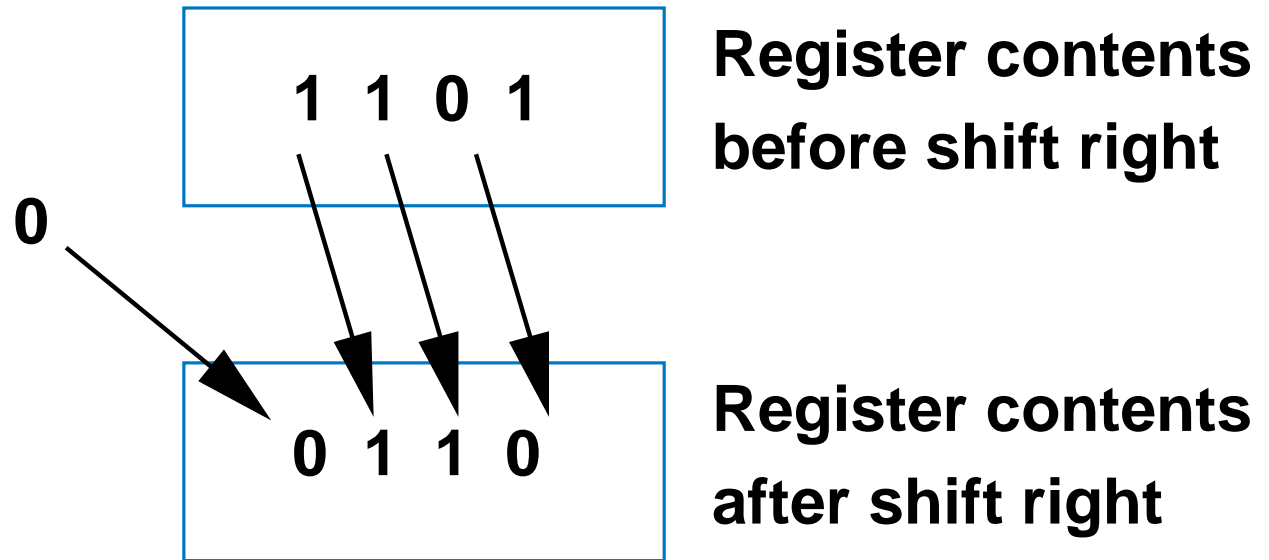


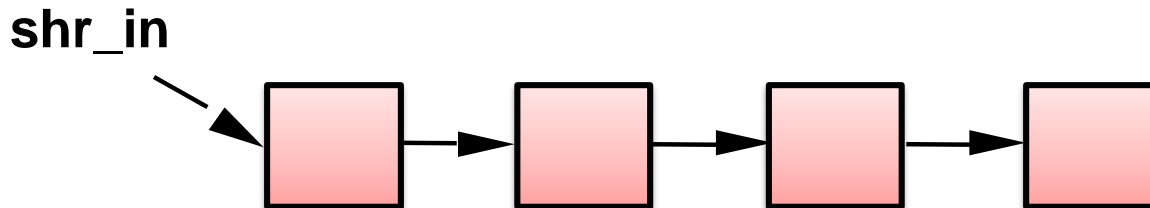- **Implementation: Connect flip-flop output to next flip-flop's input**




Shift Registers

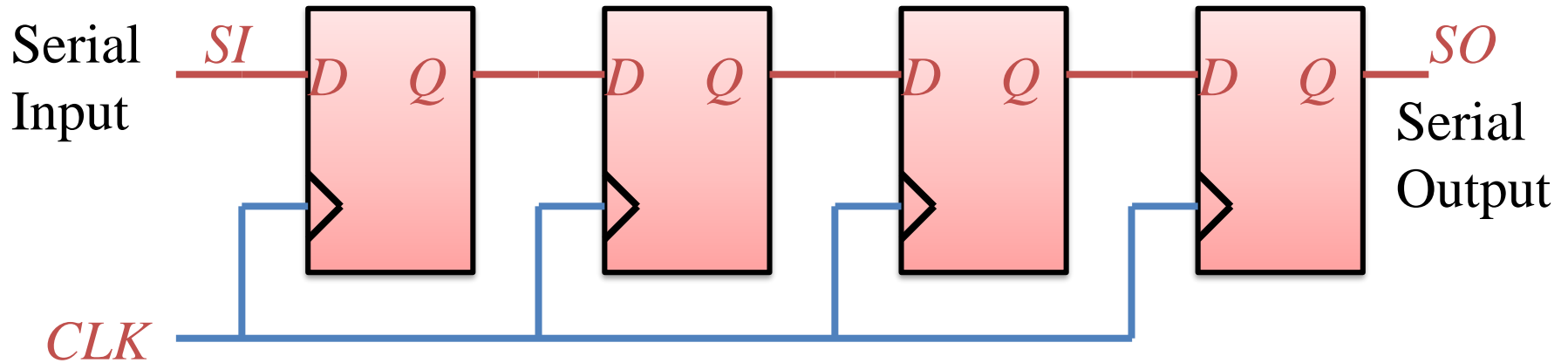- 4-Bit Shift Register
- Serial in Serial Out (SISO)




Shift Registers (SISO)

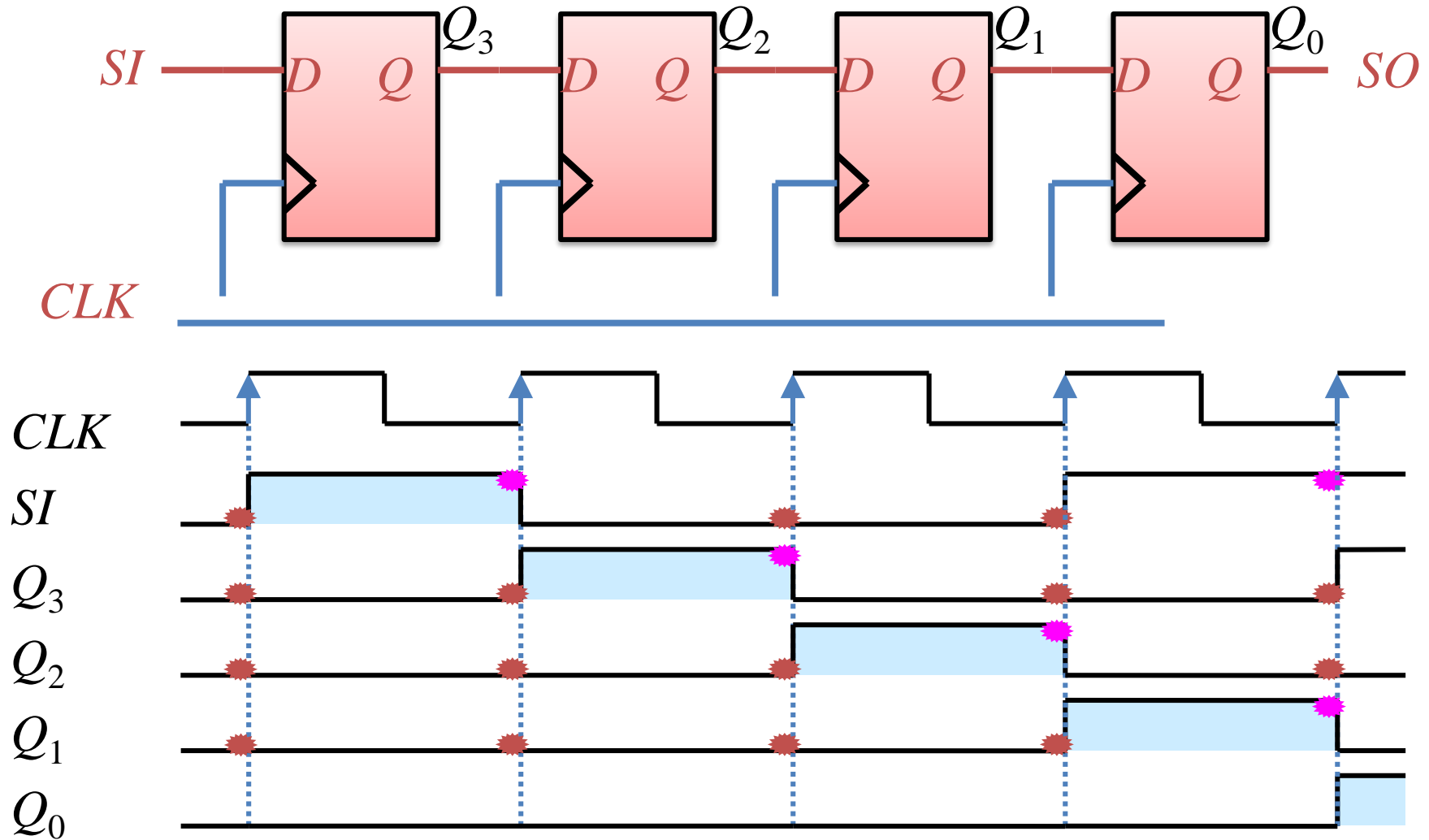


Shift Register with Control

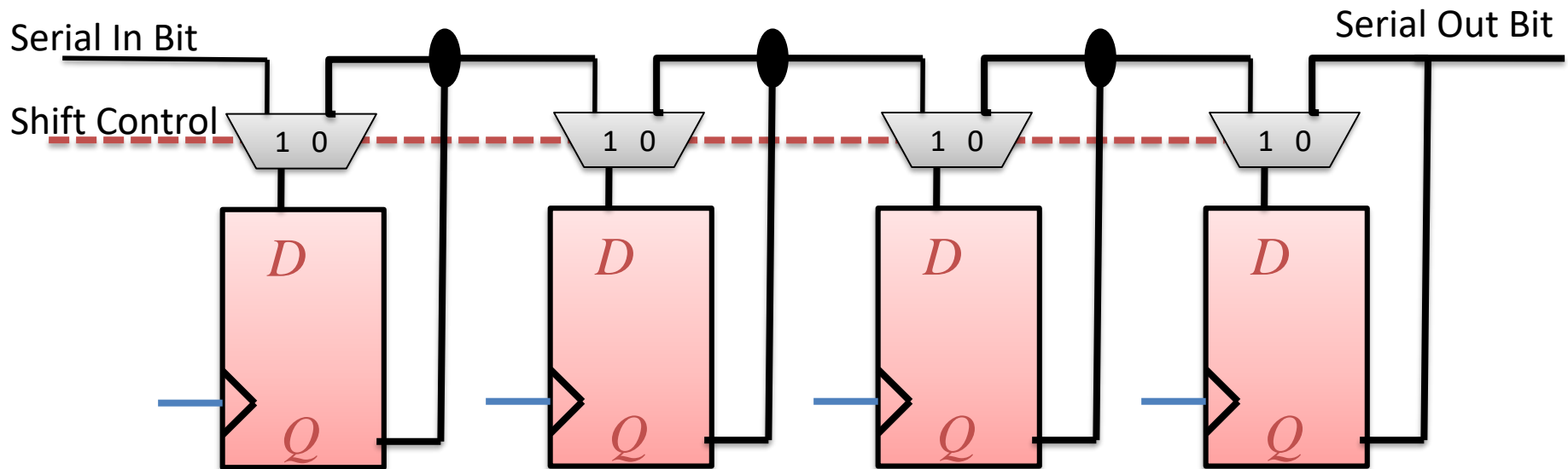- To allow register to either shift or retain, use 2x1 muxes
 - **Shift Control: shr: 0 means retain, 1 shift**
 - shr_in: value to shift in : May be 0/1, or right most bit



Shift Register with Control

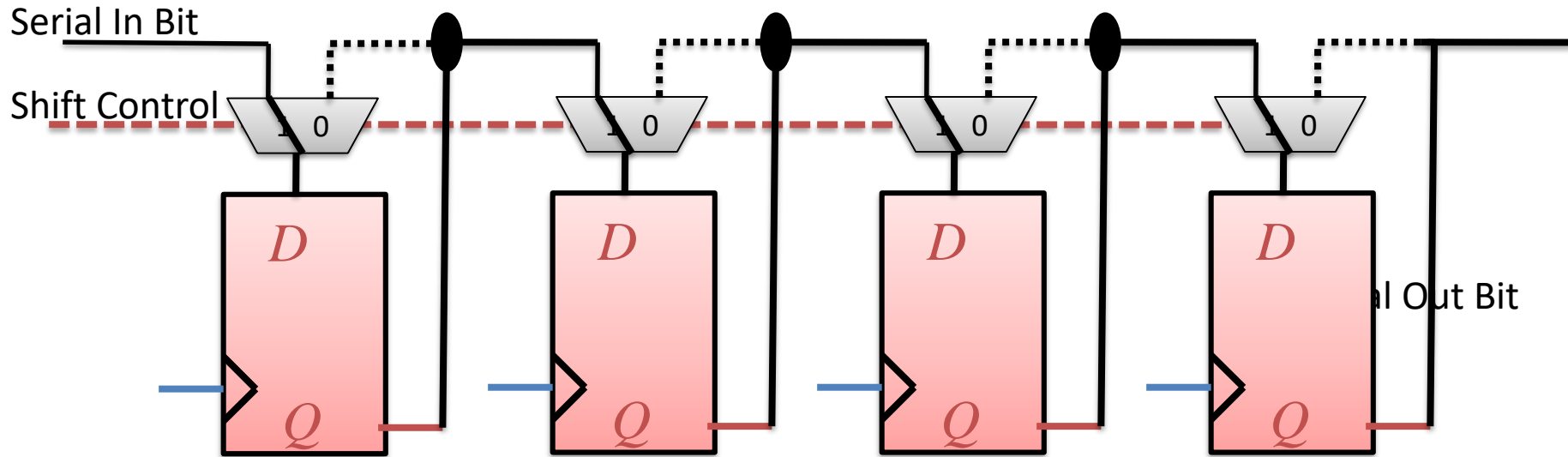Shift Control=1, Do one right shift per cycle



Shift Register with Control

Shift Control=0, No change to Data

