

**CS221: Digital Design**

# **FSM Optimization : Implication Chart Method**

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

# Outline

- FSM State Optimization
  - Row Matching Method (Last Class)
  - Partitioning Method (Last Class)
  - Implication Chart Method
- FSM State Encoding
  - Binary, gray, One-hot
  - Heuristic Based

# FSM State Minimization

- Minimizing number of state reduce
  - Requirement of bigger size state register
  - Possibly reduce the CCC

## Some Definitions

- **State Equivalence:** S1 and S2 are equivalent if for every input sequence applied to machine goes to same NS and Output
  - If  $S1(t+1)=S2(t+1)$  and  $Z1=Z2$  then  $S1=S2$
- **Distinguishable States:** Two states S1 and S2 are Distinguishable iff there exist at least one finite input sequence which produce different outputs from S1 and S2

# Methods

- Row Matching Method or Partitioning Method
- Implication Chart Method

# Implication Chart Methods

# FSM Reduction: Implication Chart

## Method

Problem:



Single input X, Single output Z

Output a 1 whenever the serial sequence 010 or 110 has been observed at the inputs

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_0$	$S_0$	0	0
01	$S_4$	$S_0$	$S_0$	1	0
10	$S_5$	$S_0$	$S_0$	0	0
11	$S_6$	$S_0$	$S_0$	1	0
  
# Implication Chart Method

Enumerate all possible combinations of states taken two at a time



Naive Data Structure:

$X_{ij}$  will be the same as  $X_{ji}$

Also, can eliminate the diagonal



# Implication Chart Method

## Filling in the Implication Chart

Entry  $X_{ij}$  — Row is  $S_i$ , Column is  $S_j$


$S_i$  is equivalent to  $S_j$  if outputs are the same and next states are equivalent

$X_{ij}$  contains the next states of  $S_i$ ,  $S_j$  which must be equivalent if  $S_i$  and  $S_j$  are equivalent

If  $S_i$ ,  $S_j$  have different output behavior, then  $X_{ij}$  is crossed out
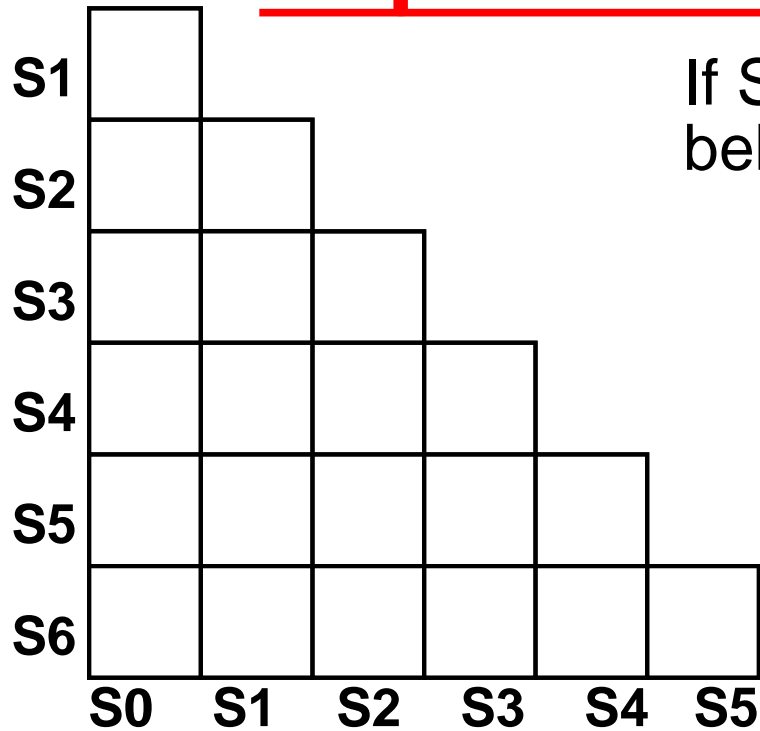
# Implication Chart Method

If  $S_i, S_j$  have different output behavior, then  $X_{ij}$  is crossed out



Starting Implication Chart


		NS		Output	
Input	P State	X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_0$	$S_0$	0	0
01	$S_4$	$S_0$	$S_0$	1	0
10	$S_5$	$S_0$	$S_0$	0	0
11	$S_6$	$S_0$	$S_0$	1 <sub>10</sub>	0

# Implication Chart Method

If  $S_i, S_j$  have different output behavior,  
then  $X_{ij}$  is crossed out

$S_4$  have different out put behavior with  
 $S_0, S_1, S_2, S_3, S_5$

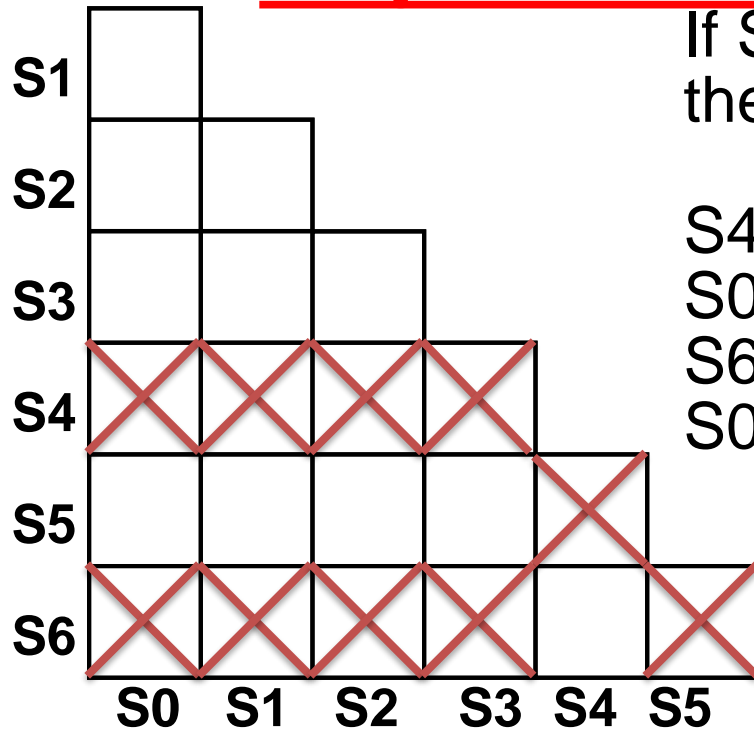
$S_6$  have different out put behavior with  
 $S_0, S_1, S_2, S_3, S_5$



Starting Implication Chart

		NS		Output	
Input	P State	X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_0$	$S_0$	0	0
01	$S_4$	$S_0$	$S_0$	1	0
10	$S_5$	$S_0$	$S_0$	0	0
11	$S_6$	$S_0$	$S_0$	1 <sub>11</sub>	0

# Implication Chart Method

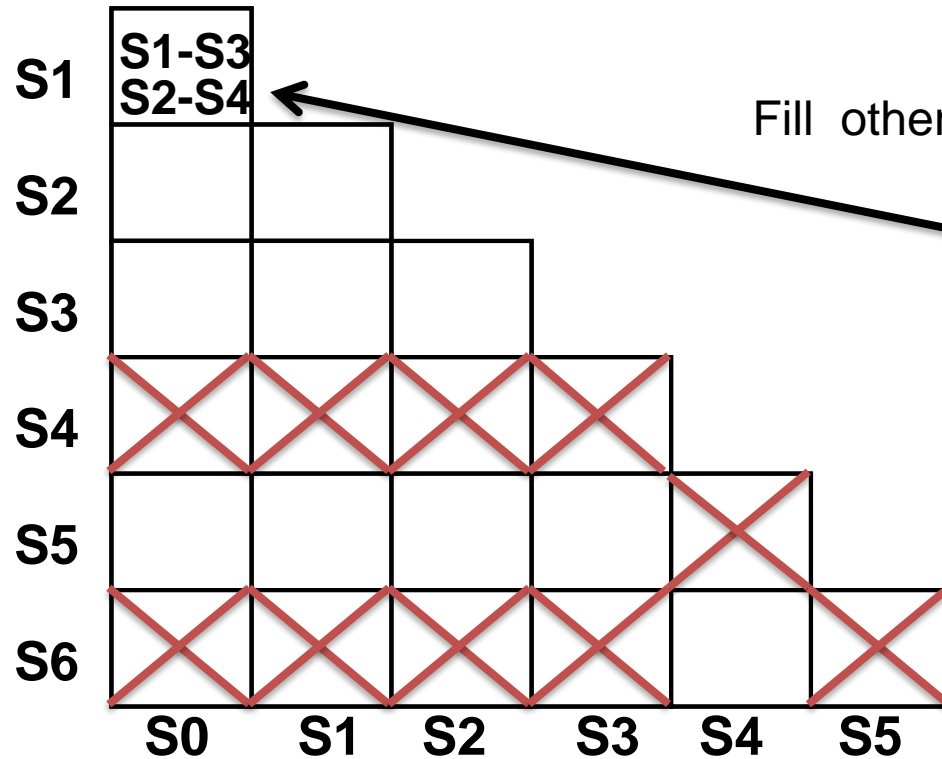


Fill other  $S_{ij}$  Based on Next State Transaction

$S_0$  :  $S_1, S_2$  when  $X=0, 1$

$S_1$  :  $S_3, S_4$  when  $X=0, 1$

		NS		Output	
Input	P State	$X=0$	$X=1$	$X=0$	$X=1$
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_0$	$S_0$	0	0
01	$S_4$	$S_0$	$S_0$	1	0
10	$S_5$	$S_0$	$S_0$	0	0
11	$S_6$	$S_0$	$S_0$	1 <sub>12</sub>	0

# Implication Chart Method

 


Fill others S<sub>ij</sub> Based on Next State Transaction

Starting Implication Chart

Input	P State	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
0	S <sub>1</sub>	S <sub>3</sub>	S <sub>4</sub>	0	0
1	S <sub>2</sub>	S <sub>5</sub>	S <sub>6</sub>	0	0
00	S <sub>3</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
01	S <sub>4</sub>	S <sub>0</sub>	S <sub>0</sub>	1	0
10	S <sub>5</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
11	S <sub>6</sub>	S <sub>0</sub>	S <sub>0</sub>	1 <sub>13</sub>	0

# Implication Chart Method

 


**S2 and S4  
have  
different  
I/O  
behavior**

This implies that  
S1 and S0 cannot  
be combined

Marked with Cross

# Implication Chart Method

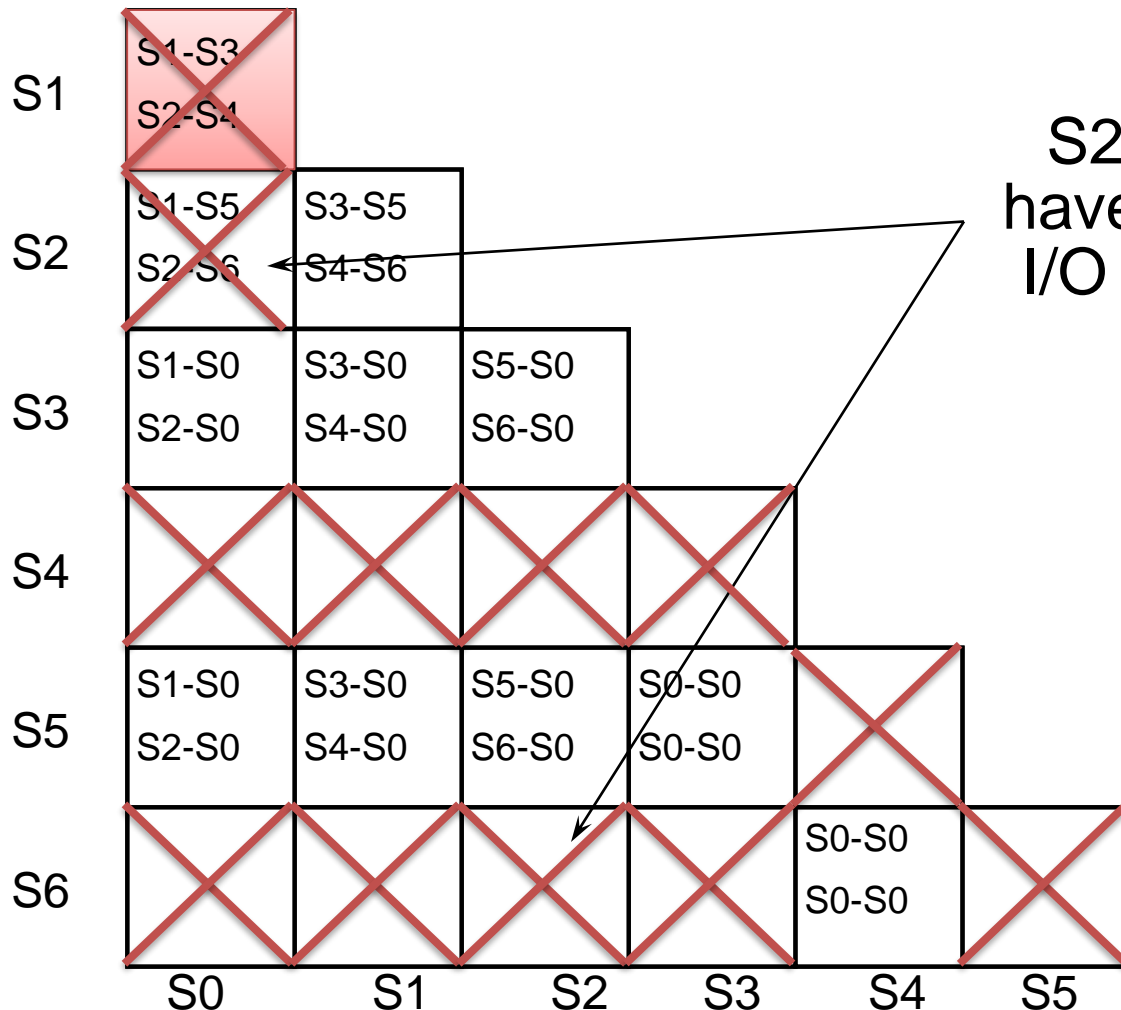


S2 and S6  
have different  
I/O behavior

This implies that  
S2 and S0 cannot  
be combined


Marked with Cross

# Implication Chart Method

 




# Implication Chart Method

 


**S1 S0 is already crossed**

**So S3 S0**


# Implication Chart Method

 

# Implication Chart Method

 


# Implication Chart Method

 

**S2 S0 is already crossed**

**So S5 S0**

# Implication Chart Method

 


S3 and S5 are equivalent  
S4 and S6 are equivalent  
S1 and S2 are equivalent

**Second Pass Adds No New Information**

# Final : Reduce State Table

- Reduces State table

Input	P State	NS		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_0$	$S_0$	0	0
01	$S_4$	$S_0$	$S_0$	1	0
10	$S_5$	$S_0$	$S_0$	0	0
11	$S_6$	$S_0$	$S_0$	1	0

 

Input	PS	NS		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1'$	$S_1'$	0	0
0 or 1	$S_1'$	$S_3'$	$S_4'$	0	0
00 or 10	$S_3'$	$S_0$	$S_0$	0	0
01 or 11	$S_4'$	$S_0$	$S_0$	1	0